


Example

PROB 4.14

Solve 4.6 by mesh analysis
(change powers of 10)

Can see that only is in this part
I.H.J.

same idea GA portion

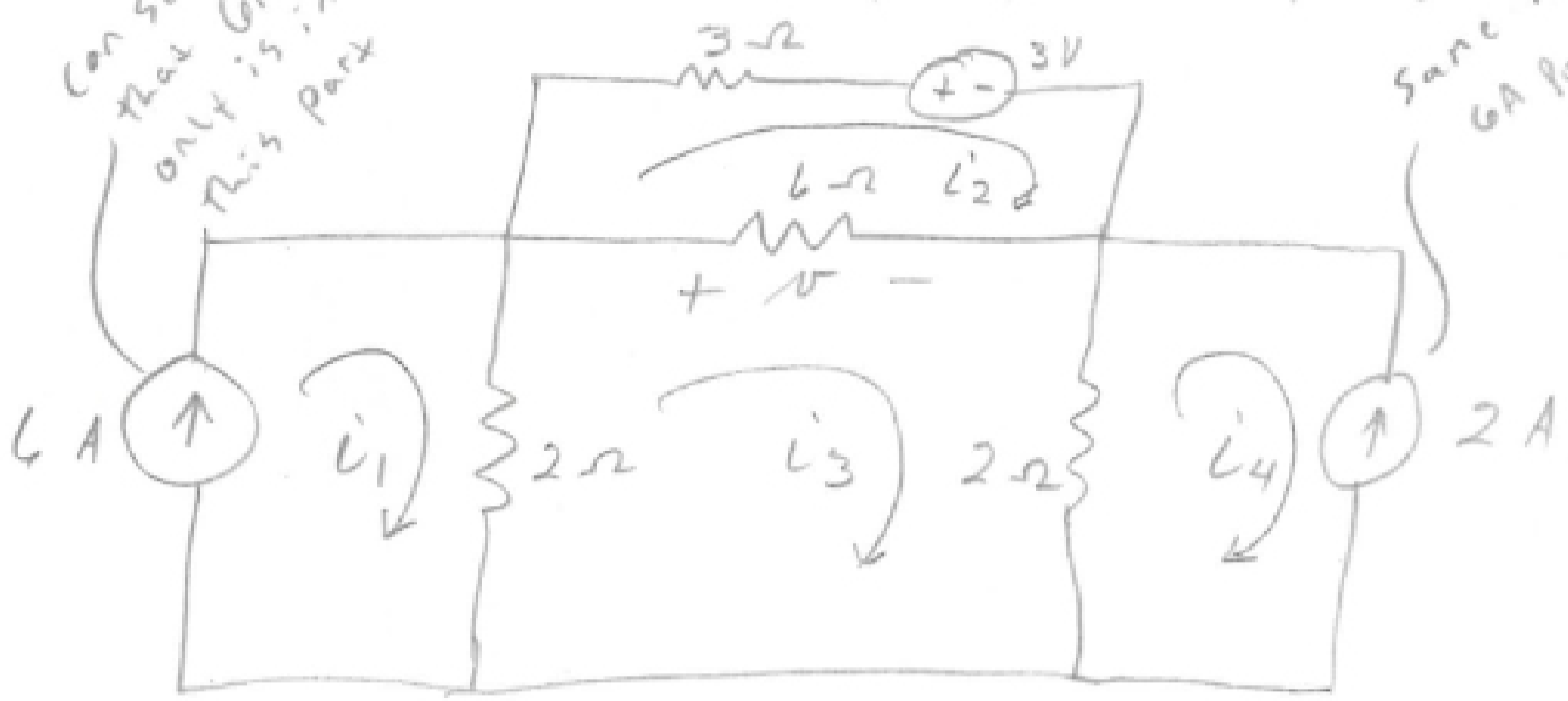

Find v

$$i_1 = 4$$

$$i_4 = -2$$

$$M2: 3i_2 + 3 + 6(i_2 - i_3) = 0$$

$$M3: 2(i_3 - i_1) + 6(i_3 - i_2) + 2(i_3 - i_4) = 0$$

$9i_2 - 6i_3 = -3$
$-6i_2 + 10i_3 = 8$

$$2(i_1 + i_4)$$

$$\therefore i_2 = -\frac{1}{3} + \frac{2}{3}i_3$$

$$i_3 = \frac{4}{5} + \frac{3}{5}i_2$$

$$= \frac{4}{5} - \frac{1}{5} + \frac{2}{5}i_3$$

$$\frac{3}{5}i_3 = \frac{3}{5}$$

$$i_3 = 1$$

$$\therefore i_2 = -\frac{1}{3} + \frac{2}{3}(1)$$

$$i_2 = \frac{1}{3}$$


$$\therefore v = 6(i_3 - i_2)$$

$$= 6(1 - \frac{1}{3})$$

$$v = 4 \text{ V}$$

B. Circuits containing current sources

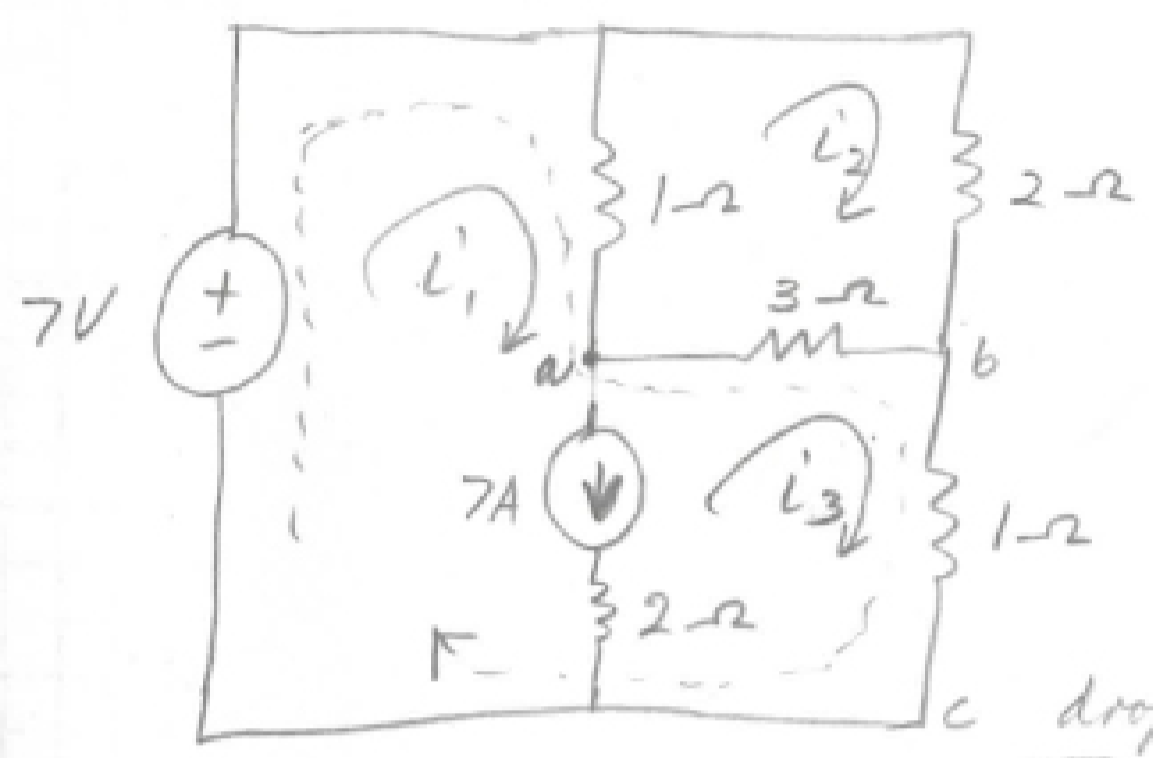1. Can't use a current source in a KVL eqn.



The 7A Source does not solely exist in its own circuit - have to create SUPERMESH

a) KVL: M1 $-7 + 1(i_1 - i_2) + 3(i_3 - i_2) + i_3 = 0$ ①

M2 $1(i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0$ ②

M3 same as for M1

Get 3rd eqn from current source relation

$i_1 - i_3 = 7$ or $i_3 = i_1 - 7$ ③

b) Trick: open current source to get "supermesh"

c) Substituting for i_3 gives: (or could solve 3rd order)


$-7 + (i_1 - i_2) + 3(i_1 - 7 - i_2) + (i_1 - 7) = 0$

$(i_2 - i_1) + 2i_2 + 3(i_2 - i_1 + 7) = 0$

or $\begin{bmatrix} 5 & -4 \\ -4 & 6 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 35 \\ -21 \end{bmatrix}$

$i_1 = 9A$; $i_2 = 2.5A$; $i_3 = 2A$ ↙ $i_1 - 7$

Concept of the supermesh

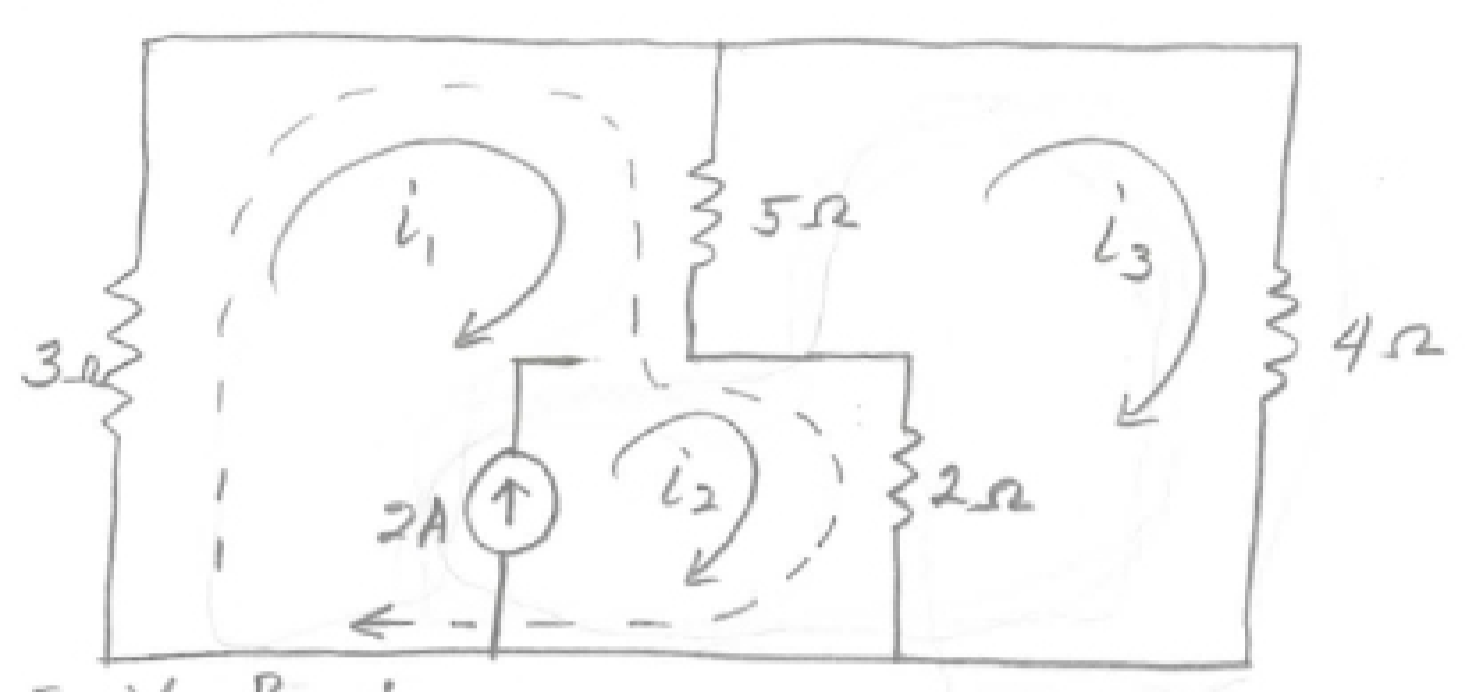

Hook
~~4.2~~
 4.2, 4.3
 Reg
 Mark

Find $P_{4\Omega}$:

1. The 2A source cannot be expressed in terms of a single mesh current.

\therefore Open source to form supermesh

2. M3: $5(i_3 - i_1) + 4i_3 + 2(i_3 - i_2) = 0$

SM: $3i_1 + 5(i_1 - i_3) + 2(i_2 - i_3) = 0$

$i_2 - i_1 = 2$

$P = I^2 \cdot R$

$-7i_1 + 11i_3 = 4$

$10i_1 - 7i_3 = -4$

$$\therefore i_3 = \frac{\begin{vmatrix} -7 & 4 \\ 10 & -4 \end{vmatrix}}{\begin{vmatrix} -7 & 11 \\ 10 & -7 \end{vmatrix}} = \frac{28 - 40}{49 - 110} = \frac{12}{61} = 0.197 \text{ A}$$

$\therefore P_{4\Omega} = (0.197)^2 (4) = 0.155 \text{ W}$