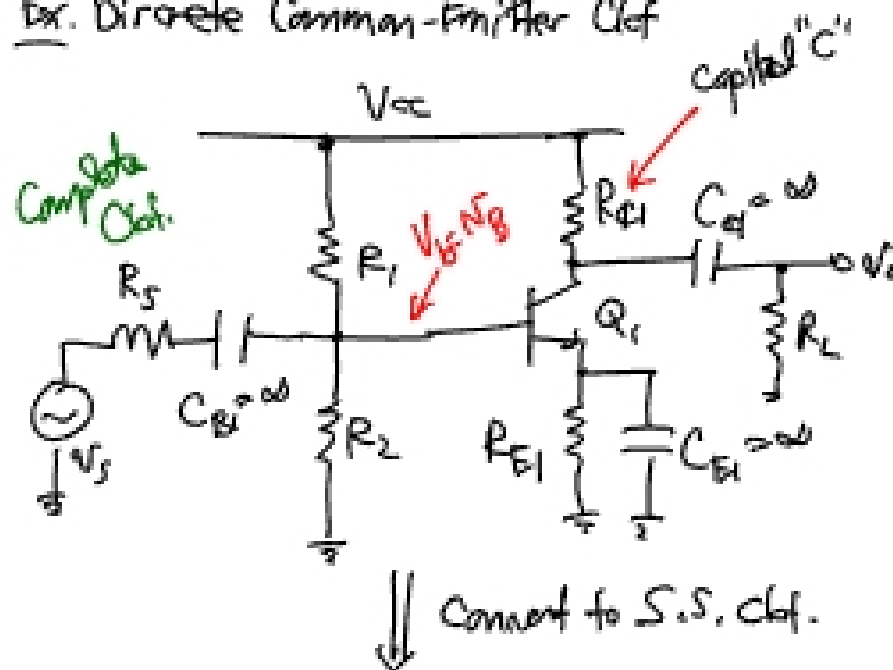


Lecture 4: Inspection Analysis

- Announcements:
- Course website has been up and running
 - ↳ Just point your browser to <http://www-inst.eecs.berkeley.edu/~ee140/sp11/>
- I'm here today, but as your syllabus shows, will be traveling again next Tuesday, 2/1
 - ↳ Flying back next Tuesday, 2/1
 - ↳ Make-up lecture:
- -----
- Lecture Topics:
 - ↳ Procedure for Small Signal Analysis
 - ↳ Inspection Formulas
 - ↳ 1-Tx Amplifier Examples
- -----



Procedure for Small-Signal Analysis

Ex. Discrete Common-Emitter Ckt



Procedure:

- ① Find the DC operating pt. → get the DC voltages & currents of all nodes & branches, respectively
- ② Determine the small-signal (S.S.) parameters for devices in the signal path.
- ③ Convert the full ckt. to the S.S. ckt.
 - ⇒ Zero out the DC sources
 - ⇒ short out large caps.
- ④a IF needed, replace the Xrista w/ its S.S. Ckt.
 - ⇒ this should not be NEEDED often!
 - ⇒ when is it needed? → generally, only in cases where there is feedback
- ④b Analyze by inspection based on prior S.S. analysis experience!
 - Go through Inspection Analysis handout
 - ↳ Best to commit the equations on this sheet to memory

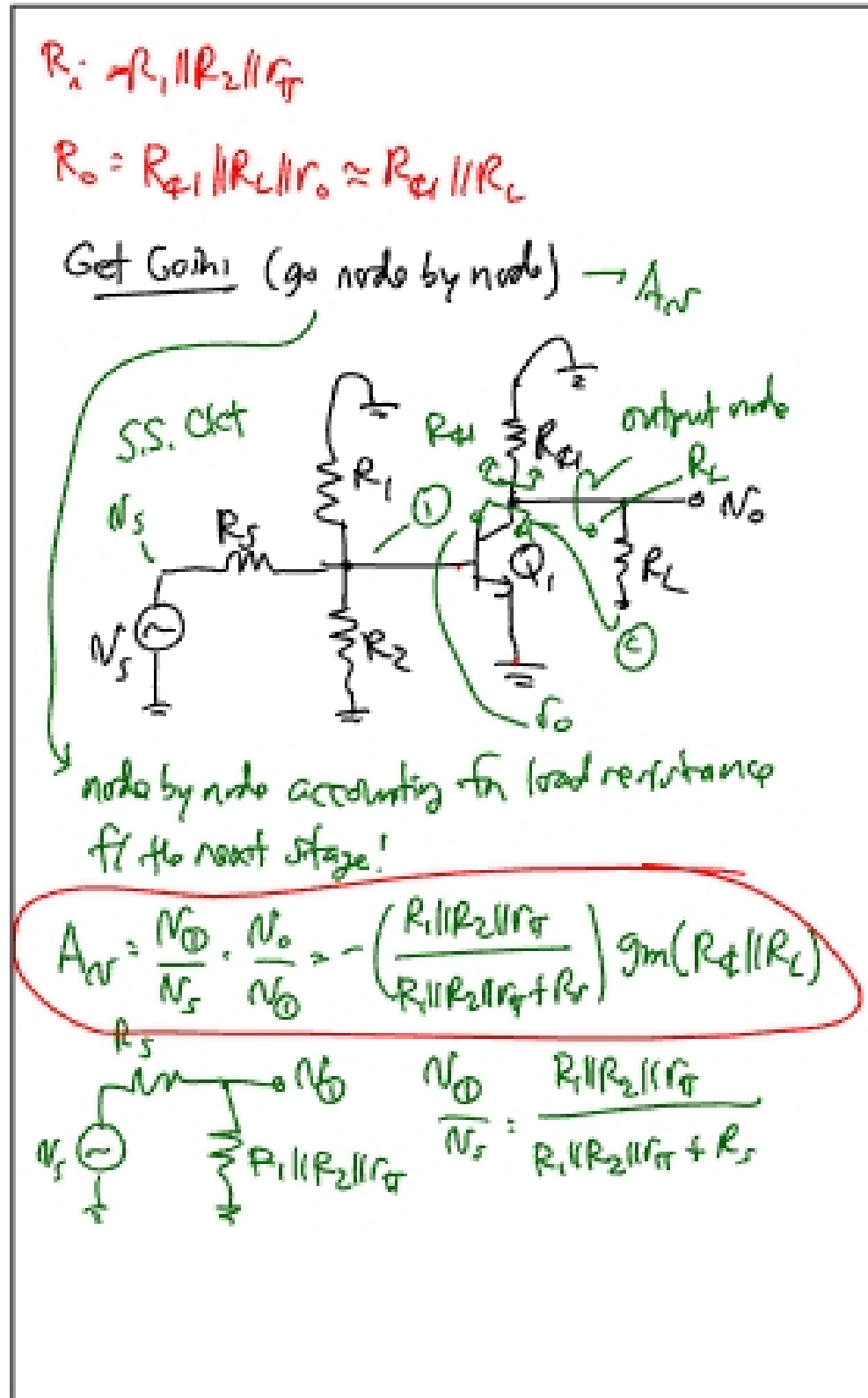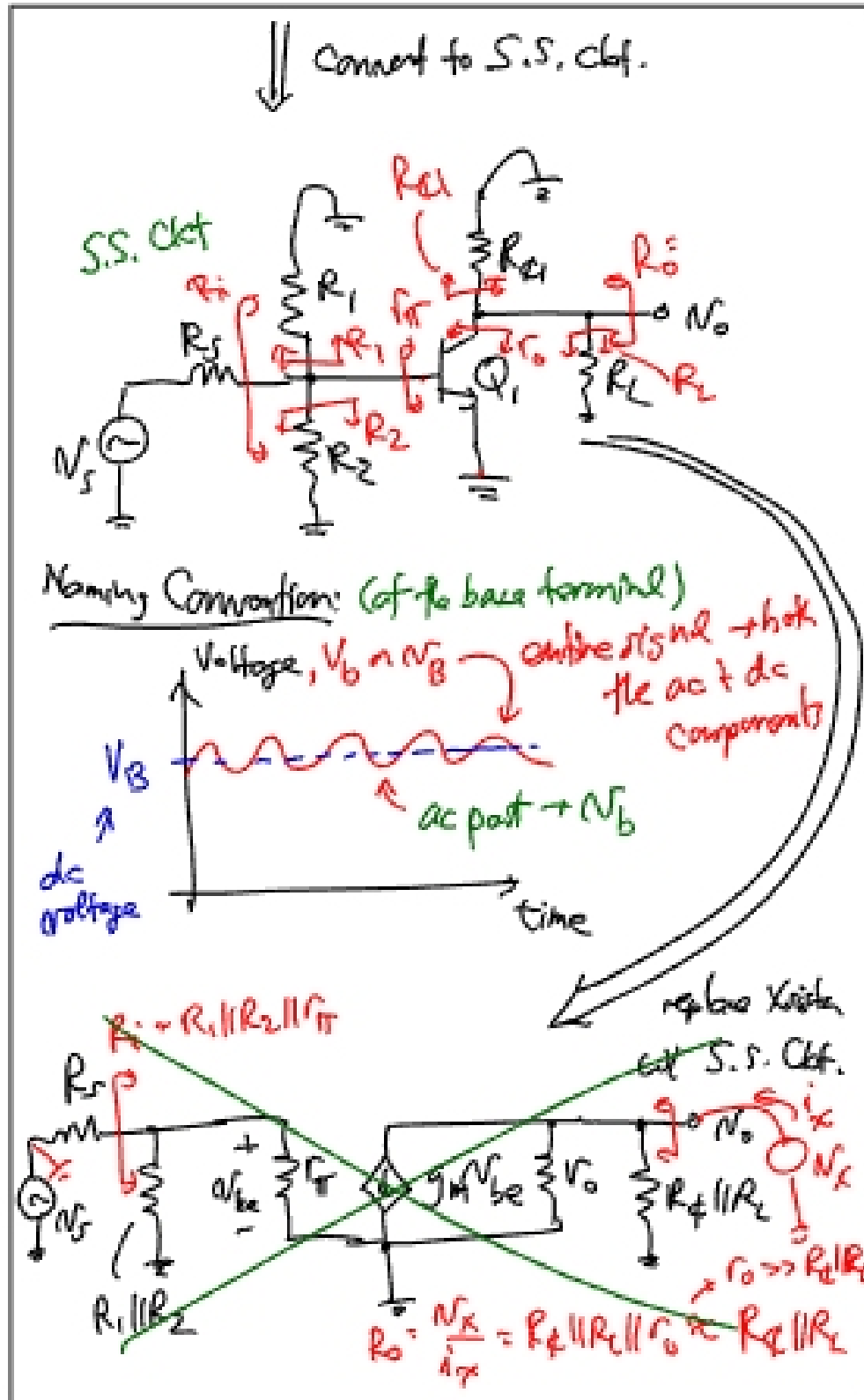

$$\frac{v_o}{v_i} = -G_m R_{\odot} = -g_m (R_c \parallel R_L \parallel r_o) \approx -g_m (R_c \parallel R_L)$$

$$\frac{g_m}{1 + g_m R_E} = g_m$$

$$R_{\odot} = R_c \parallel R_L \parallel r_o \approx R_c \parallel R_L$$

$$R_i = r_{\pi} + (\beta + 1) R_E$$

$$\frac{v_o}{v_i} = \frac{R_E}{r_{\pi} + R_E} = \frac{(\beta + 1) R_E}{r_{\pi} + (\beta + 1) R_E}$$

$$\frac{1}{g_m} \rightarrow \frac{\beta}{g_m} = r_{\pi}$$

$$(R_E \parallel r_o) \approx R_E$$

$$R_o = r_o \parallel R_c \approx R_c$$

$$R_o = \frac{1}{g_m} \parallel R_E \approx \frac{1}{g_m}$$

Ex. Common-Collector: if $R_E \gg \frac{1}{g_m}$

Ex. Common-Base: $R_o = r_o \parallel R_c \approx R_c$

$$R_i = \frac{1}{g_m}$$

$$\frac{v_o}{v_i} = g_m (r_o \parallel R_c) \approx g_m R_c$$

\Rightarrow so far, we've been talking about "midband" analysis

\Rightarrow Bode Plot: (for the 1st amp we analyzed) C.E.

\Rightarrow we want this!
 \leftarrow use OCTC (open circ. time constant) analysis