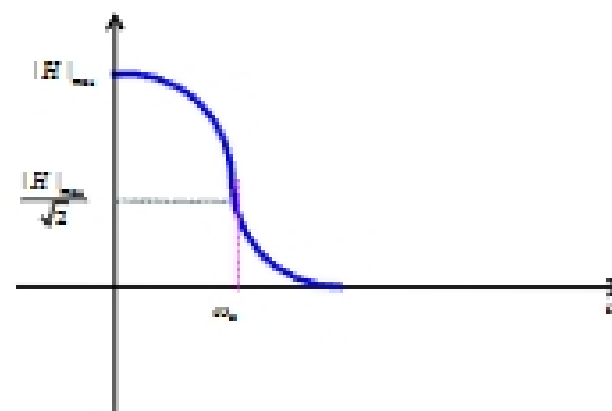



Low pass filters:

$$H(j\omega) = \frac{(k)\omega_c}{\omega_c + j\omega}$$




High pass filters:
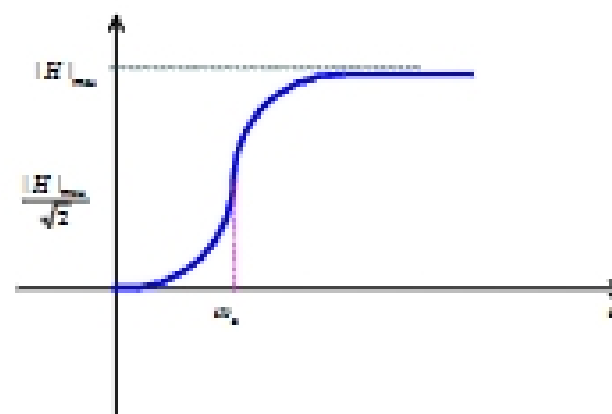
$$H(j\omega) = \frac{j\omega(k)}{\omega_c + j\omega}$$




Band-Pass filter:
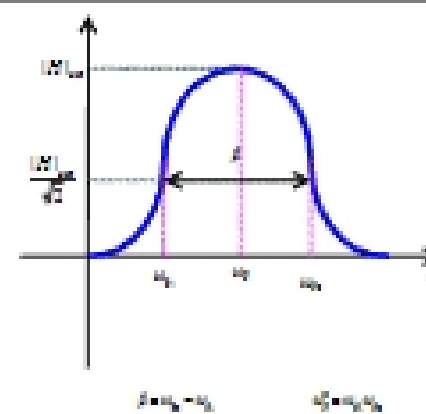
$$H(j\omega_c) = \frac{j\omega_c \beta(k)}{(\omega_c^2 - \omega^2) + j\omega_c \beta}$$



Band-reject filter:


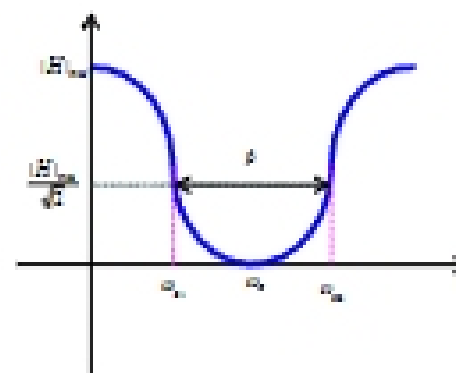
$$H(j\omega) = \frac{[\omega_c^2 - \omega^2](k)}{[\omega_c^2 - \omega^2] + j[\omega\beta]}$$



Design a low pass filter using a capacitor  $C = 0.4 \mu F$

With a cutoff frequency  $\omega_c = 5k \text{ rad/s}$

Solution:

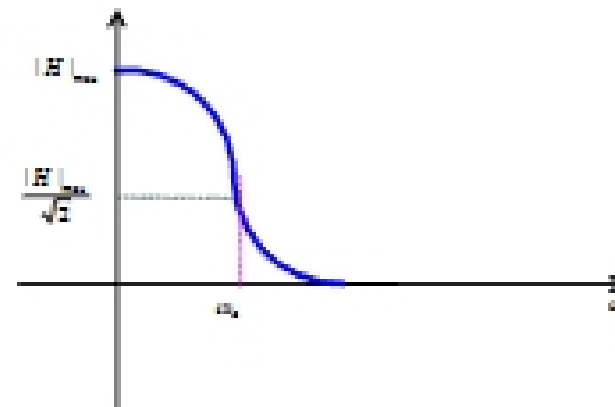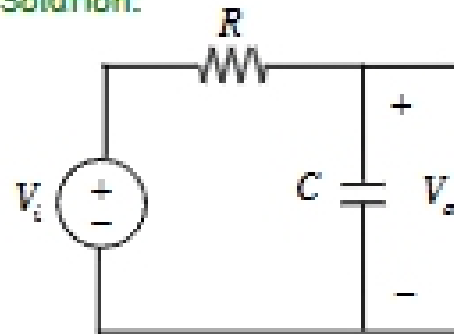

$$H = \frac{1}{R + \frac{1}{j\omega C}}$$

$$H = \frac{1}{1 + j\omega RC}$$

$$H = \frac{1/RC}{1/RC + j\omega}$$

$$H = \frac{\omega_c}{\omega_c + j\omega}$$

$$\omega_c = \frac{1}{RC}$$



$$5k = \frac{1}{R(0.4\mu)}$$

$$R = \frac{1}{(5k)(0.4\mu)}$$

$$R = 500\Omega$$

Connect a resistive load to the filter  $R_2 = 100k\Omega$

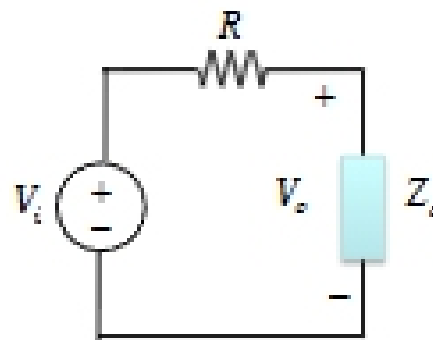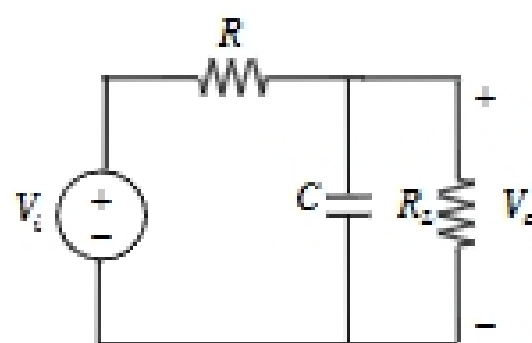Find the transfer function of the loaded filter.



$$Z_o = \frac{R_2 \left( \frac{1}{j\omega C} \right)}{R_2 + \left( \frac{1}{j\omega C} \right)}$$

$$Z_o = \frac{R_2}{1 + j\omega CR_2}$$

$$H = \frac{R_2}{R + \frac{R_2}{1 + j\omega CR_2}}$$

$$H = \frac{R_2}{R(1 + j\omega CR_2) + R_2}$$

$$H = \frac{R_2}{(R + R_2) + j\omega CRR_2}$$

$$H = \frac{R_2 / CRR_2}{(R + R_2) / CRR_2 + j\omega}$$

$$H = \frac{1/CR}{(R + R_2) / CRR_2 + j\omega}$$

$$H = \frac{k}{\omega_c + j\omega}$$

$$\omega_c = \frac{R + R_2}{RR_2 C}$$

$$\omega_c = \frac{500 + 100}{(500)(100)(0.4\mu)}$$

$$\omega_c = 30k \text{ r/s}$$

### Filter Circuits

#### \* Passive Filters:

Using passive elements ( Resistors, Inductors and Capacitors)

#### \* Active Filters:

Using OP. AMPS

Advantages of active filters:

- Size
- Weight
- Gain control
- Loading effect is negligible

### First order Low-Pass filter

Test:

$$\omega = 0 \quad V_o = ?$$

$$\omega = \infty \quad V_o = ?$$

