

# Lecture 21

## Frequency Response of Amplifiers

### (I)

#### Common-Emitter Amplifier

### Outline

- Review frequency domain analysis
- BJT and MOSFET models for frequency response
- Frequency Response of Intrinsic Common-Emitter Amplifier
- Effect of transistor parameters on  $f_T$


#### **Reading Assignment:**

Howe and Sodini, Chapter 10, Sections 10.1-10.4

# I. Frequency Response Review

## Phasor Analysis of the Low-Pass Filter

- Example:

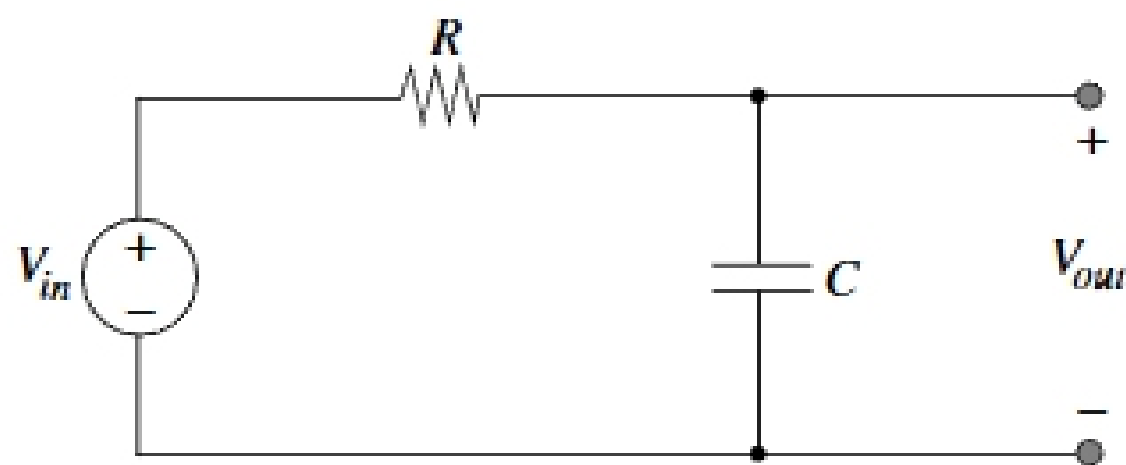

- Replacing the capacitor by its impedance,  $1 / (j\omega C)$ , we can solve for the ratio of the phasors  $V_{out} / V_{in}$


$$\frac{V_{out}}{V_{in}} = \frac{1 / j\omega C}{R + 1 / j\omega C}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + j\omega RC}$$

- $V_{out} \equiv$  Phasor notation

## Magnitude Plot of LPF

- $|V_{out} / V_{in}| \rightarrow 1$  for “low” frequencies
- $|V_{out} / V_{in}| \rightarrow 0$  for “high” frequencies

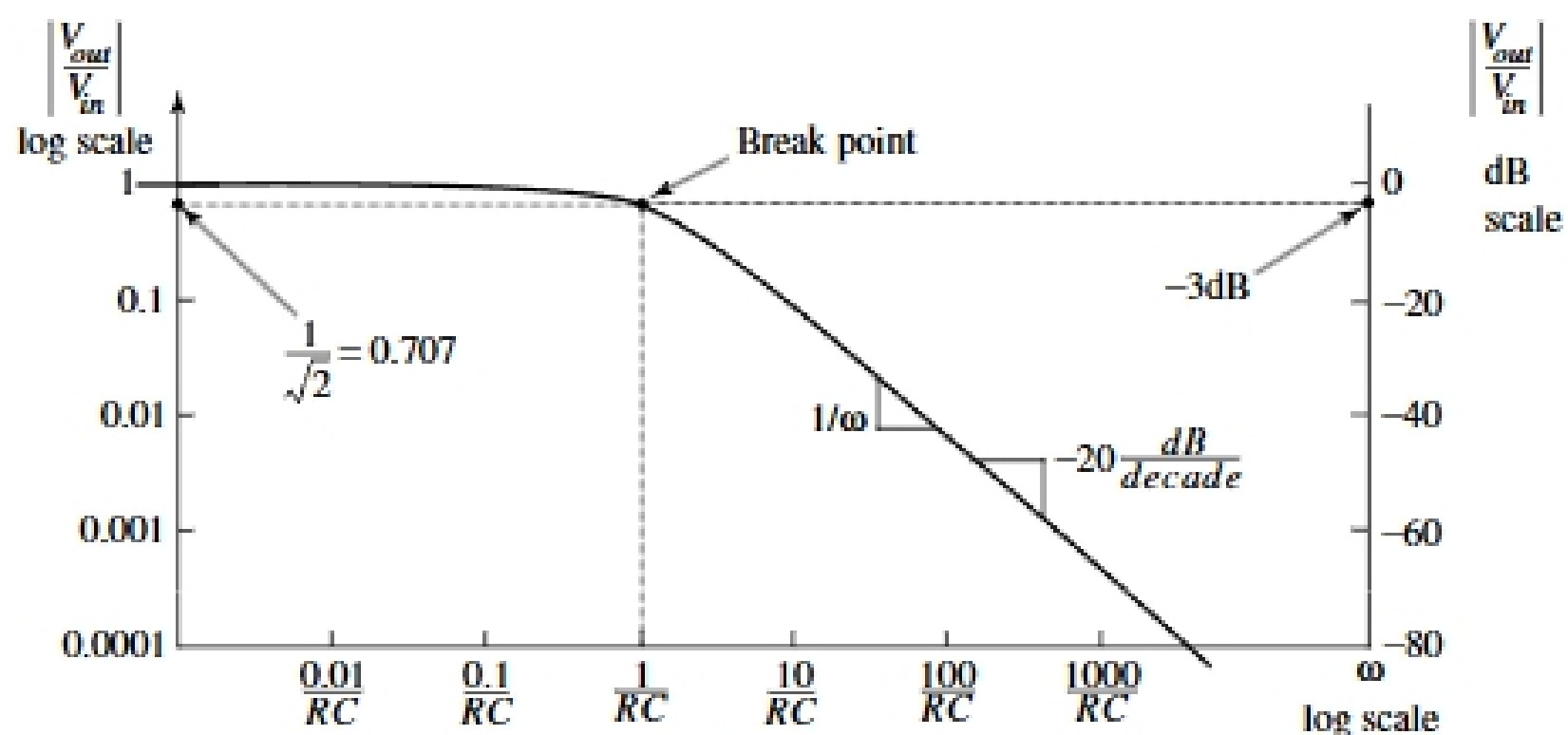

- The “break point” is when the frequency is equal to  $\omega_o = 1 / RC$
- The break frequency defines “low” and “high” frequencies.
- $\text{dB} \equiv 20 \log x \rightarrow 20\text{dB} = 10, 40\text{dB} = 100, -40\text{dB} = .01$
- At  $\omega_o$  the ratio of phasors has a magnitude of - 3 dB.