

EE 462: Laboratory Assignment 6  
Biasing of Transistors: N- channel MOSFET

by  
Dr. A.V. Radun and  
Dr. K.D. Donohue (10/2/03)  
Department of Electrical and Computer Engineering  
University of Kentucky  
Lexington, KY 40506

Laboratory # 6      Pre-lab due at lab sessions October 14, 15, and 16.  
Lab due at lab sessions October 21, 22, and 23.

### I. Instructional Objectives

- Analyze the metal oxide semiconductor (MOS) field effect transistor (FET) (MOSFET) using a DC load line
- Design a circuit to set a DC operating point for a MOSFET
- Measure the operating points in a DC biased FET circuit

See Horenstein 5.2, 7.3.1, and 7.3.3

### II. Background

Transistors are nonlinear devices, but over certain operating regions they can be approximated with linear models. To ensure a transistor operates in its linear region, a DC level is added to its input signal. The design of this DC level is referred to as biasing the transistor, and the DC values of the transistor's currents and voltages are referred to as the transistor's DC operating point, its bias point, or its quiescent operating point. Once a transistor is biased in its linear region, currents and voltages in a neighborhood around the bias point will vary linearly (approximately). It is assumed that the variation of the transistor's input signal and the transistor's currents and voltages are small enough that they do not move the system into nonlinear regions of operation (triode region or cutoff).

The simplest common source MOSFET amplifier biasing scheme is shown in Fig. 1. Since only the DC operating point is of interest right now, the time varying part of the input signal is omitted. The actual signal would be an AC signal added to the  $V_{GG}$  (Gate to Ground DC signal). The transfer characteristic (output as a function of the input) for this circuit can be derived. Apply KVL in Fig. 1 to obtain:

$$V_{out} = V_{DD} - R_D I_D, \quad (1)$$

then using a relationship between  $I_D$  and the gate voltage  $V_{GG}$  when the MOSFET is in the saturated (forward active) region, Eq. (1) becomes:

$$V_{out} = V_{DD} - R_D \frac{K_p}{2} (V_{GG} - V_{tr})^2 \quad \text{where } \frac{K_p}{2} = K \quad (\text{Horrenstein uses } K \text{ and Spice uses } K_p), \quad (2)$$

and  $V_{tr}$  is the threshold voltage between the cutoff and triode operation region.

 


Fig. 1 Basic common source amplifier biasing.

The operating points of  $V_{GG}$  and  $V_{out}$  are the DC or quiescent values at the input and output, respectively. Ideally, for a given  $V_{GG}$ ,  $V_{out}$  should not vary if the temperature varies or if different transistors of the same type are used. Unfortunately the MOSFET's transconductance parameter  $K_p$  cannot be controlled well during manufacturing. In addition,  $K_p$  also varies with temperature. For example, the 2N7000 MOSFET transistor's  $K_p$  can vary by more than 3.2 to 1. Note that  $K_p$  is not directly specified in the data sheet but rather the transconductance  $g_m$  is specified. The relationship between the MOSFET's transconductance  $g_m$  and  $K_p$  will be addressed in future labs. Since  $K_p$  varies significantly, a circuit biased correctly for one transistor may not be biased correctly for another transistor of the same manufacture and part number. Therefore, a more robust biasing scheme than the one shown in Fig. 1 is needed, such that the MOSFET's quiescent operating point is less sensitive to changes in  $K_p$ .

Insensitivity of the MOSFET's quiescent operating point can be achieved by adding a resistor  $R_S$  into the source branch of the circuit as shown in the Fig. 2. An analysis this new circuit, similar to before, results in the following equations:

$$V_{GG} = V_{GS} + I_D R_S \quad (3)$$

$$I_D = \frac{K_p}{2} (V_{GS} - V_{tr})^2 = \frac{K_p}{2} (V_{GG} - I_D R_S - V_{tr})^2 =$$

$$\frac{K_p}{2} (V_{GG} - V_{tr})^2 - K_p R_S (V_{GG} - V_{tr}) I_D + \frac{K_p}{2} R_S^2 I_D^2$$

(4)

$$I_D^2 - \left( \frac{2(V_{GG} - V_{tr})}{R_S} + \frac{2}{R_S^2 K_p} \right) I_D + \frac{(V_{GG} - V_{tr})^2}{R_S^2} = 0$$

(5)

 


Fig. 2 Basic common source amplifier with reduced  $K_p$  sensitivity.

Note that when  $R_S$  goes to zero (multiply by  $R_S^2$  and let  $R_S$  go to zero), Eq. (5) simplifies to:

$$I_D = \frac{K_p}{2} (V_{GS} - V_{tr})^2$$

(6)

which is the same relationship for the circuit in Fig. 1. (Why should this be expected?) On the other hand, if the  $R_S$  is large (relative to 2), then Eq. (5) is approximated by:

$$I_D^2 - \frac{2(V_{GG} - V_{tr})}{R_S} I_D + \frac{(V_{GG} - V_{tr})^2}{R_S^2} = 0$$

(7)

Notice that in Eq. (5),  $K_p$  only appeared in one term, whose effect was minimized (relative to the other terms) by a large  $R_S$  value. The quadratic in Eq. (7) is a perfect square and can be rewritten as: