

EECS150 - Digital Design
Lecture 29 - Asynchronous Sequential
Circuits

May 6, 2003
John Wawrzynek

Outline


- Synchronizers
 - Figures from
 - "Digital Design", John F. Wakerly
 - Prentice Hall, 2000
 - An excellent treatment of the topic.
- Purely asynchronous circuits
 - "self-timed" circuits
 - Mano has another class of asynchronous circuits (not covered in class)

Asynchronous Inputs to Synchronous Systems

- Many synchronous systems need to interface to asynchronous input signals:
 - Consider a computer system running at some clock frequency, say 1GHz with:
 - Interrupts from I/O devices, keystrokes, etc.
 - Data transfers from devices with their own clocks
 - Ethernet has its own 100MHz clock
 - PCI bus transfers, 66MHz standard clock.
 - These signals could have no known timing relationship with the system clock of the CPU.

“Synchronizer” Circuit

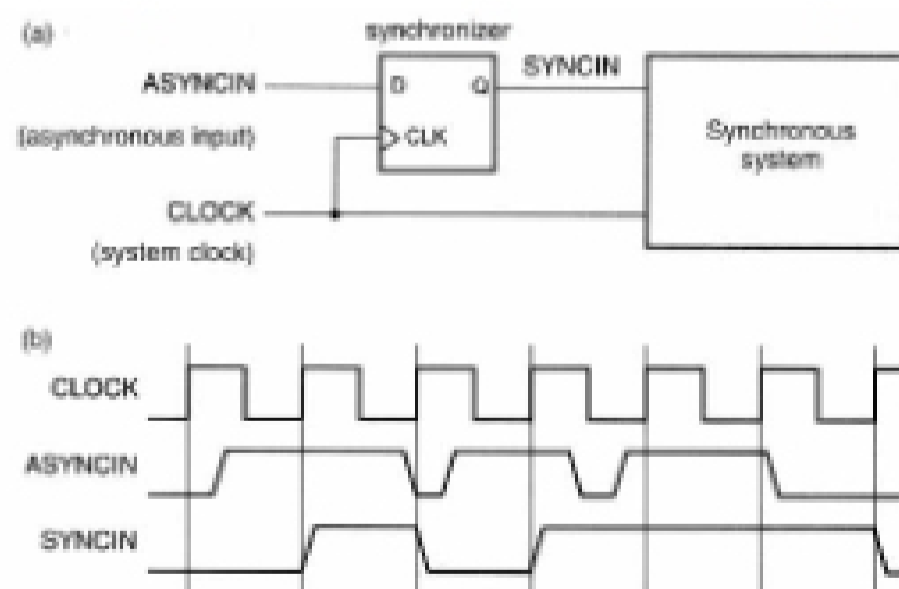
- For a single asynchronous input, we use a simple flip-flop to bring the external input signal into the timing domain of the system clock:



- The D flip-flop samples the asynchronous input at each cycle and produces a synchronous output that meets the setup time of the next stage.

“Synchronizer” Circuit

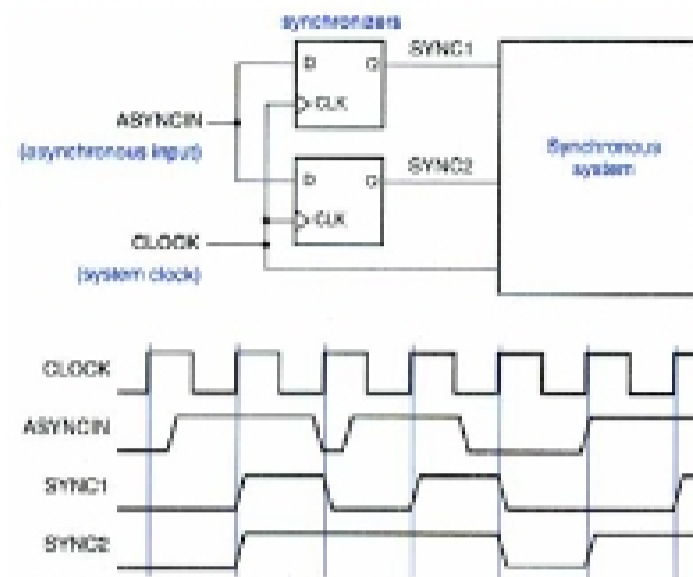
- It is essential for asynchronous inputs to be synchronized at only one place.



- Two flip-flops may not receive the clock and input signals at precisely the same time (clock and data skew).
- When the asynchronous changes near the clock edge, one flip-flop may sample input as 1 and the other as 0.

“Synchronizer” Circuit

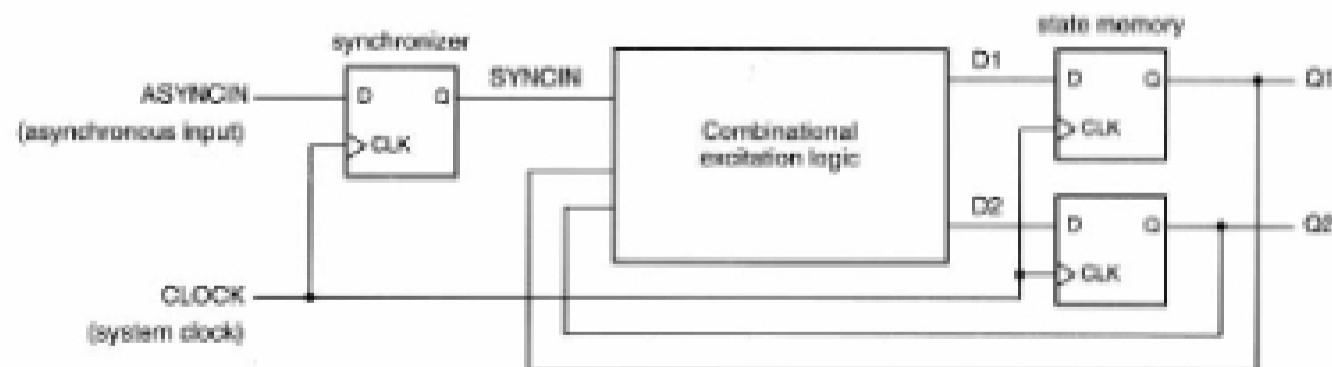- Single point of synchronization is even more important when input goes to a combinational logic block (ex. FSM)
- The CL block can accidentally hide the fact that the signal is synchronized at multiple points.
- The CL magnifies the chance of the multiple points of synchronization seeing different values.



- Sounds simple, right?