

# Circuits II

EE221


Unit 4

Instructor: Kevin D. Donohue

Transfer Function, Complex Frequency,  
Poles and Zeros, and Bode Plots,  
Resonant Circuits
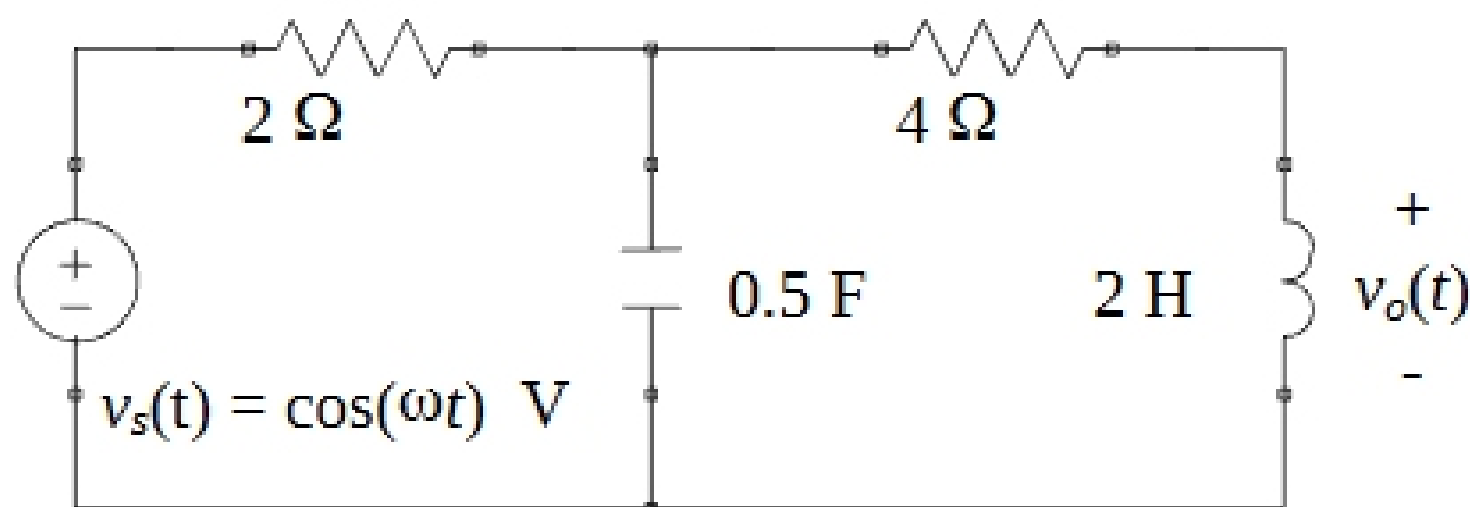
# Node Voltage Example

- Perform phasor analysis to determine  $v_o(t)$ . Since the frequency of the source is not specified, leave impedances in terms of  $j\omega = s$ . Express the phasor of  $v_o(t)$  in terms of a product between a rational polynomial in  $s$  and the phasor of the input. Then substitute  $\omega = 2$  and solve for  $v_o(t)$ .



- Show that

- Show  $v_o(t) = \frac{.33 \cos(2t - 9.46^\circ)}{s^2 + 3s + 3} \underline{\hat{V}_s}$  when  $\omega = 2$   $\square \square \square \angle(\hat{V}_s) + 90^\circ - \tan^{-1} \square \frac{3\omega}{3 - \omega^2} \square \square \square$

# Transfer Functions

- From the last example let:

$$\hat{H}(s) = \frac{s}{s^2 + 3s + 3}$$

- Note that for  $s = j\omega$ , the above function represents the phasor ratio of output to input for any  $\omega$ :

$$\frac{\hat{V}_o(j\omega)}{\hat{V}_s(j\omega)} = \hat{H}(j\omega) = \frac{\sqrt{\omega^2}}{\sqrt{(3 - \omega^2)^2 + 9\omega^2}} \angle \left[ 90^\circ - \tan^{-1} \left| \frac{3\omega}{3 - \omega^2} \right| \right]$$

- Therefore, for any input magnitude, phase, and frequency of  $\omega_i$  the output can be determined by multiplying the input magnitude by  $|\hat{H}(j\omega_i)|$  and adding  $\angle \hat{H}(j\omega_i)$  to the input phase. In this sense,  $\hat{H}(s)$  describes how to *transfer* the input value to the output value.