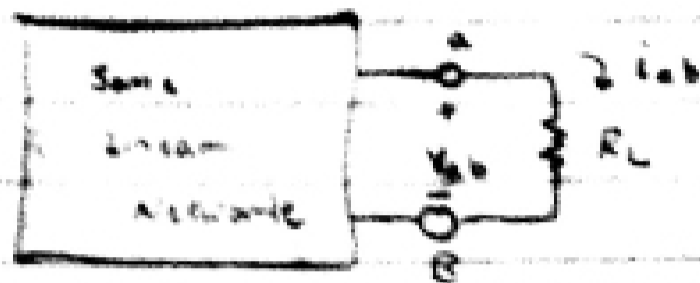


Maximum Power Transfer Theorem

1. How to replace complex circuits
2. Equivalent circuit and equivalent terminal conditions
3. Terminal conditions must be what we care about



Example




Need Two Things to define Terminal conditions



1. $V_{oc} = V_{th}$



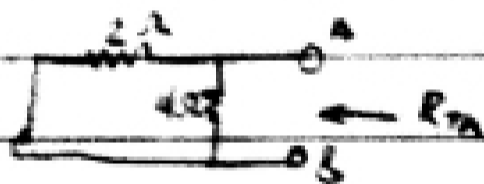2. R_{th} is the equivalent resistance of the Dead network


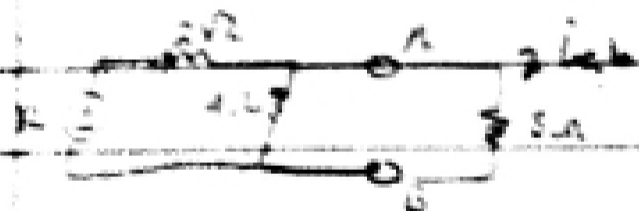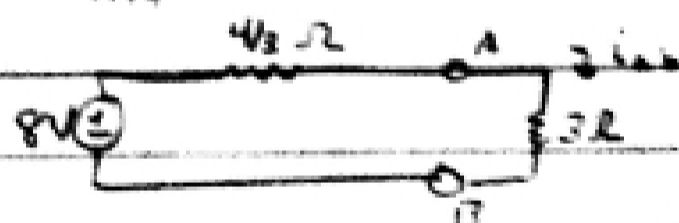
$$R_{th} = \frac{2 \parallel 4}{1} = \frac{8}{6} = \frac{4}{3} \Omega$$



$$i_{AB} = \frac{8V}{\frac{4}{3} + 3} = \frac{24}{13} A$$

$$4 \parallel 3 = \frac{12}{7}$$

$$\frac{12}{7} \text{ series } 2 = \frac{24}{7} \quad \therefore \frac{12}{\frac{24}{7}} = \frac{12 \cdot 7}{24} = \frac{7}{2} A$$


$$i_{AB} = \left(\frac{7}{4+3}\right) \left(\frac{24}{7}\right) = \frac{24}{13} A$$

Next equivalent

1. The short circuit current
2. Same R_{th}



$$I_{sc} = \frac{12V}{2\Omega} = 6A$$

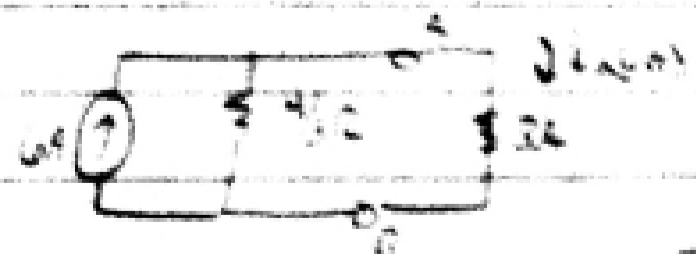

$$i_{AB} = \frac{6}{\frac{4}{3} + 3} (6) = \frac{6}{\frac{13}{3}} = \frac{36}{13} A$$

V_{TH}, R_{TH}, I_{SC}

$V_{TH} = R_{TH} \cdot I_{SC}$


$V_{TH} = 8V$

$R_{TH} = 4/3 \Omega$


$I_{SC} = 6A$

$6A = \frac{8V}{4/3} = 24/4$

Example

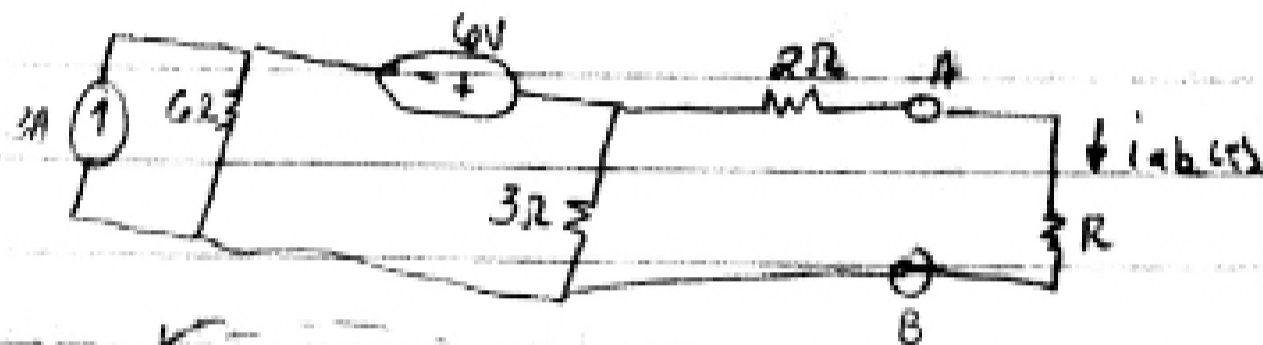

Find i_{AB}

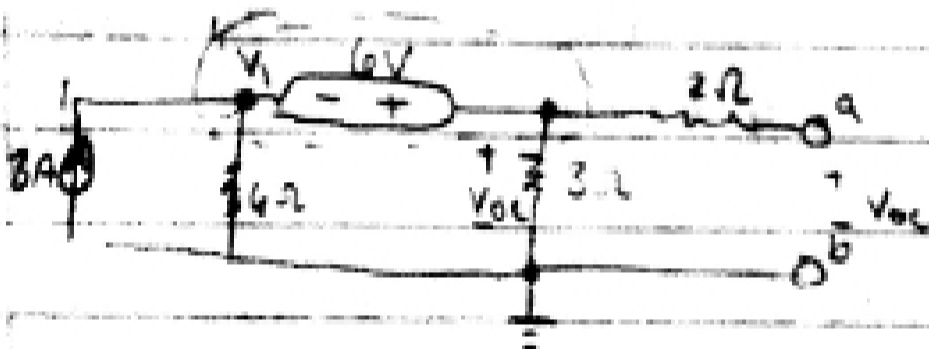

SN: $-3 \cdot \frac{V_1}{6} + \frac{V_{OC}}{3} = 0$


$V_1 = V_{OC} - 6$

$-3 + \frac{V_{OC} - 6}{6} + \frac{V_{OC}}{3} = 0$

$-18 + V_{OC} - 6 + 2V_{OC} = 0$

$3V_{OC} = 24$

$V_{OC} = 8V$

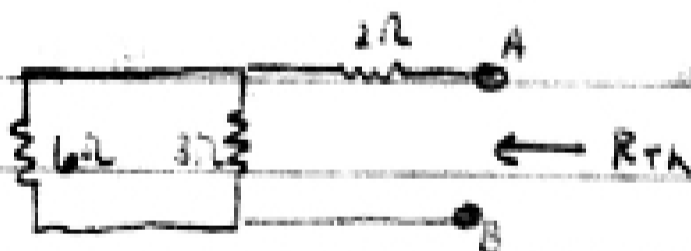

$6 \parallel 3 = 2\Omega$

$2 + 2 = 4\Omega$

$R_{TH} = 4\Omega$



$I_{SC} = \frac{8V}{4\Omega} = 2A$

Another:



SN: $-3 + \frac{V_1}{6} + \frac{V_2}{3} + \frac{V_2}{2} = 0$

$V_1 = V_2 - 6$


$-3 + \frac{V_2 - 6}{6} + \frac{V_2}{3} + \frac{V_2}{2} = 0$

$-18 + V_2 - 6 + 2V_2 + 3V_2 = 0$


$6V_2 = 24$

$V_2 = 4V$

$\therefore I_{SC} = \frac{4V}{2} = 2A$

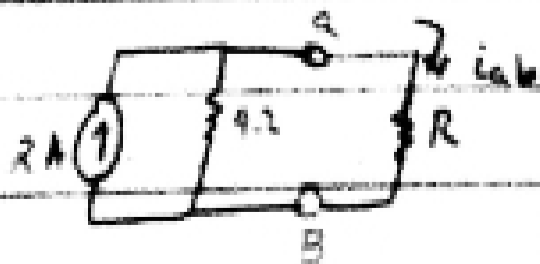

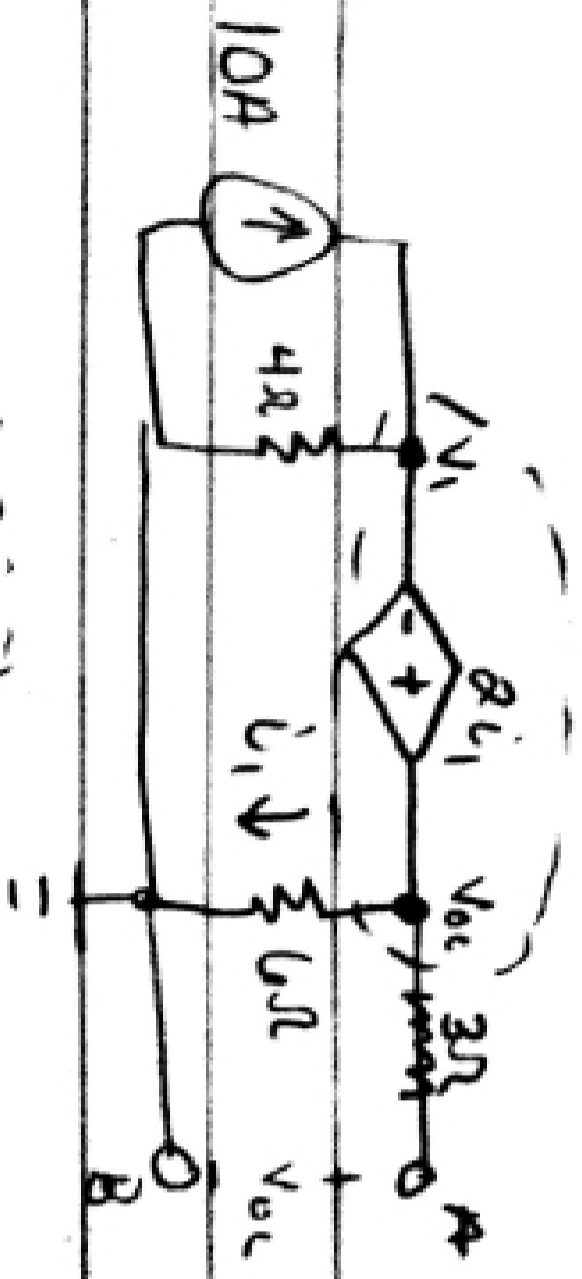$i_{AB} = \frac{4V}{4\Omega + R} = \frac{4}{4+R}$



$$-10 + \frac{V_1}{4} + \frac{V_{oc}}{6} = 0$$


$$V_1 = V_{oc} - 2i_1$$

$$-10 + \frac{V_{oc}}{6} + \frac{V_{oc}}{6} = 0$$

$$i_1 = \frac{V_{oc}}{6\Omega}$$

$$2V_{oc} = 60$$

$$V_{oc} = 30V$$

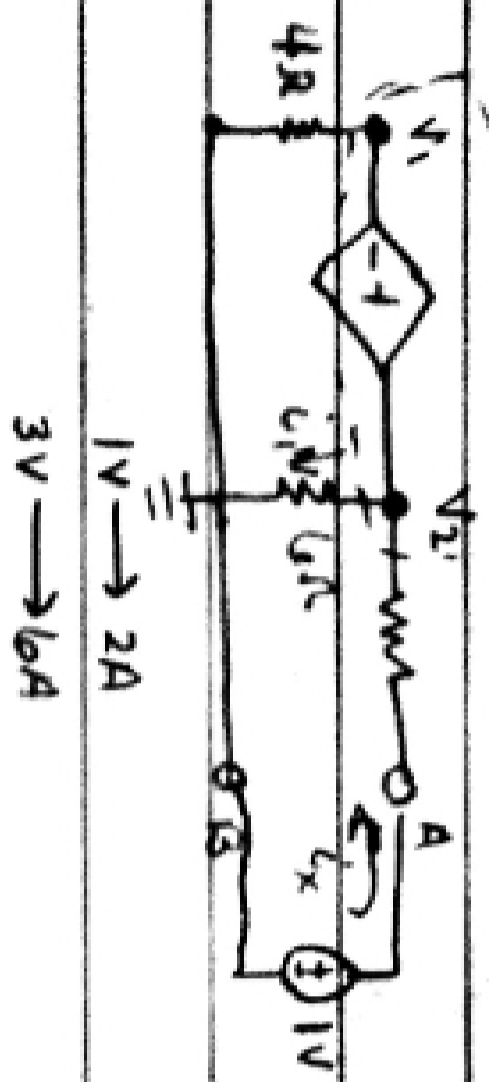

$$SN = \frac{V_1}{4} + \frac{V_2}{6} + \frac{V_2 - 1}{3} = 0$$

$$V_1 = V_2 - 2i_1 = \frac{2}{3}V_2$$

$$i_1 = \frac{V_2}{6}$$

$$\frac{1}{6}V_2 + \frac{1}{6}V_2 + \frac{V_2 - 1}{3} = 0$$

$$V_2 + V_2 + 2V_2 - 2 = 0$$

$$V_2 = \frac{1}{2}$$

$$i_c = \frac{1V - 0.5V}{3} = \frac{0.5}{3} = \frac{1}{6}A$$

$$R_{in} = \frac{1V}{\frac{1}{6}A} = 6\Omega$$

HW. 5.32, 5.34