

Lecture 15 - Digital Circuits: CMOS - Outline

- **Announcements**

 - One supplemental reading on Stellar
Exam 2 - Thursday night, Nov. 5, 7:30-9:30

- **Review - Inverter performance metrics**

 - **Transfer characteristic:** logic levels and noise margins

 - **Power:** $P_{ave, static} + P_{ave, dynamic} (= I_{ON}V_{DD}/2 + f C_L V_{DD}^2)$

 - **Switching speed:** charge thru pull-up, discharge thru pull-down

 - If can model load as linear **C:** $dv_{OUT}/dt = i_{CH}(v_{OUT})/C_L; = i_{DCH}(v_{OUT})/C_L$

 - If can say i_{CH}, i_{DCH} constant: $\tau_{HI-LO} = C_L(V_{HI}-V_{LO})/I_{CH}; \tau_{HI-LO} = C_L(V_{HI}-V_{LO})/I_{DCH}$

 - **Fan-out, fan-in**

(often only 10 to 90% swings)

 - **Manufacturability**

- **CMOS**

 - **Transfer characteristic**

 - **Gate delay expressions**

 - **Power and speed-power product**

- **Velocity Saturation**

 - **General comments**

 - **Impact on MOSFET and Inverter Characteristics**



Transfer characteristic

Node equation: $i_{PD} = i_{PU}$

$$i_{PD} = \begin{cases} 0 & \text{for } V_{IN} < V_{T,PD} \\ K_{PD}(V_{IN} - V_{T,PD})^2/2 & \text{for } V_{IN} - V_{T,PD} < V_{OUT} \\ K_{PD}(V_{IN} - V_{T,PD} - V_{OUT})^2/2 & \text{for } V_{IN} - V_{T,PD} > V_{OUT} \end{cases}$$

i_{PU} : Depends on the device used

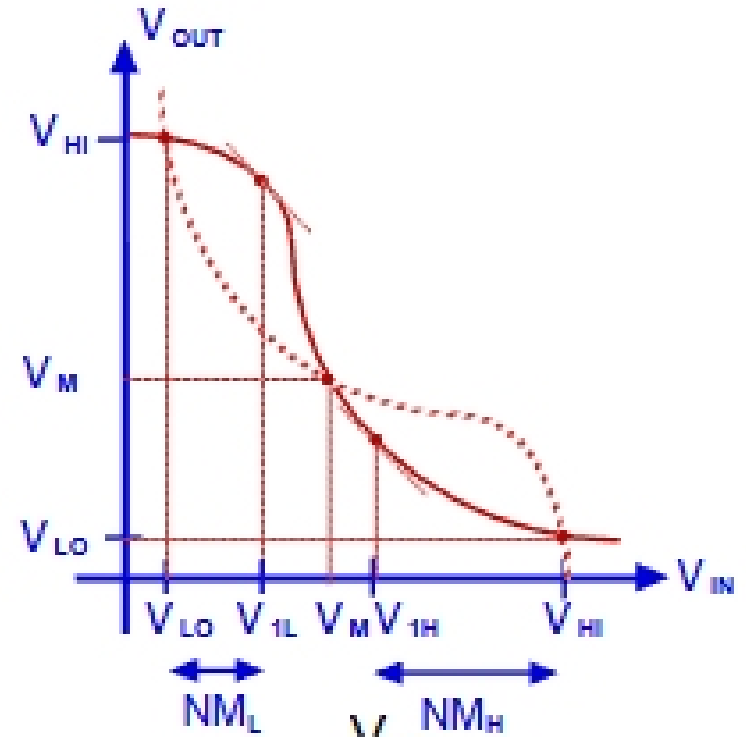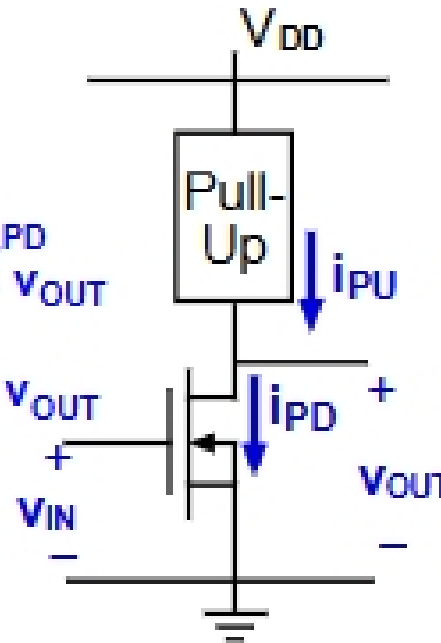Gives us: V_{HI} and V_{LO}
 NM_L and NM_H




Switching transients

General approach:

The load, C_L , is a non-linear charge store, but for MOSFETs it is fairly linear and it is useful to think linear:


$$dv_{out}/dt \approx i_{CL}/C_L$$

Bigger current
 → faster v_{OUT} change

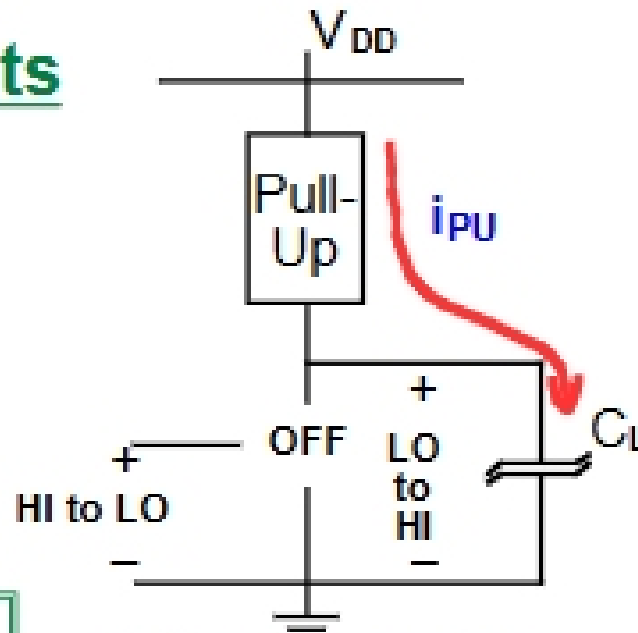

Charging cycle:

$$i_{charge} = i_{PU}$$

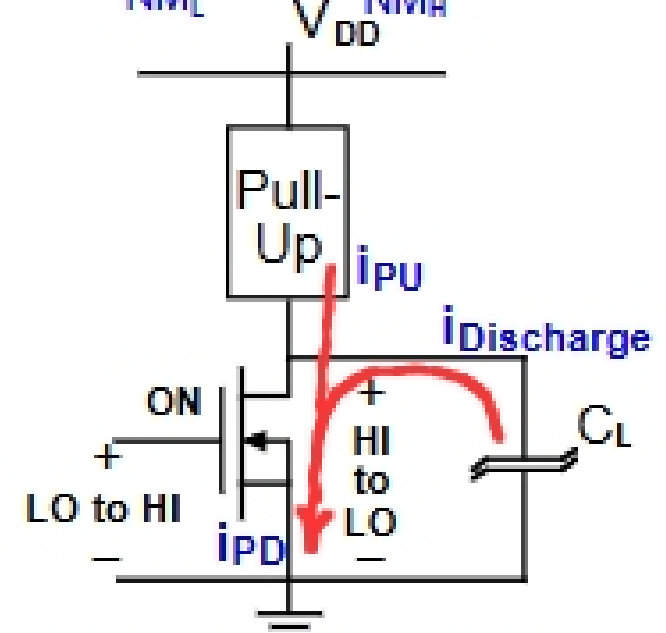


Discharging cycle:



$$i_{Discharge} = i_{PD} - i_{PU}$$

**MOS
inverters:
5 pull-up
choices**


**Generic
inverter**

 


**Resistor
pull-up**

 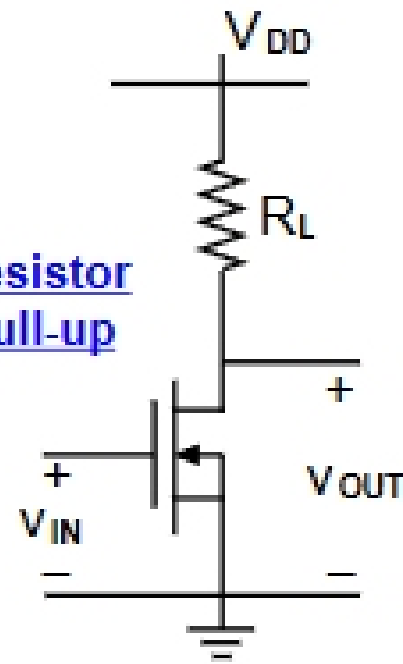

 
**n-channel, e-mode pull-up
 V_{DD} on gate**



V_{GG} on gate

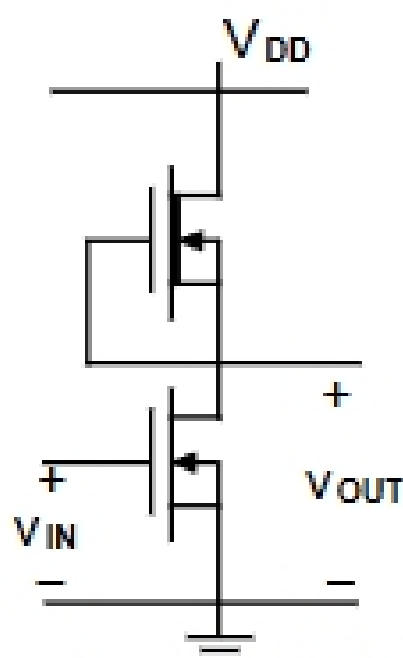

**n-channel, d-mode
pull-up (NMOS)**

 

**Active p-channel
pull-up (CMOS)****

* Known as PMOS when made with p-channel. ** Notice that CMOS has a larger (~3x) input capacitance.