

5. For the series RL network

a) Let $v_s(t) = V_m \cos(\omega t + \phi)$
 $= \text{Re} \{ \underline{V} e^{j\omega t} \}$
 where $\underline{V} = V_m e^{j\phi}$

b) Then the steady state current has the form:

$$i(t) = I_m \cos(\omega t + \beta)$$

$$= \text{Re} \{ \underline{I} e^{j\omega t} \}$$

where $\underline{I} = I_m e^{j\beta}$

c) The circuit equation was:

$$L \frac{di(t)}{dt} + R i(t) = V_m \cos(\omega t + \phi)$$

d) Substituting for $v(t)$ and $i(t)$ gives:

$$L \frac{d}{dt} \left[\text{Re} \{ \underline{I} e^{j\omega t} \} \right] + R \left[\text{Re} \{ \underline{I} e^{j\omega t} \} \right]$$

$$= \text{Re} \{ \underline{V} e^{j\omega t} \}$$

or

$$\operatorname{Re} \left\{ \frac{d}{dt} [L \underline{I} e^{j\omega t}] \right\} + \operatorname{Re} \left\{ R \underline{I} e^{j\omega t} \right\} = \operatorname{Re} \left\{ \underline{V} e^{j\omega t} \right\}$$

$$\therefore \operatorname{Re} \left\{ j\omega L \underline{I} e^{j\omega t} \right\} + \operatorname{Re} \left\{ R \underline{I} e^{j\omega t} \right\} = \operatorname{Re} \left\{ \underline{V} e^{j\omega t} \right\}$$

$$\therefore \operatorname{Re} \left\{ j\omega L \underline{I} e^{j\omega t} + R \underline{I} e^{j\omega t} \right\} = \operatorname{Re} \left\{ \underline{V} e^{j\omega t} \right\}$$

e) The arguments must be equal

$$\therefore j\omega L \underline{I} e^{j\omega t} + R \underline{I} e^{j\omega t} = \underline{V} e^{j\omega t}$$

or $j\omega L \underline{I} + R \underline{I} = \underline{V}$

$$\boxed{[R + j\omega L] \underline{I} = \underline{V}}$$

$$\therefore \underline{I} = \frac{V}{R + j\omega L}$$

f) We can write

$$R + j\omega L = \sqrt{R^2 + \omega^2 L^2} e^{j\theta}$$

$$\text{where } \theta = \tan^{-1} \frac{\omega L}{R}$$

$$\therefore \underline{I} = \frac{V}{\sqrt{R^2 + \omega^2 L^2} e^{j\theta}}$$

$$= \frac{V}{\sqrt{R^2 + \omega^2 L^2}} e^{-j\theta}$$

$$\therefore I_m e^{j\beta} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} e^{j\phi} e^{-j\theta}$$

$$= \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} e^{j(\phi - \theta)}$$

$$\text{or } I_m \cos(\omega t + \beta) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

$$\text{or } i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

$$\theta = \tan^{-1} \frac{\omega L}{R}$$