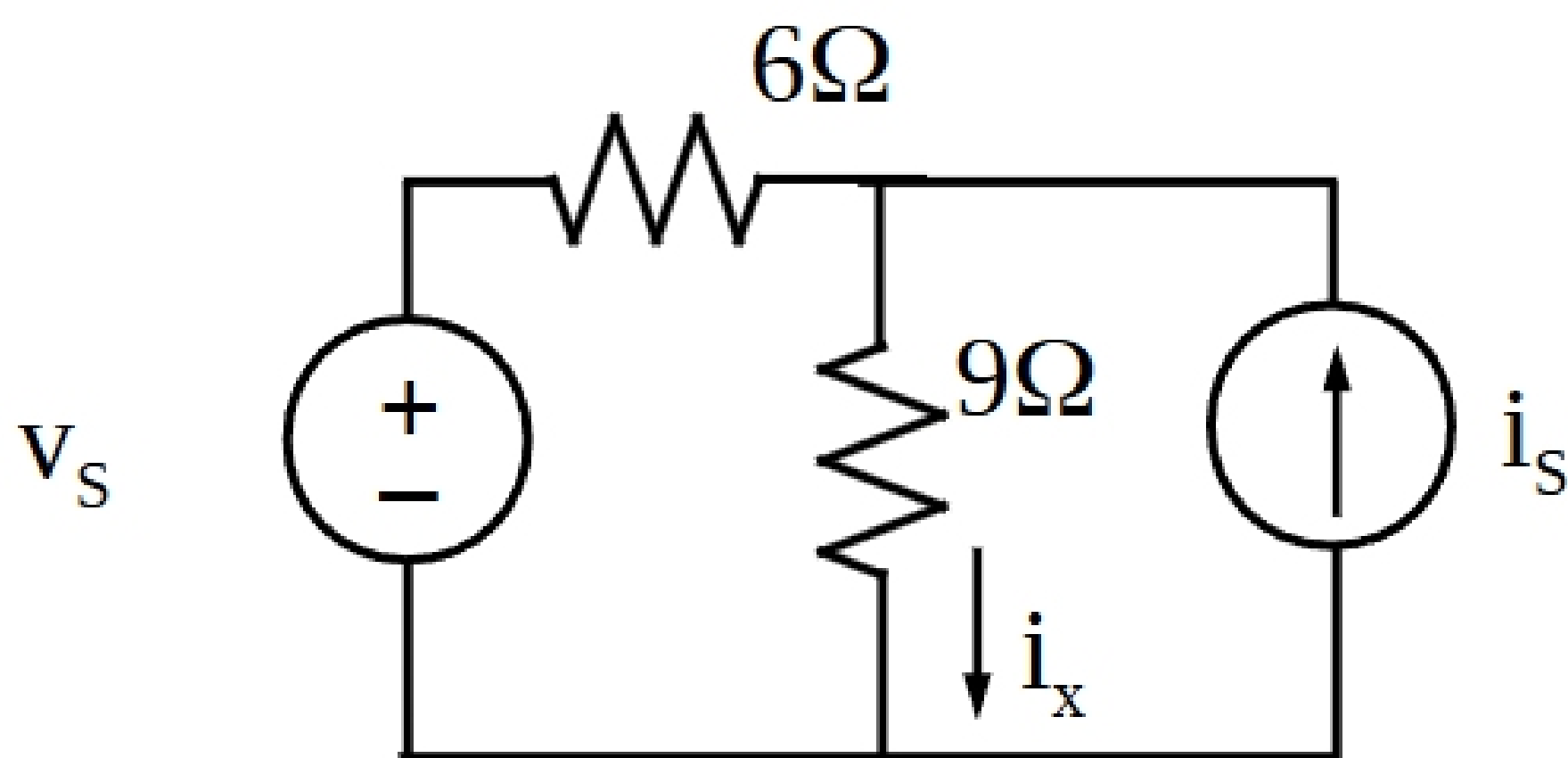


Linearity and Superposition

Consider the circuit:



We can solve for the ‘output’ i_x using mesh analysis.

$$\text{M1:} \quad v_s - 6i_1 - 9(i_1 - i_2) = 0$$

$$v_s - 15i_1 + 9i_2 = 0$$

$$\text{M2:} \quad i_2 = -i_s$$


$$\text{But,} \quad i_x = i_1 - i_2$$

$$\mathbf{i_x = (v_s / 15) + (6i_s / 15)}$$

Solution, $i_x = (v_s / 15) + (6i_s / 15)$ is linearly related to the 'inputs' v_s and i_s .

Solve for output i_x by considering the effect of **each** input separately.


Step 1: Deactivate current source

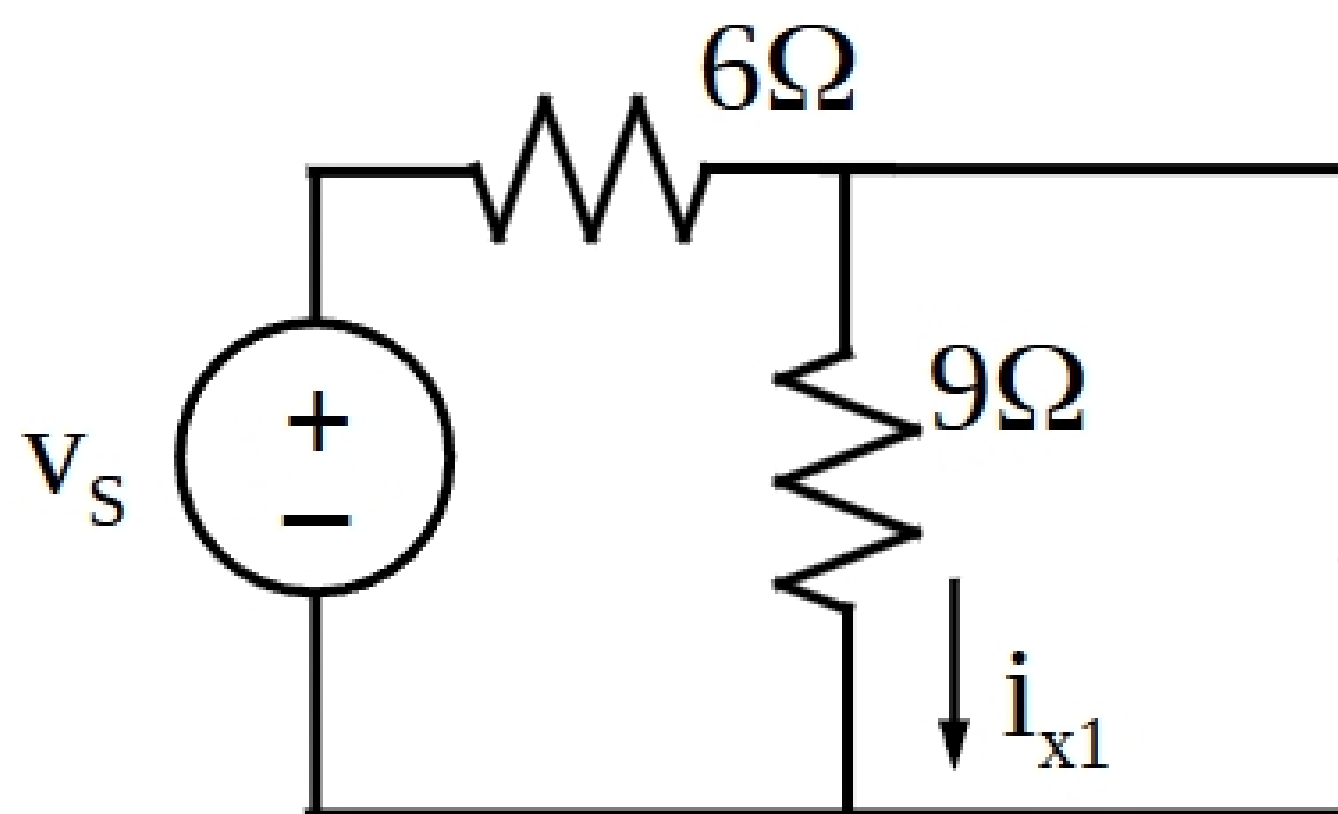

Solve for i_{x1} .

$$i_{x1} = v_s / 15$$

Step 2: Deactivate voltage source

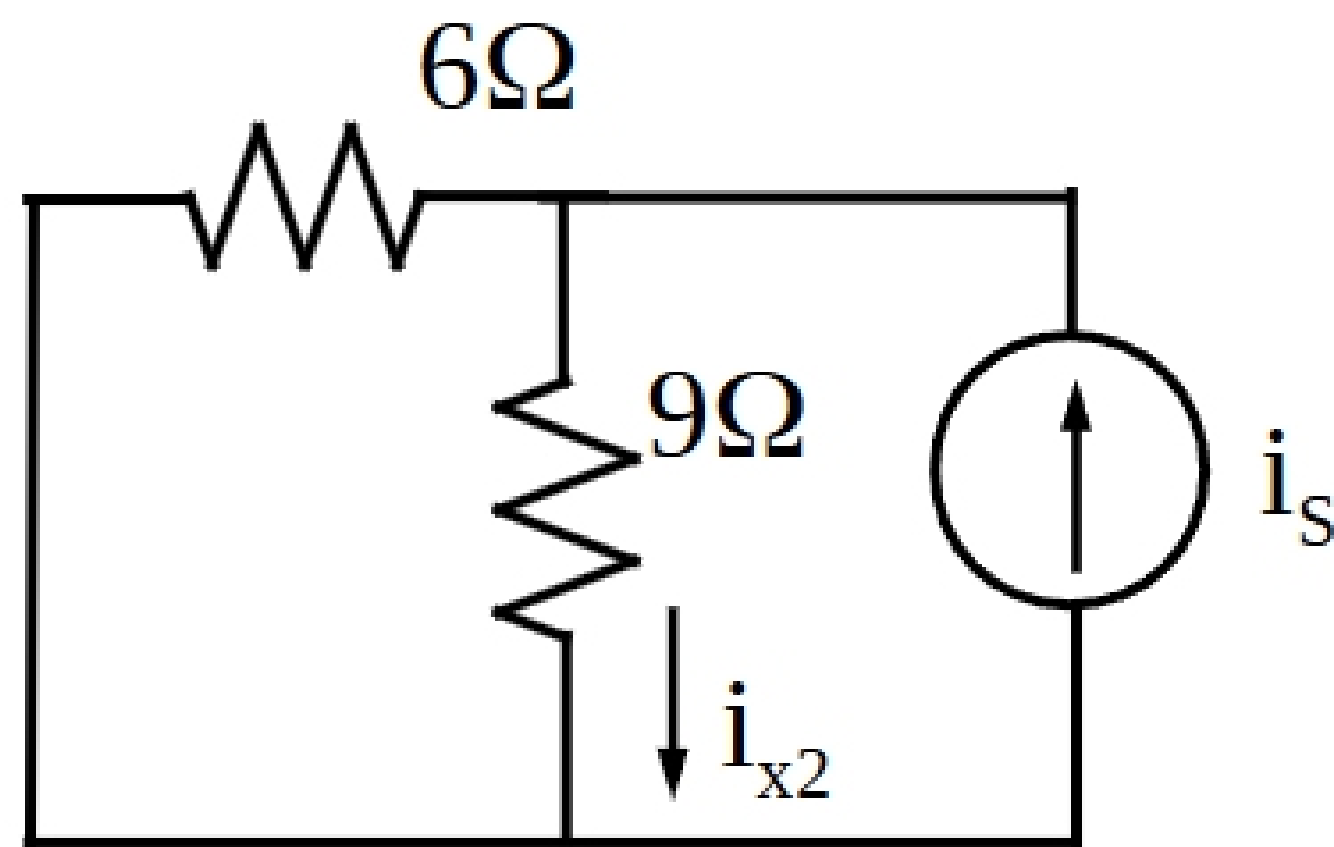

Solve for i_{x2} .

$$i_{x2} = [(1 / 9) / (5 / 18)] i_s = (2/5) i_s$$

Step 3: Add i_{x1} and i_{x2} to obtain solution.

$$i_x = (v_s / 15) + (2/5) i_s$$

$$i_x = (v_s / 15) + (6i_s / 15)$$

This technique is called **superposition**.

Superposition works because internal voltages and currents depend linearly on the independent sources.