

---

## Instantaneous and Average Power

---

Instantaneous power absorbed by a circuit element is

$$p(t) = v(t) i(t) \quad (\text{unit: Watts})$$

The average power absorbed between time  $T_1$  and time  $T_2$  is

$$P_{\text{ave}}[T_1, T_2] = \frac{1}{(T_2 - T_1)} \int_{T_1}^{T_2} p(t) dt$$

$$P_{\text{ave}} = \frac{1}{T} \int_0^T p(t) dt$$

where  $T$  is the period.

Figure 11.3


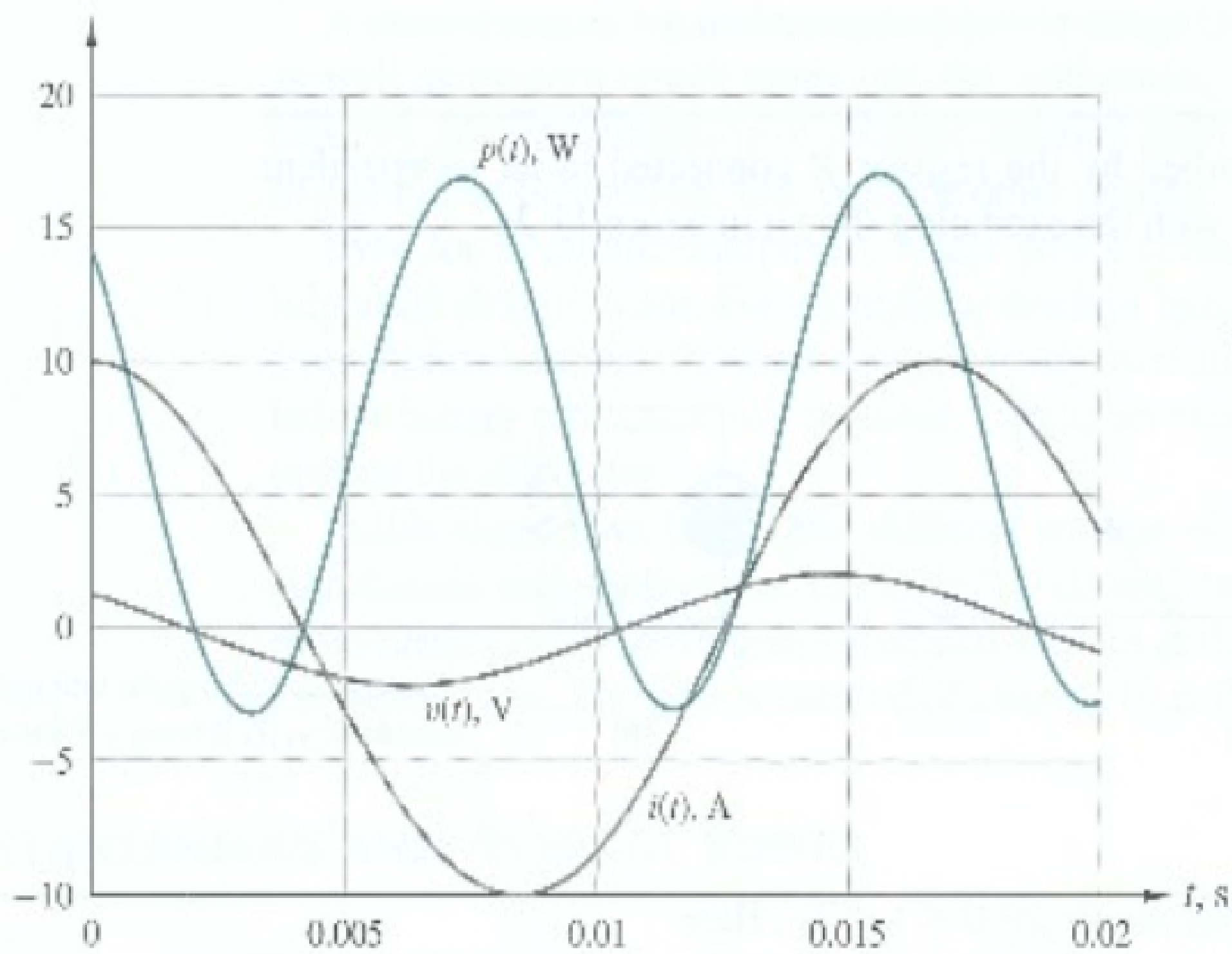


Figure 11.3 Plots of  $i(t) = 10 \cos(377t)$  A,  $v(t) = 2 \cos(377t + 45^\circ)$  V, and  $p(t) = v(t)i(t)$ .

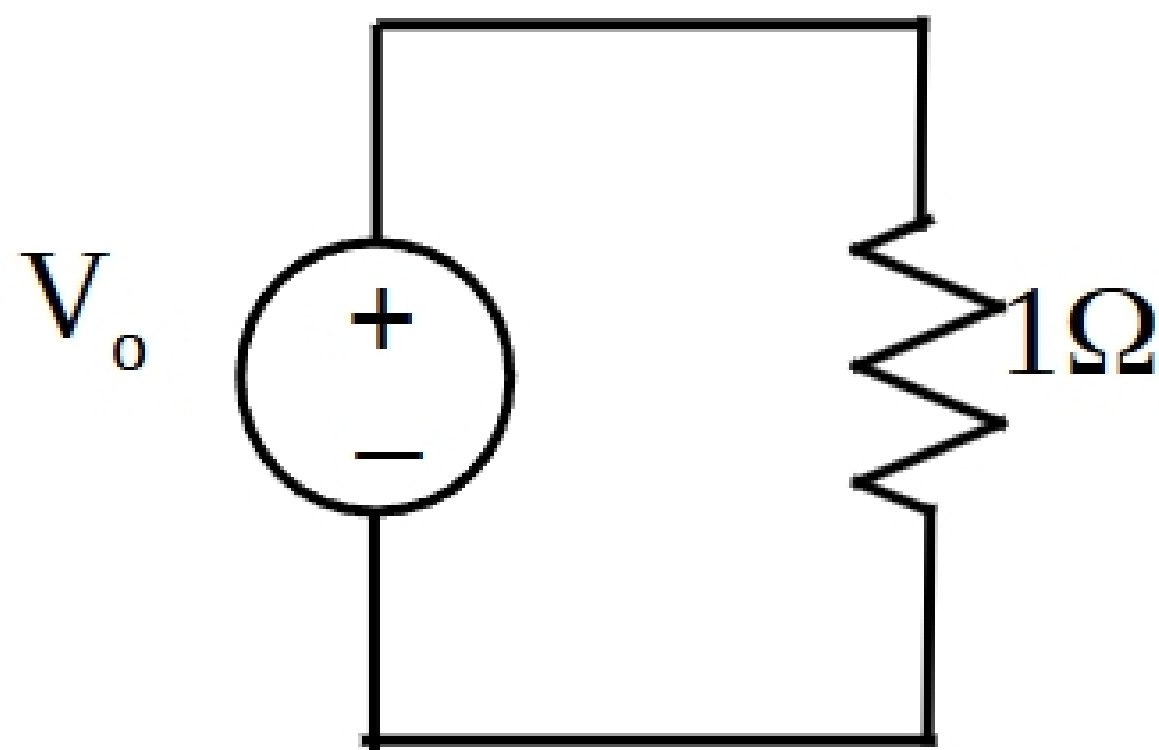**Example:** Show that the average power absorbed by a  $1\Omega$  resistor in the circuit below is  $(V_0)^2$  over any time interval  $[T_1, T_2]$ .



Source voltage-time relationship

