

Introduction:

Students taking this course must be able to perform the

- mesh**
- loop**
- nodal**


methods for DC and AC steady-state circuit analysis on circuits containing

- Resistors, Capacitors, Inductors**
- Op Amps**
- Ideal Transformers**
- Mutual Inductance**
- Independent Voltage and Current Sources**
- Dependent Voltage and Current Sources**

Students must be able to load these circuits into SPICE and determine the currents and voltages throughout the circuit.

Node Voltage Example:

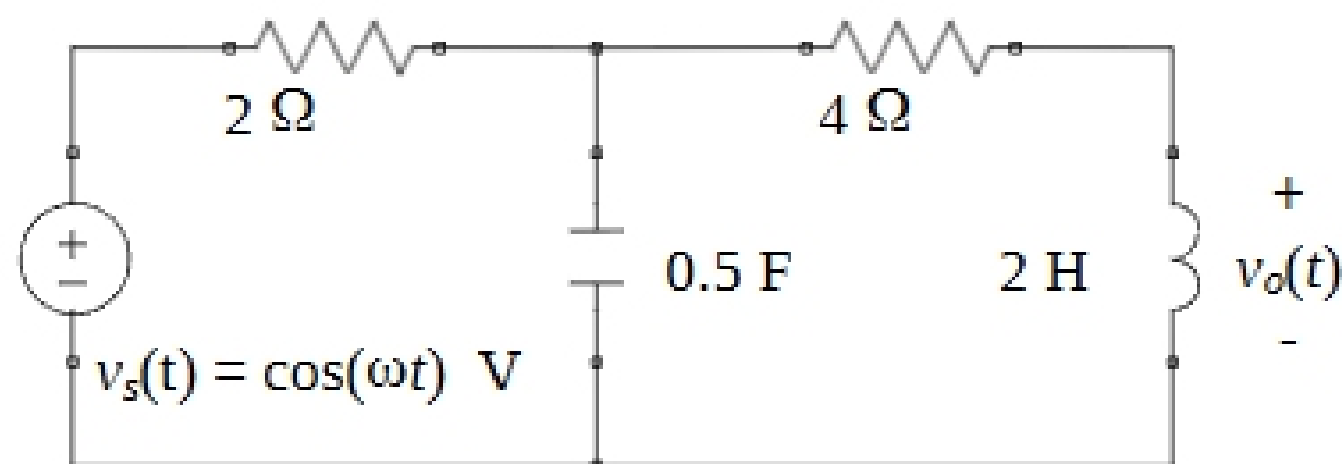Perform phasor analysis to determine \hat{V}_o . Since the frequency of the source is not specified, leave impedances in terms of $j\omega = p$.



Show that $\hat{V}_o = \hat{V}_s \frac{p}{p^2 + 3p + 3} = \hat{V}_s \frac{\sqrt{\omega^2}}{\sqrt{(3 - \omega^2)^2 + 9\omega^2}} \angle \left[90^\circ - \tan^{-1} \left| \frac{3\omega}{3 - \omega^2} \right| \right]$

Show $v_o(t) = .33\cos(2t - 9.46^\circ)$ V, when $\omega = 2$

Mesh Current Example:

Perform phasor analysis to determine \hat{V}_c . Assume $v_s(t) = 5\cos(2\pi 60t)$ v.
Write a SPICE program to also find this value.

