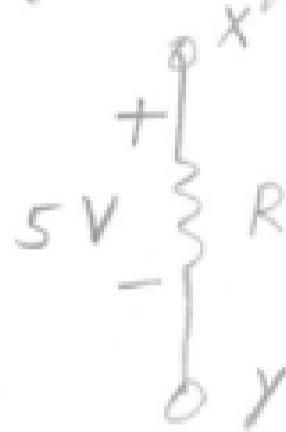



A. Basic nodal analysis

1. Still use KCL
2. But solve for node voltages
3. Voltage - potential between 2 points



- a) need a reference
- b) X wrt Y
- c) or Y wrt X
- d) ⏏


4.

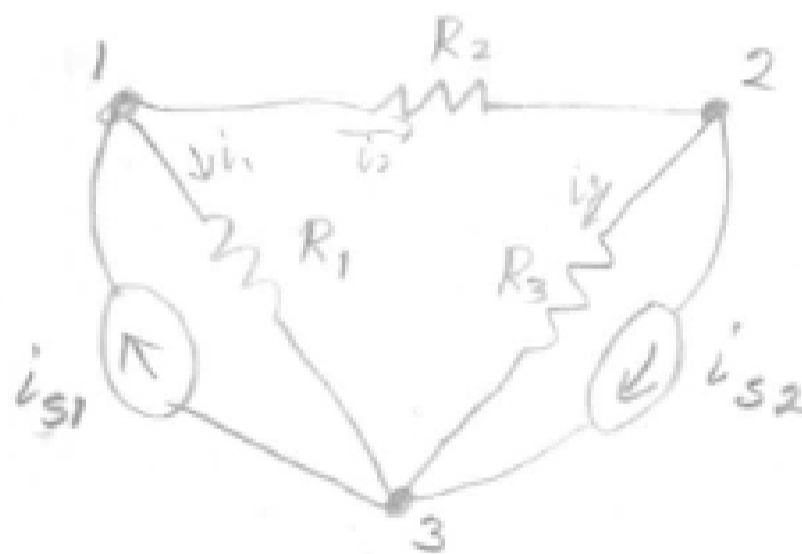

- a) circuit has 3 nodes
- b) Pick a reference (N3)
- c) $\therefore v_3$ wrt $v_3 = 0$
- d) Find v_1 and v_2

Essential node -
a node which
connects three or
more circuit
elements.

Example (Drill 4.16)

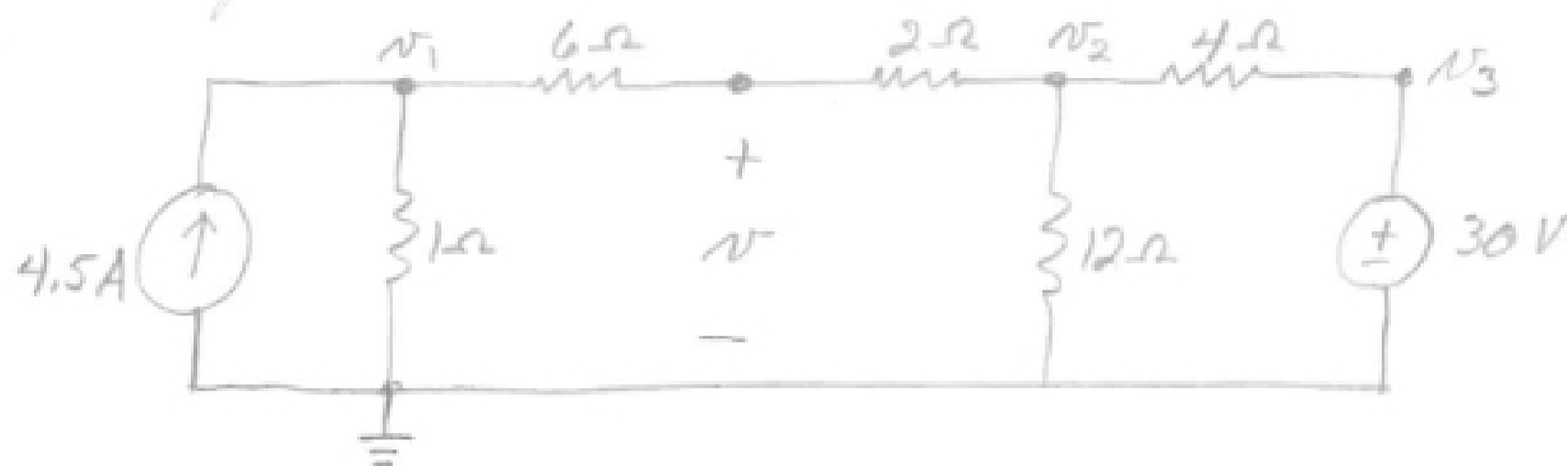

Find v :

$$-4.5 + \frac{v_1}{1} + \frac{v_1 - v}{6} = 0$$

$$\frac{v - v_1}{6} + \frac{v - v_2}{2} = 0$$

$$\frac{v_2 - v}{2} + \frac{v_2}{12} + \frac{v_2 - v_3}{4} = 0$$

$$v_3 = 30$$

$$\begin{bmatrix} 7 & -1 & 0 \\ -1 & 4 & -3 \\ 0 & -6 & 10 \end{bmatrix} \begin{bmatrix} v_1 \\ v \\ v_2 \end{bmatrix} = \begin{bmatrix} 27 \\ 0 \\ 90 \end{bmatrix}$$

$$v = \frac{\begin{vmatrix} 7 & 27 & 0 \\ -1 & 0 & -3 \\ 0 & 90 & 10 \end{vmatrix}}{\begin{vmatrix} 7 & -1 & 0 \\ -1 & 4 & -3 \\ 0 & -6 & 10 \end{vmatrix}} = \frac{(7)(270) - (-1)(270)}{(7)(22) - (-1)(10)} = \frac{2160}{144} = 15 \text{ V}$$

Hint 4.3, 4.7

Make currents entering - and those leaving + to avoid confusion with shortcut procedure (i.e., voltage at node minus voltage away)

e) at node 1:

KCL: or $i_1 + i_2 - i_{s1} = 0$

ohm's law: $i_1 = \frac{\Delta v}{R_1} = \frac{v_1 - 0}{R_1} = \frac{v_1}{R_1}$

$i_2 = \frac{v_1 - v_2}{R_2}$

$\therefore \frac{v_1}{R_1} + \frac{v_1 - v_2}{R_2} - i_{s1} = 0$

f) at node 2:

KCL: $-i_2 + i_3 + i_{s2} = 0$

ohm's law: $-i_2 = \frac{\Delta v}{R_2} = -\frac{v_1 - v_2}{R_2} = \frac{v_2 - v_1}{R_2}$

$i_3 = \frac{\Delta v}{R_3} = \frac{v_2 - 0}{R_3} = \frac{v_2}{R_3}$

$\therefore \frac{v_2 - v_1}{R_2} + \frac{v_2}{R_3} + i_{s2} = 0$

g) Voltage at this node minus the voltage away

h) Rearrange equations

$(\frac{1}{R_1} + \frac{1}{R_2})v_1 + \frac{1}{R_2}v_2 = i_{s1}$

$-\frac{1}{R_2}v_1 + (\frac{1}{R_2} + \frac{1}{R_3})v_2 = -i_{s2}$

could use G or

$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_3} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} i_{s1} \\ -i_{s2} \end{bmatrix}$