

Lecture 19w: Stability

Lecture 19: Stability

Announcements:



- This is our make-up lecture, which replaces tomorrow's (Thursday's) lecture, since I will be traveling on Thursday
- Again, I will be using software local to my computer to record the lecture

Lecture Topics:

- Finish Output Stages
- Stability
- Single-Pole Op Amp in Feedback
- Multi-Pole Op Amp in Feedback
- Phase Margin

Last Time:

Actual Implementation

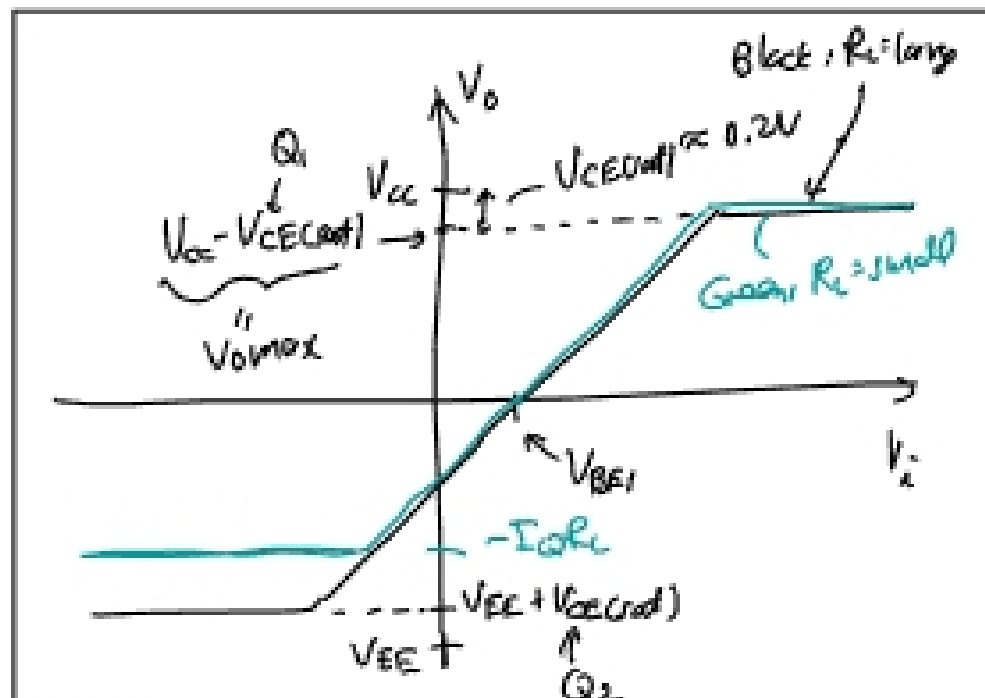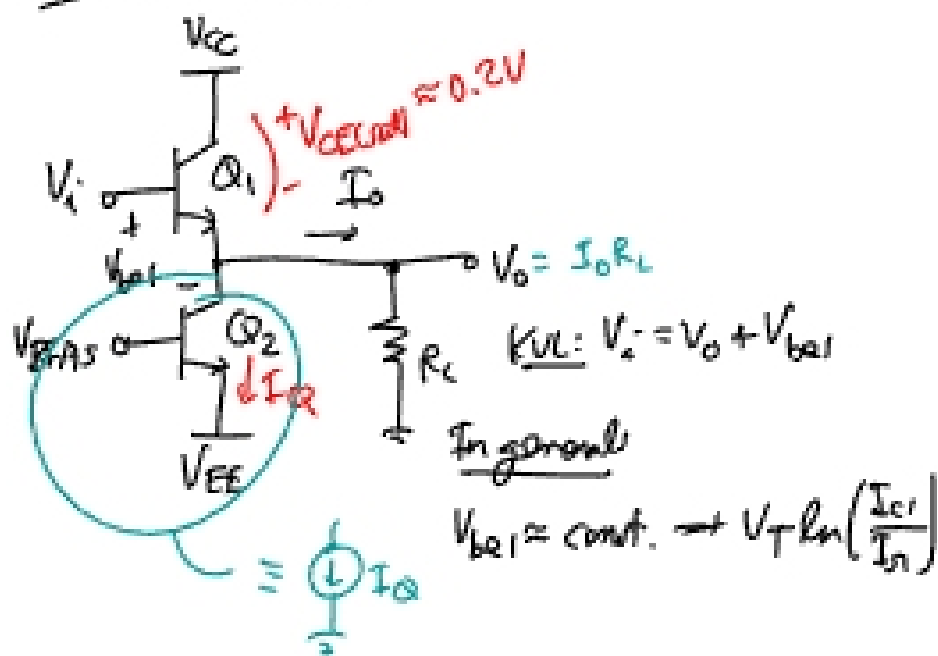

Two Cases:

Case 1: $R_L = \text{large} \rightarrow I_o < I_Q$
 $\Rightarrow I_o$ not doing much to get a large ΔV_o

For $V_i = \text{large}$ and (1): Q_1 must source $I_o + I_Q$ to make $V_o \uparrow$

at some pt., Q_1 will saturate as $V_o \uparrow$

$V_{omax} = V_{CC} - V_{CE(sat)}$

and $V_i = V_{CC} - V_{CE(sat)} + V_{BE1}$

not always possible if input signal is limited by V_{CC} supply rail

For $V_i = \text{large}$ and $(-)$: V_o follows V_i until Q_2 saturates

$$V_{\text{min}} = V_{EE} + V_{CE(\text{sat})}$$

↙ of Q_2

$$V_i = V_o + V_{BE1} = V_{EE} + V_{CE2(\text{sat})} + V_{BE1}$$

Case 2: $R_L = \text{small} \rightarrow$ thus, I_o can be large!

For $V_i = (+)$ and large: Q_1 can source as much current as needed until it saturates (or until it fires)

For $V_i = (-)$ and large: $V_o = I_o R_L \rightarrow \text{min. } V_o = -I_o R_L$

$\rightarrow Q_1$ cut off ($I_{E1} = 0$)

$\rightarrow V_o$ clamps @ $-I_o R_L$

\rightarrow further decrease in $V_i \rightarrow$ no Δ in V_o !

\rightarrow solve raise I_Q to set to $V_{EE} + V_{CE(\text{sat})}$, if desired

Problem: Need large $I_Q \rightarrow$ DC current

always free, whether or not there is a V_i

\rightarrow always have DC power diss!


often, too much!

$$P_Q = (V_{CC} - V_{EE}) I_Q$$

quiescent DC \rightarrow large DC power consumption! **Bad!!**

Solution: **Class B Output Stage**

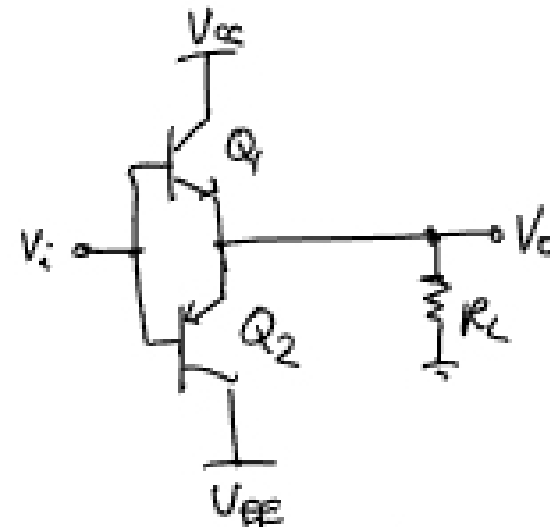\leftarrow DC
 \rightarrow can attain zero quiescent power




Operation:

zero power consumption

$|V_i| < V_{BE(\text{on})} \rightarrow I_{E1} = I_{E2} = 0 \rightarrow V_o = 0V$


$V_{CC} > V_i > V_{BE(\text{on})} \rightarrow V_o \approx V_i - V_{BE(\text{on})}$ (Q_1 on; Q_2 off)

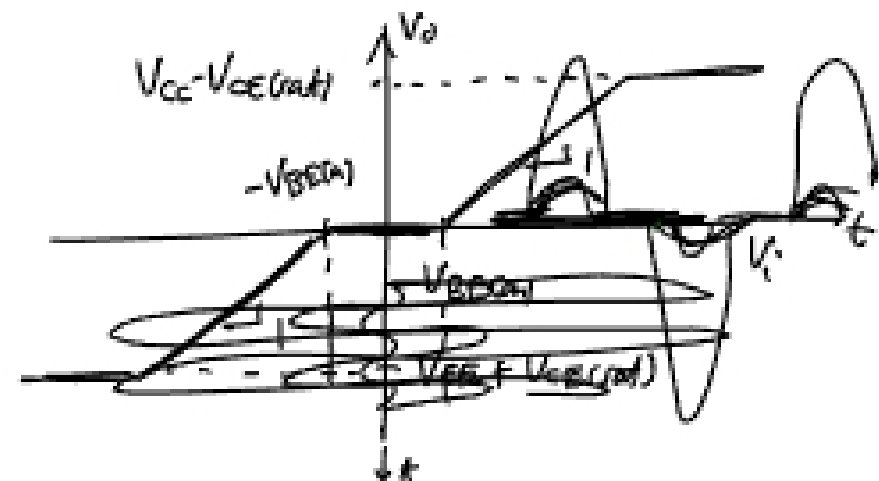$-V_{BE(\text{on})} > V_i > V_{EE} \rightarrow V_o \approx V_i + V_{BE(\text{on})}$




To solve the dead zone (while maintaining low DC bias currents)

Use Class AB

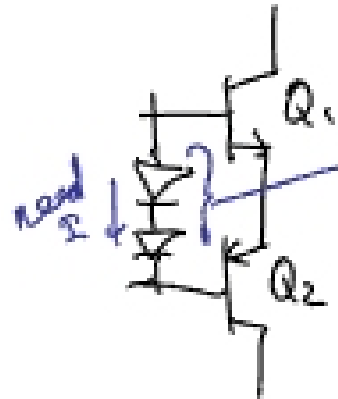

insure enough voltage to keep Q1 + Q2 on
∴ no dead zone
⇒ see your HWs!

Stability & Compensation in Op Amps

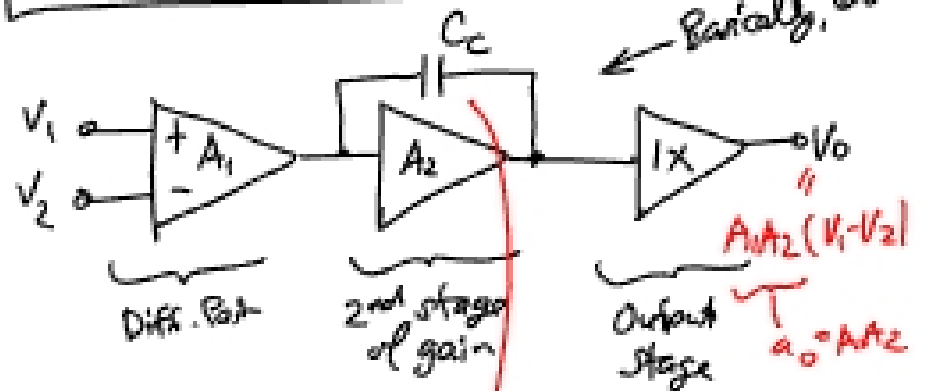

Used Cc to set BW:



Stability & Compensation in Op Amps

In general, op amp are used in neg FB loops.


res. FB, if not really neg. FB, can cause instability

Reasons:

- ① Feedback sets the biasing → no large coupling or bypass caps needed.
- ② FB increases BW.
- ③ FB increases linearity of input stage. (eg. emitter degeneration is a type of FB)
- ④ Gain determined by external FB components → more accurate than op amp gain.
- ⑤ FB sets Ri and Ro.
- ⑥ FB can improve temperature stability.

⇒ Problem: any FB loop can become unstable under certain conditions → ∴ must compensate to suppress instability!

Ex. Non-inverting Amplifier

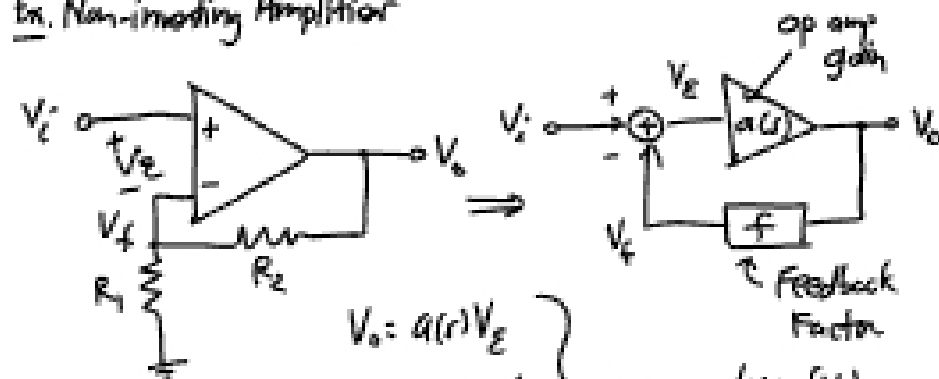

$$\left. \begin{aligned} V_o &= a(s)V_E \\ V_E &= V_i - V_f \\ V_f &= fV_o \end{aligned} \right\} V_o = a(s)(V_i - fV_o)$$

$$A(s) = \frac{V_o}{V_i}(s) = \frac{a(s)}{1 + a(s)f} = \frac{a(s)}{1 + T(s)}$$