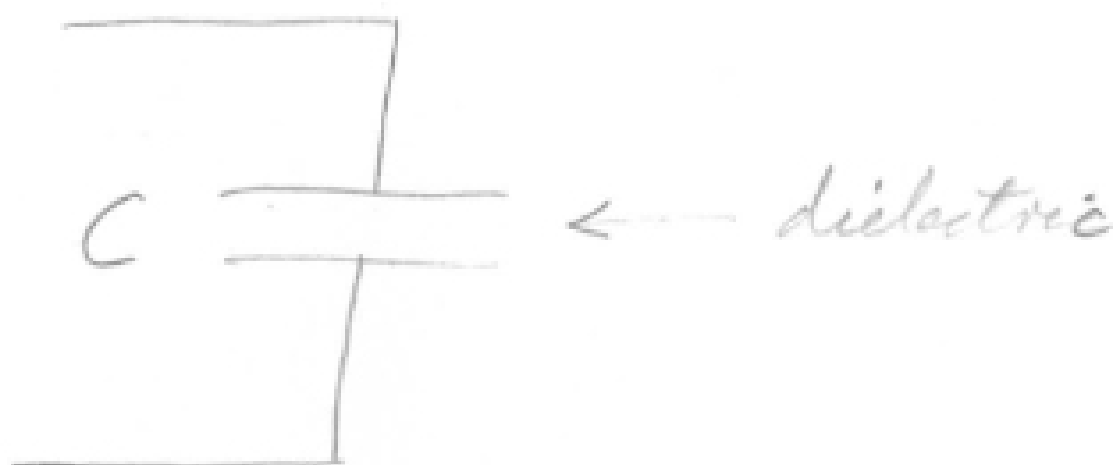


A. Capacitor

(6~1)

1. Two conductors separated by an insulator



2. Terminal characteristics

a) $+\Delta q$ from bottom to top

b) requires Δv

c) specifically:

$$\Delta q = C \Delta v$$

(linear relation)

or $q = C v$

C is capacitance in Farads

d) requires time Δt

$$\therefore \frac{\Delta q}{\Delta t} = C \frac{\Delta v}{\Delta t}$$

$$\lim_{\Delta t \rightarrow 0} \frac{\Delta q}{\Delta t} = \lim_{\Delta t \rightarrow 0} C \frac{\Delta v}{\Delta t}$$

$$\frac{dq}{dt} = C \frac{dv}{dt}$$

or $i = C \frac{dv}{dt}$

$$C = \frac{q}{v}$$

$$C = \frac{\epsilon A}{d}$$

$$\epsilon = \epsilon_r \epsilon_0$$

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$$

Permittivity


3. Additional properties

a) since $i = C \frac{dv}{dt}$

b) $i = 0$ for constant v

c) \therefore open circuit to d.c. (for steady state)

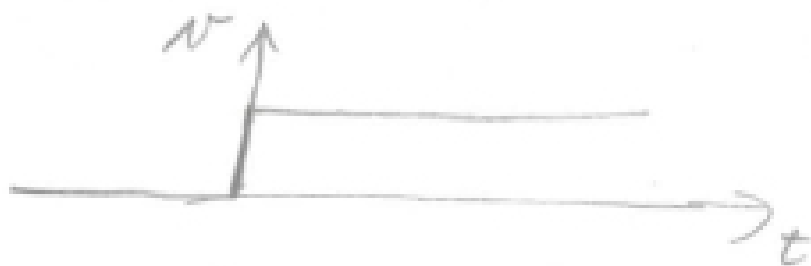d) Also, the voltage across a capacitor cannot change instantaneously



$$\frac{dv}{dt} = \infty$$

 $\therefore i = C \frac{dv}{dt} = \infty$ would require an ∞ current

c) voltage in terms of the current

$$dv = \frac{1}{C} i dt$$

$$\int_{v(t_0)}^{v(t)} dv = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau$$

$$\therefore \boxed{v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)}$$

initial voltage

f) Energy relation

$$\begin{aligned}
 W(t) &= \int_{-\infty}^t v i \, dx \\
 &= \int_{-\infty}^t v \left(C \frac{dv}{dx} \right) dx \\
 &= C \int_{v(-\infty)}^{v(t)} v \, dv \\
 &= \frac{1}{2} C v^2 \Big|_{v(-\infty)}^{v(t)}
 \end{aligned}$$

$$\boxed{W(t) = \frac{1}{2} C v^2(t)}$$

stored in an electric field

∴ $W \geq 0$ (capacitor is a passive element)

RADMASTER Made in U.S.A.