

• Announcements:

- Your project cannot use ideal current sources; all you have is V<sub>DD</sub> and V<sub>SS</sub>
- You need to design your own current sources if you need them
- You should also try to minimize area, as usual (e.g., a design using an enormous resistor will not be as good as one using a much smaller one, or no resistor at all)




• Today:

• CMOS Op Amp Compensation

Last Time -

Choosing C<sub>c</sub> (assume no RHP zeros & |p<sub>2</sub>| >> |p<sub>1</sub>|)  
 ⇒ assume  $\frac{1}{RC_c} \ll$  (surrounding resistors) @ high freq.

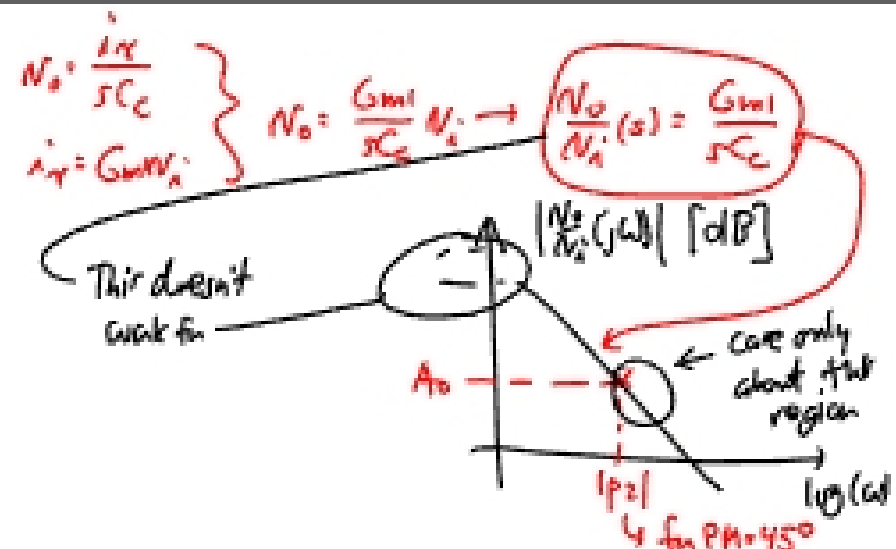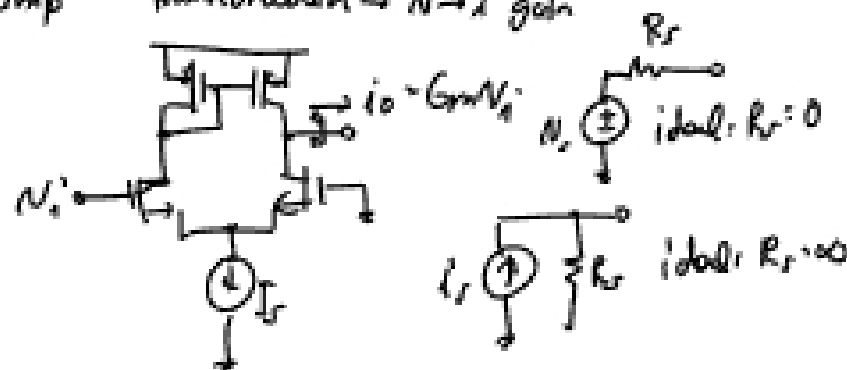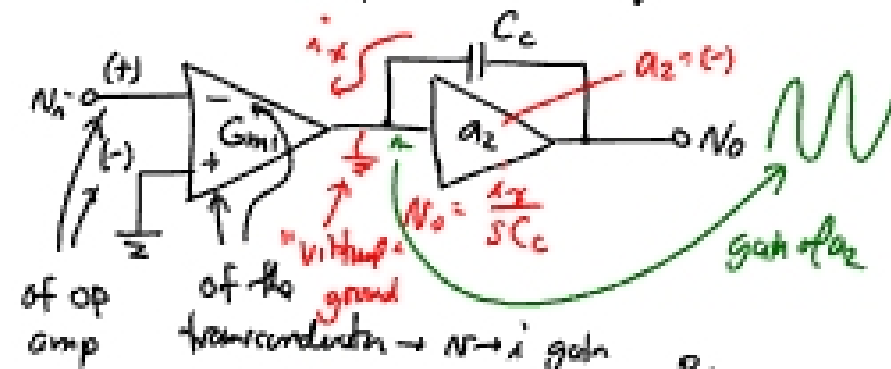① Case: Two-stage Amplifier, Miller Compensation




$\left| \frac{N_2}{N_1}(j\omega) \right| = \frac{G_{m1}}{\omega C_c} \Rightarrow$  this should equal  $A_0$  @ the freq.  $\omega$  corresponding to the target phase margin

For PM = 45°:  
 $\omega_{u1g} = \omega @ |T(j\omega)| = 1$   
 "u1g" = "unity loop gain"  
 For PM = 45° →  $\omega_{u1g} = \omega_2$  ← freq. of the 2nd pole in the  $a(s)$  transfer function

$\left| \frac{N_2}{N_1}(j\omega_2) \right| = A_0 = \frac{G_{m1}}{\omega_2 C_c}$   
 $C_c = \frac{G_{m1}}{\omega_2 A_0}$  ← For PM = 45° (provided high-order poles are far away, i.e., |p<sub>2</sub>| >> |p<sub>1</sub>|)

For PM = 60°:  
 $\omega_{u1g} = \frac{\omega_2}{1.73} \rightarrow \left| \frac{N_2}{N_1}(j\frac{\omega_2}{1.73}) \right| = A_0 = \frac{G_{m1}}{(\frac{\omega_2}{1.73}) C_c}$   
 $C_c = \frac{1.73 G_{m1}}{\omega_2 A_0}$  ← For PM = 60°

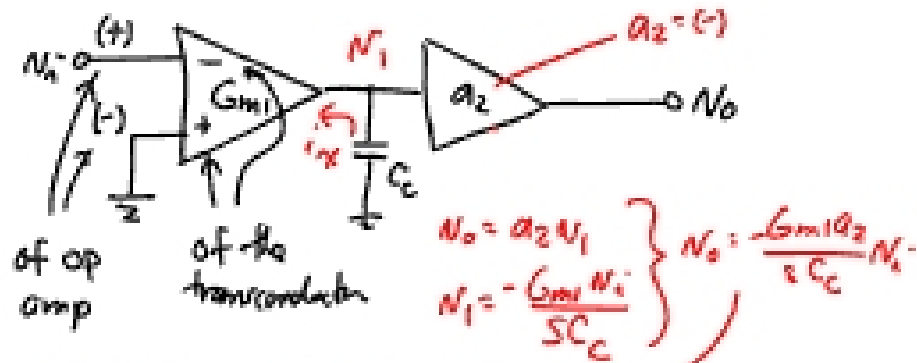Case 1: Two-Stage Amplifier, Shunt  $C_c$  Compensation



$\therefore \frac{N_o}{N_i}(s) = -\frac{G_{m1} a_2}{s C_c}$  } Closed loop gain  $A_{cl}$  must again intersect the curve @ the right w/ly for a given PM


For PM = 45°:

$\left| \frac{N_o}{N_i}(j\omega_{45}) \right| = A_0 \cdot \frac{G_{m1} a_2}{\omega_{45} C_c}$   
 For PM = 45°:  $\omega_{45} = \omega_{45} \rightarrow C_c = \frac{G_{m1} a_2}{\omega_{45} A_0}$  ← For PM = 45°

For PM = 60°:



$C_c = \frac{1.73 G_{m1} a_2}{\omega_{45} A_0}$

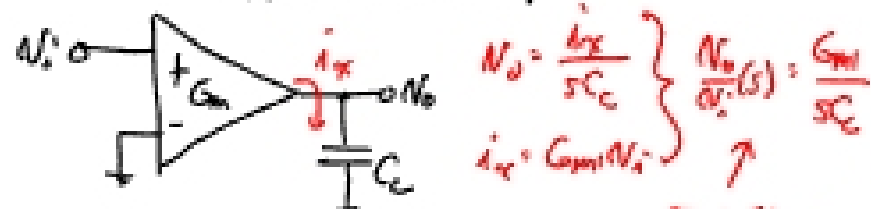Case 2: Single-Stage Amplifier, Shunt  $C_c$  Compensation  
e.g., telescopic op amp



$C_c = \frac{G_{m1}}{\omega_{45} A_0}$  ← PM = 45°       $C_c = \frac{1.73 G_{m1}}{\omega_{45} A_0}$  ← PM = 60°

CMOS 2-Stage Op Amp Compensation

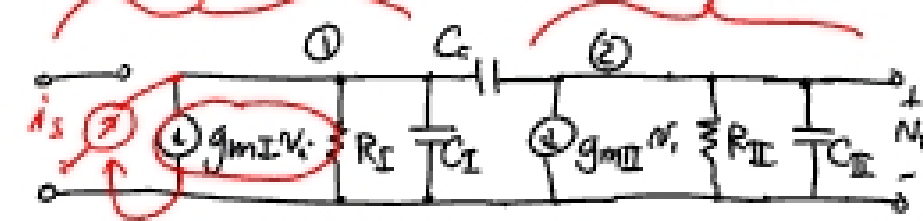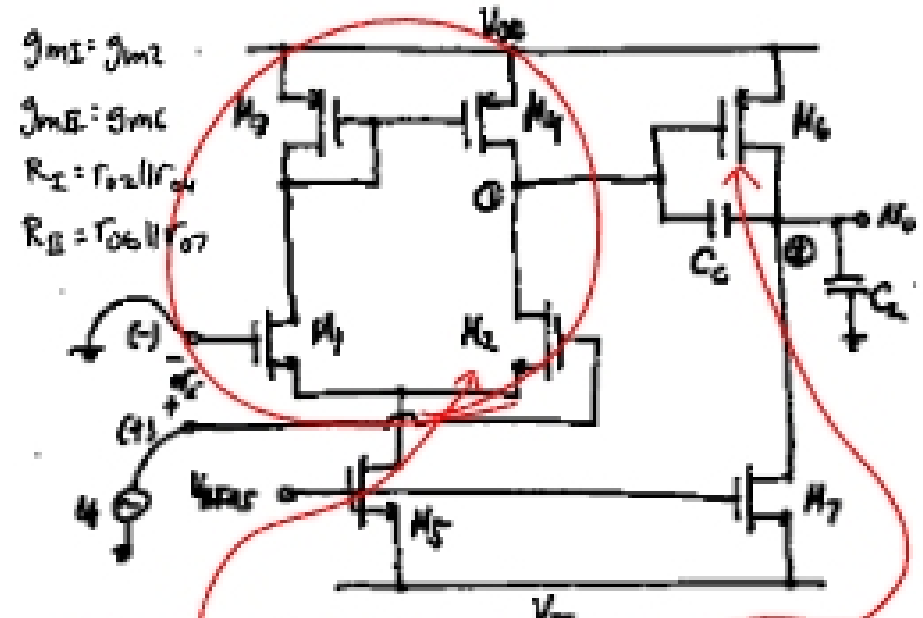

KCL ①:  $i_s = \frac{N_i}{R_I} + s C_c N_i + (N_i \cdot N_o) s C_c$   
 KCL ②:  $g_{mII} N_i + \frac{N_o}{R_{II}} + s C_{II} N_o + (N_o - N_i) s C_c = 0$

$\frac{N_o}{i_s} = \frac{(g_{mII} - s C_c) R_I R_{II}}{1 + s [(C_c + C_{II}) R_{II} + (C_c + C_{II}) R_I + g_{mII} R_I R_{II} C_c] + s^2 R_I R_{II} (C_c C_{II} + C_c C_c + C_c C_{II})}$   
 $= \frac{N(s)}{D(s)}$

This xfm fn has 2 poles & a zero!

The zero:  $N(s) = 0 \rightarrow z = \frac{g_{m2}}{C_c} \leftarrow (+) \text{ and real}$   
 $s = s$

The poles:

$$D(s) = \left(1 - \frac{s}{p_1}\right)\left(1 - \frac{s}{p_2}\right) = 1 - s\left(\frac{1}{p_1} + \frac{1}{p_2}\right) + \frac{s^2}{p_1 p_2}$$

$$[p_2 \gg p_1] \approx 1 - \frac{s}{p_1} + \frac{s^2}{p_1 p_2}$$

$\uparrow$  i.e.,  $p_1$  is a dominant pole

Thus:

$$p_1 = \frac{1}{(C_D + C_c)R_D + (C_I + C_c)R_I + g_{m1}R_I R_D C_c}$$


As  $C_c \uparrow \rightarrow p_1 \downarrow \rightarrow \omega_{-3dB} = \frac{1}{g_{m1}R_I R_D C_c}$

For the 2nd pole:

$$p_1 p_2 = \frac{1}{R_I R_D (C_I C_D + C_c C_I + C_c C_D)}$$

$$p_2 \approx - \frac{g_{m2} C_c}{C_c C_D + C_c C_I + C_c C_D}$$

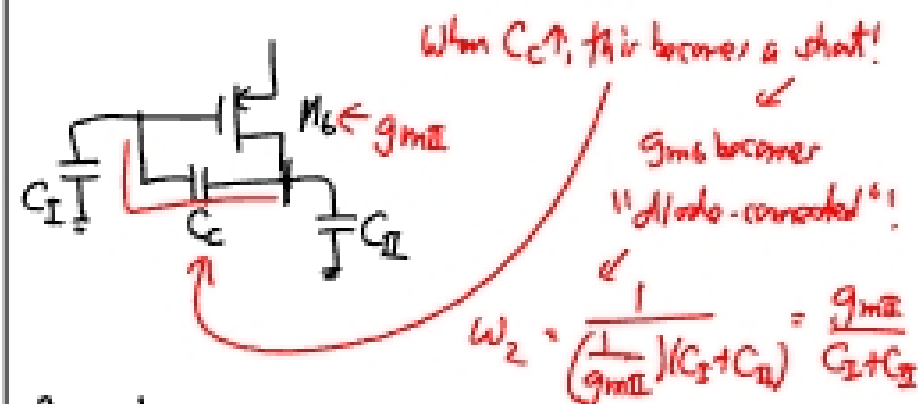As  $C_c \uparrow \rightarrow p_2 \approx - \frac{g_{m2}}{C_I + C_D} \leftarrow$  This is higher than before!  
 $C_c \uparrow \rightarrow p_2 \uparrow$



Remarks:

- ① Note that as  $C_c \uparrow \rightarrow p_1 \downarrow \rightarrow 0$
- ② As  $C_c \uparrow \rightarrow p_2 \uparrow \rightarrow p_2 = \frac{g_{m2}}{C_I + C_D}$
- ③ With  $C_c = 0$  (i.e., before compensation)

$$p_1 = -\frac{1}{R_I C_I}, \quad p_2 = -\frac{1}{R_D C_D}$$

④ On a pole zero diagram:

