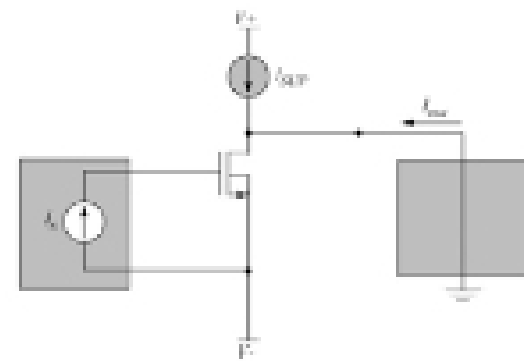


EE105 - Fall 2005
Microelectronic Devices and Circuits

Lecture 20

Common Source Amplifier
Frequency Response

Common Source Amplifier: $A_i(j\omega)$



DC Bias is problematic: what sets V_{GS} ?


6

Announcements

- › Homework 9 due next Tuesday
- › Lab 7 this week
- › Lab 8 next week (please read Chapter 9)
- › Reading: Chapter 10 (10.2, 10.3.2, 10.4.3-5)

2

CS Short-Circuit Current Gain

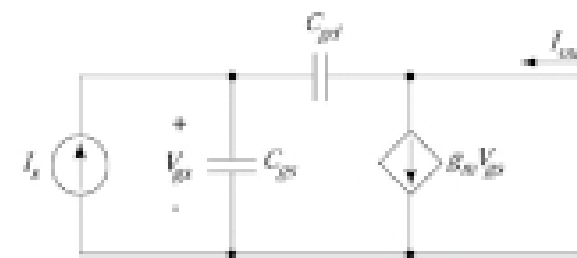

Transfer function:
$$A_i(j\omega) = \frac{g_m(1 - j\omega C_{gd}/g_m)}{j\omega(C_{gs} + C_{gd})}$$


8

Lecture Material

- › Last lecture
 - › Second-order circuits
 - › Started frequency response of amplifiers
- › This lecture
 - › Common source amplifier – frequency response
 - › Miller effect
 - › Zero-order time constants

3

Magnitude Bode Plot

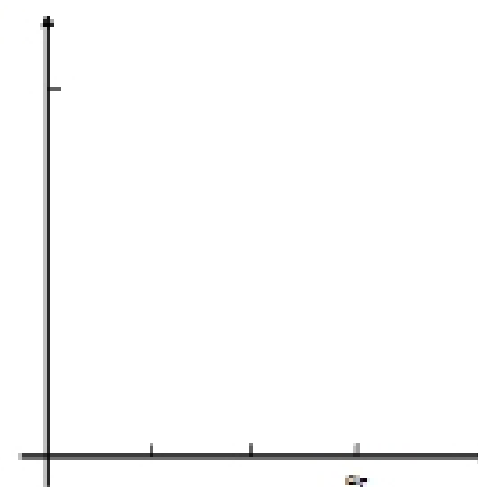

Transition frequency:
Current gain = 1

7

MOS Unity Gain Frequency

- Since the zero occurs at a higher frequency than pole, assume it has negligible effect:

$$A \approx \frac{g_m}{j\omega(C_{gs} + C_{gd})} = 1 \rightarrow \omega_u = \frac{g_m}{C_{gs} + C_{gd}}$$

$$\omega_u \approx \frac{g_m}{C_{gs}} = \frac{\mu C_{ox} \frac{W}{L} (V_{gs} - V_T)}{\frac{2}{3} W L C_{ox}} = \frac{3}{2} \frac{\mu (V_{gs} - V_T)}{L^2}$$

Performance improves with L^2 for long channel devices!
For short channel devices the dependence is $\sim L^1$

$$\omega_u \approx \frac{3}{2} \frac{\mu (V_{gs} - V_T)}{L} \sim \frac{\mu \frac{V_{gs} - V_T}{L}}{L} = \frac{\mu E_{sc}}{L} = \frac{v}{L} = \tau_c^{-1}$$

Time to cross channel τ_c

Frequency Response

KCL at input and output nodes; analysis is made complicated due to Z_{gs} branch \rightarrow see H&S pp. 839-840 (for common emitter)


$$\frac{V_{out}}{V_{in}} = \frac{-g_m [r_o \parallel r_{oc} \parallel R_L] (1 - j\omega/\omega_z)}{(1 + j\omega/\omega_{p1})(1 + j\omega/\omega_{p2})}$$

Low-frequency gain:

$$\text{Zero: } \omega_z > \omega_T = \frac{g_m}{C_{gs} + C_{gd}}$$

11

Common-Source Voltage Amplifier

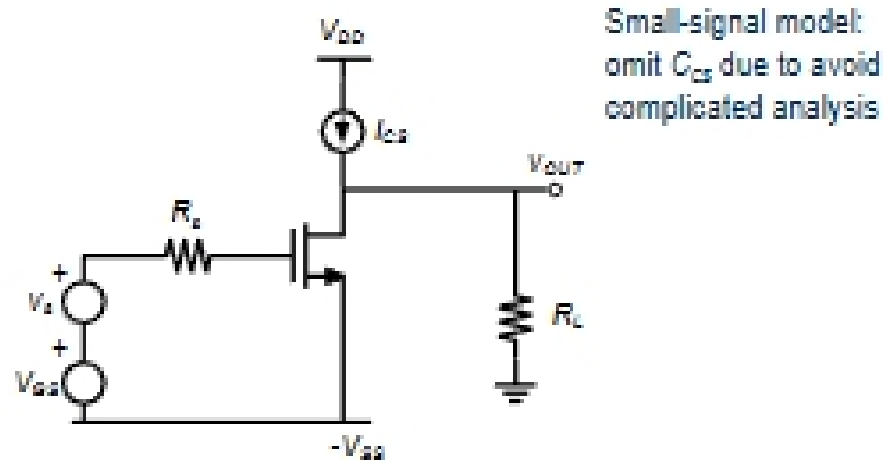

Small-signal model:
omit C_{gs} due to avoid
complicated analysis

8


Poles

$$\omega_{p1} \approx \frac{1}{R_S \{C_{gs} + (1 + g_m R'_{out}) C_{gd}\} + R'_{out} C_{gd}}$$

$$\omega_{p2} \approx \frac{R'_{out} / R_S}{R_S \{C_{gs} + (1 + g_m R'_{out}) C_{gd}\} + R'_{out} C_{gd}}$$

12

CS Voltage Amp Small-Signal Model

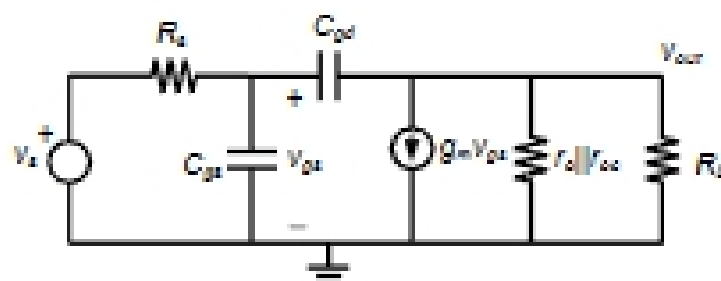


10

Miller Impedance

- Consider the current flowing through an impedance Z hooked up to a "black-box" where the voltage gain from one terminal to the other is fixed

$$A_v = \frac{v_2}{v_1}$$

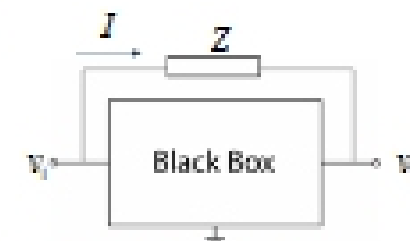

$$I = \frac{v_1 - v_2}{Z} = \frac{v_1 - A_v v_1}{Z} = v_1 \frac{1 - A_v}{Z}$$

13

Miller Impedance

- Notice that the current flowing into Z from terminal 1 looks like an equivalent current to ground where Z is transformed down by the Miller factor:

$$I = v_1 \frac{1-A_v}{Z} \rightarrow Z_{in,1} = \frac{Z}{1-A_v}$$

- From terminal 2, the situation is reciprocal

$$-I = \frac{v_2 - v_1}{Z} = \frac{v_2 - A_v^{-1}v_2}{Z} = v_2 \frac{1-A_v^{-1}}{Z}$$

$$Z_{in,2} = \frac{Z}{1-A_v^{-1}}$$

14

Comparison with "Exact Analysis"

Miller result:

$$\omega_{p1}^{-1} =$$


Exact result:

$$\omega_{p1}^{-1} = (R_S \parallel r_{\pi}) \{ C_{\pi} + (1 + g_m R'_{out}) C_{\mu} \} + R'_{out} C_{\mu}$$

17

Miller Equivalent Circuit

Note: $Z_{in,1} + Z_{in,2} = Z$

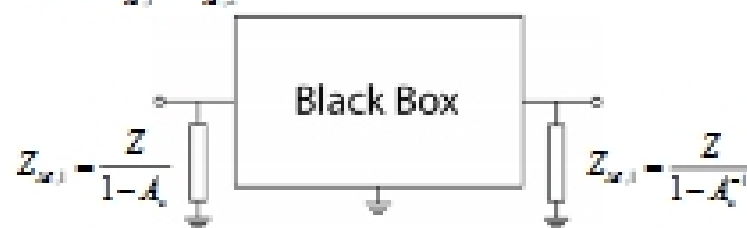

- We can decouple these terminals if we can calculate the gain A_v across the impedance Z
- Often the gain A_v is weakly dependent on Z
- The approximation is to ignore Z , calculate A_v , and then use the decoupled Miller impedances

16

Some Examples

Common source amplifier:

$$A_v C_{gd} = \text{negative, large number } (-100)$$

Miller multiplied cap has detrimental impact on bandwidth

Common drain amplifier:


$$A_v C_{gd} = \text{slightly less than 1}$$

"Bootstrapped" cap has negligible impact on bandwidth!

18

CE Amplifier using Miller Approx.

Use Miller to transform C_{gd}

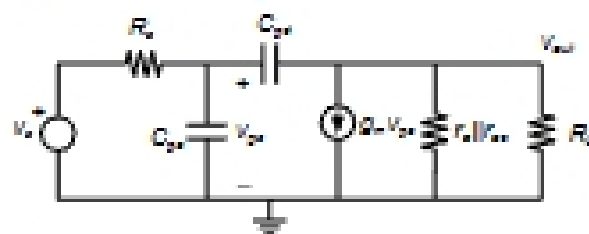

18

Method of Open Circuit Time Constants

- This is a technique to find the dominant pole of a circuit (only valid if there really is a dominant pole!)
- For each capacitor in the circuit you calculate an equivalent resistor "seen" by capacitor and form the time constant $\tau_i = R_i C_i$
- The dominant pole then is the sum of these time constants in the circuit

$$\omega_{p,dom} = \frac{1}{\tau_1 + \tau_2 + \dots}$$

18