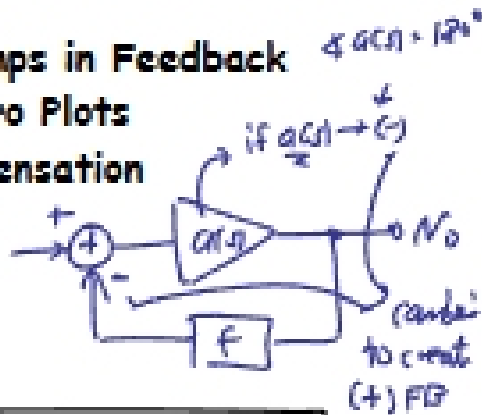


• Announcements:

- ↳ Evening lecture today, 7 p.m., in 289 Cory
- ↳ You should be finished with a draft design of your op amp project by now

• Today:

- ↳ Stability of Op Amps in Feedback  $\angle a(s) = 180^\circ$
- ↳ Review of Pole/Zero Plots
- ↳ Methods for Compensation
  - Narrowbanding
  - Pole-Splitting



Last Time -

Stability of FB Ckt. Using a Single Pole Op Amp

For a single pole op amp:  $a(s) = \frac{a_0}{1 - \frac{s}{P_1}} \equiv$  op amp transfer function

Then: closed loop Xfb. For

$$A(s) = \frac{a(s)}{1 + a(s)f} = \frac{a_0}{1 + a_0f} \frac{1}{1 - \frac{s}{P_1(1 + a_0f)}}$$

↑  
mult high 3dB freq.


$A_0 =$  closed loop dc gain  $\rightarrow (1 + a_0f) \approx a_0f \times$  smaller than  $a_0$   
 $\approx \frac{1}{f}$

$T_0 = a_0f =$  loop gain (defined at dc)

$T(s) = a(s)f =$  loop transmission (defined for general frequencies)

Bode Plot:  $\rightarrow$  use to determine

$\angle a(s)f$  when  $|a(s)f| = 1 \leftarrow$  then can determine stability

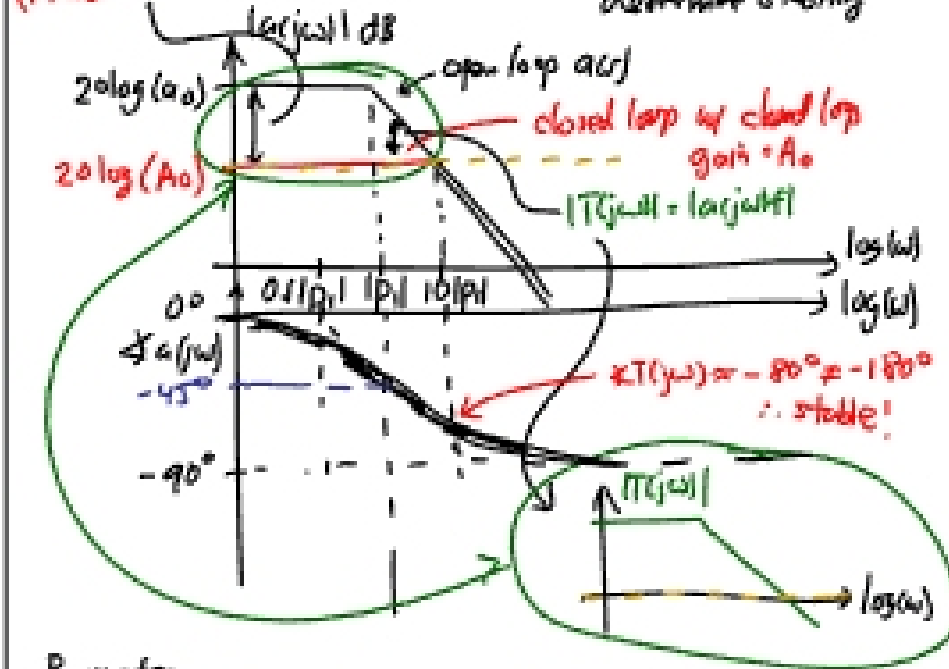


Remarks:

- ① For the case of a single pole op amp, FB can never reach  $\angle T(j\omega) = -180^\circ!$  ( $90^\circ$  is the limit!)
- ② Thus, an op amp FB ckt. w/  $f =$  const. and using a single-pole op amp is always stable!

↓  
But add a few non-dominant poles  $\rightarrow$  then instability is possible!

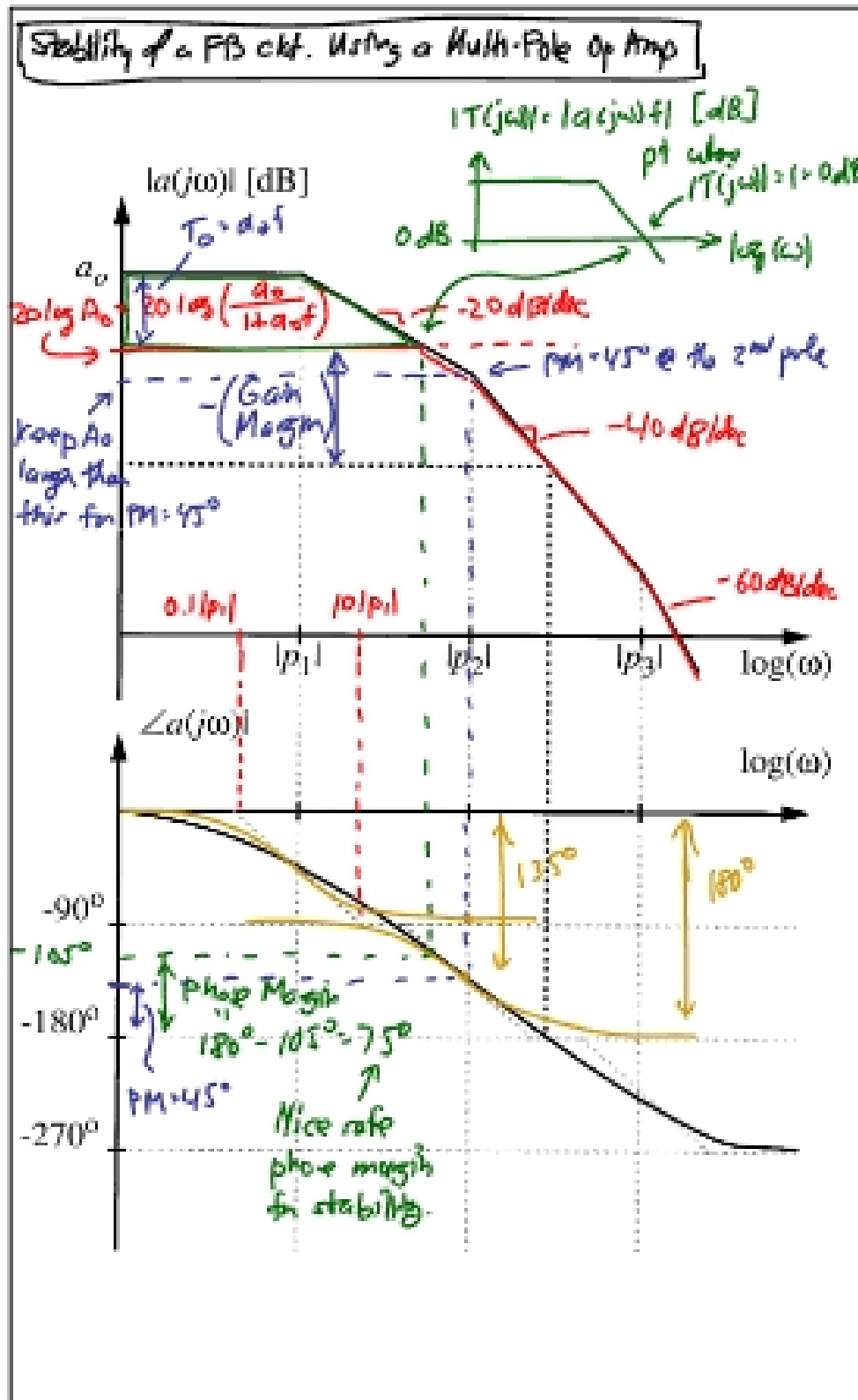Since now,  $\angle T(j\omega)$  can reach  $-180^\circ!$   
 $\rightarrow$  Can't visualize this via a Bode plot.



For the more general case where a LO has multiple poles  
 $\Rightarrow A(s)$  has the same additional poles  
 $\Rightarrow$  i.e., @ freqs.  $> |p_1|$  (H a.o.f), the  $A(s)$  curve just follows the a(s) curve

$$A(s) \cong \frac{A_0}{\left(1 - \frac{s}{p_1(H a.o.f)}\right) \left(1 - \frac{s}{p_2}\right) \left(1 - \frac{s}{p_3}\right)}$$

makes sense, because @ freqs.  $> |p_1|$  (H a.o.f), the loop transmission  $|T(j\omega)| < 1 \rightarrow \therefore$  there isn't really much FB anymore...

Definition:

Phase Margin =  $180^\circ + (\angle T(j\omega) \text{ @ the freq. where } |T(j\omega)| = 1)$

$\Rightarrow$  Phase Margin must be  $> 0^\circ$  for stability

For Stability:  $\text{Phase Margin} > 0^\circ$

$\Rightarrow$  For safety, though, usually design for


Phase Margin  $\geq 45^\circ$

Design Criterion (for practical design)

Definition:

Gain Margin  $\equiv |T(j\omega)|$  in dB @ freq. where  $\angle T(j\omega) = -180^\circ$

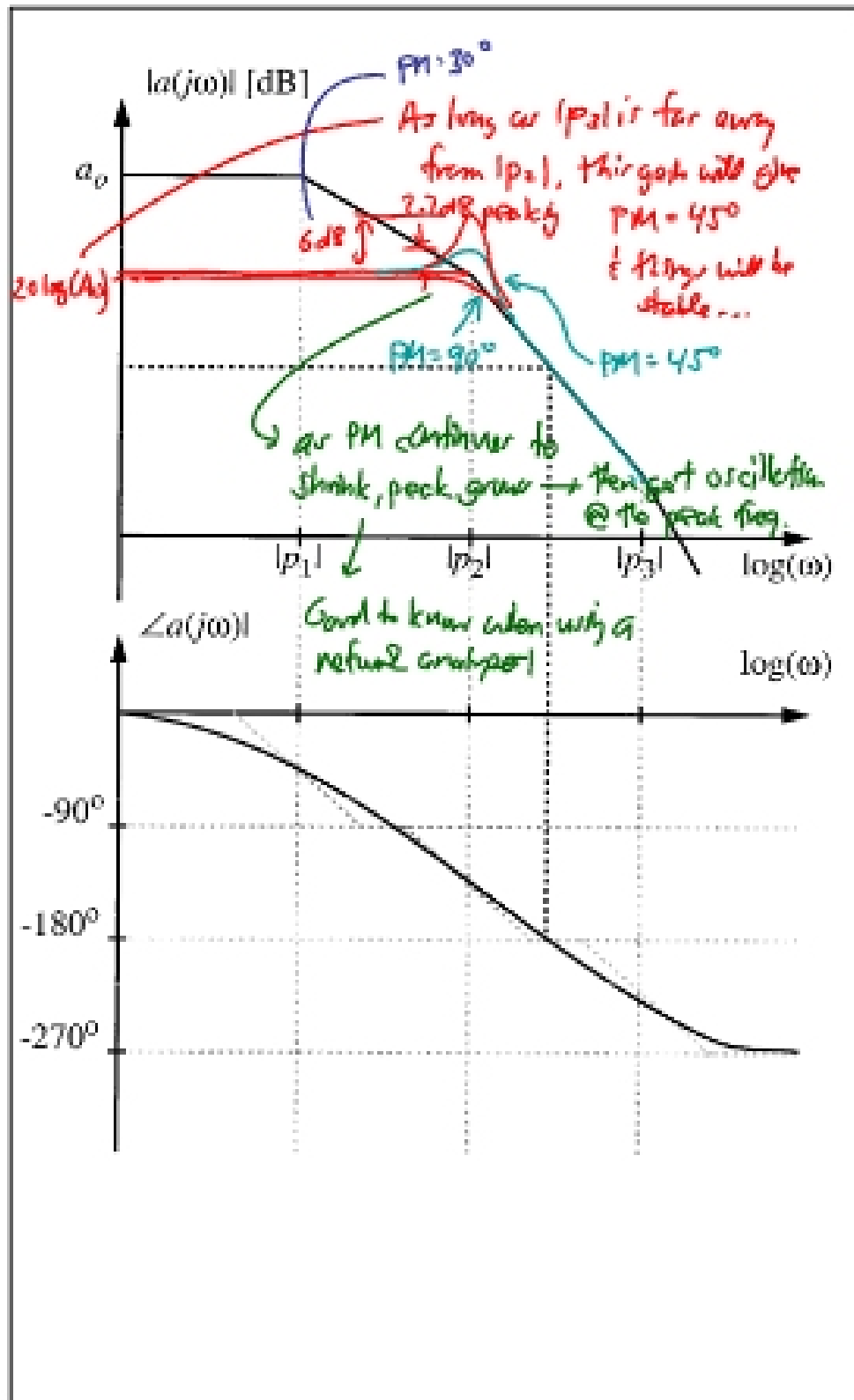For stability:  $\text{Gain Margin} < 0 \text{ dB}$



### Compensation of Op Amps

To compensate, need the distance between  $p_1$  &  $p_2$  to be large enough to encompass the largest desired loop gain!

$|a(j\omega)|$  [dB]

$\log(\omega)$

steepest = -20 dB/dec

maximum  $T_{max}$  to that still allow  $PM = 45^\circ$

$\log(\omega)$

$\frac{a_0}{1+c_0 T_{max}}$

$a_0$

$1+c_0 T_{max}$

$20 (\log |p_2| - \log |p_1|) = 20 \log (T_{max})$

$\frac{|p_2|}{|p_1|} = T_{max} \rightarrow |p_2| = |p_1| T_{max}$

largest desired (expected) loop gain

provided  $|p_2| \gg |p_1|$

Need for stability w/  $PM = 45^\circ$  @ all desired closed loop gains

Two Ways to Compensate:

- ① Narrowbanding
- ② Pole-splitting

Basically, there is a minimum separation between  $p_1$  &  $p_2$  that insures stability.