 


Instructor: Robert Dick
 Office: L477 Tech
 Email: dickrp@northwestern.edu
 Phone: 847-467-2298


TA: Neal Oza
 Office: Tech. Inst. L375
 Phone: 847-467-0033
 Email: neoza@u.northwestern.edu

TT: David Bild
 Office: Tech. Inst. L470
 Phone: 847-401-2083
 Email: d-bild@northwestern.edu




NORTHWESTERN
UNIVERSITY

Other TG diagram

 

Impact of control on input

 

Two-Level Logic and Canonical Forms

- The previous example illustrated one standard representation (product of sums).
- These standard forms are known collectively as two-level logic:
 - Product of Sums (POS) e.g.


$$f = (a + \bar{b})(\bar{a} + b)$$

- Sum of Products (SOP) e.g.


$$f = \bar{a}\bar{b} + ab$$

- Can you see why these two are equivalent?
- Why is this known as two-level logic?

CMOS transmission gate (TG)

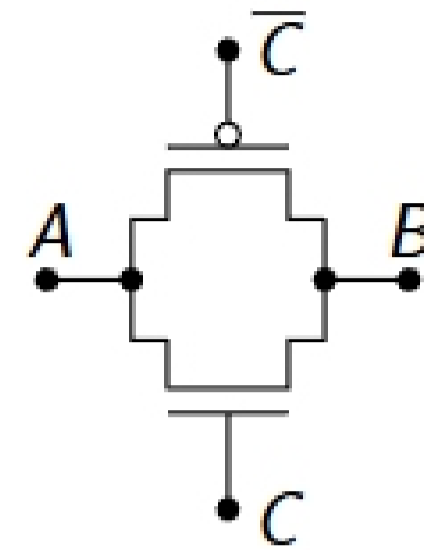

TG example

 

Practice w/ Boolean Minimization

Simplify this expression so that it has the minimal possible literal count:

$$(a + \bar{b})(\bar{a}\bar{b} + cd)$$

Canonical forms - SOP

For Sum of Products (SOP) the canonical form is constructed out of minterms.

- Product term in which all variables appear in complemented or uncomplemented forms once
- For an n-input function corresponds to one of 2^n possible input combinations
- Use binary representation to enumerate minterms

Canonical forms – SOP

x	y	z	term	symbol	m_0	m_1	m_2	m_3	m_4	m_5	m_6	m_7
0	0	0	$\bar{x}\bar{y}\bar{z}$	m_0	1	0	0	0	0	0	0	0
0	0	1	$\bar{x}\bar{y}z$	m_1	0	1	0	0	0	0	0	0
0	1	0	$\bar{x}y\bar{z}$	m_2	0	0	1	0	0	0	0	0
0	1	1	$\bar{x}yz$	m_3	0	0	0	1	0	0	0	0
1	0	0	$x\bar{y}\bar{z}$	m_4	0	0	0	0	1	0	0	0
1	0	1	$x\bar{y}z$	m_5	0	0	0	0	0	1	0	0
1	1	0	$xy\bar{z}$	m_6	0	0	0	0	0	0	1	0
1	1	1	xyz	m_7	0	0	0	0	0	0	0	1

11

R. Dick

Introduction to Computer Engineering – EECS 303

Canonical forms – POS

For Products of Sums (POS) the canonical form is constructed out of maxterms.

- Sum term in which all variables appear in complemented or uncomplemented forms once
- Use binary representation to enumerate maxterms (note: function is not true for maxterms)

13

R. Dick

Introduction to Computer Engineering – EECS 303

Using Canonical Products of Sums Representation

Convenient representation uses \prod operator and minterms:

$$f(x_1, \dots, x_n) = \prod M_i$$

For given function f , list all maxterms for which the function is false:

$$\begin{aligned} f(a, b, c) &= (a + \bar{c})(\bar{a} + b) \\ &= M_1 \cdot M_3 \cdot M_4 \cdot M_5 \\ &= \prod M(1, 3, 4, 5) \end{aligned}$$

15

R. Dick

Introduction to Computer Engineering – EECS 303

Logic minimization motivation

- Want to reduce area, power consumption, delay of circuits
- Hard to exactly predict circuit area from equations
- Can approximate area with SOP cubes
- Minimize number of cubes and literals in each cube
- Algebraic simplification difficult
 - Hard to guarantee optimality

17

R. Dick

Introduction to Computer Engineering – EECS 303

Using Canonical Sum of Products Representation

Convenient representation uses \sum operator and minterms:

$$f(x_1, \dots, x_n) = \sum m_i$$

For given function f , list all minterms for which the function is true:

$$\begin{aligned} f(a, b, c) &= ab + \bar{a}c \\ &= (m_6 + m_7) + (m_0 + m_2) \\ &= \sum m(0, 2, 6, 7) \end{aligned}$$

12

R. Dick

Introduction to Computer Engineering – EECS 303

Canonical forms – POS

x	y	z	term	symbol	M_0	M_1	M_2	M_3	M_4	M_5	M_6	M_7
0	0	0	$x+y+z$	M_0	0	1	1	1	1	1	1	1
0	0	1	$x+y+\bar{z}$	M_1	1	0	1	1	1	1	1	1
0	1	0	$x+\bar{y}+z$	M_2	1	1	0	1	1	1	1	1
0	1	1	$x+\bar{y}+\bar{z}$	M_3	1	1	1	0	1	1	1	1
1	0	0	$\bar{x}+y+z$	M_4	1	1	1	1	0	1	1	1
1	0	1	$\bar{x}+y+\bar{z}$	M_5	1	1	1	1	1	0	1	1
1	1	0	$\bar{x}+\bar{y}+z$	M_6	1	1	1	1	1	1	0	1
1	1	1	$\bar{x}+\bar{y}+\bar{z}$	M_7	1	1	1	1	1	1	1	0

14

R. Dick

Introduction to Computer Engineering – EECS 303

More examples of two-level logic

$$f(a, b, c, d) = \sum m(1, 4, 8, 10, 13, 15)$$

$$f(w, x, y, z) = \prod M(5, 13, 14)$$

$$f(u, v) = u + \bar{u}v$$

16

R. Dick

Introduction to Computer Engineering – EECS 303

Logic minimization motivation

- K-maps work well for small problems
 - Too error-prone for large problems
 - Don't ensure optimal prime implicant selection
- Quine-McCluskey optimal and can be run by a computer
 - Too slow on large problems
- Some advanced heuristics usually get good results fast on large problems
- Want to learn how these work and how to use them?
- Take Advanced Digital Logic Design

18


R. Dick

Introduction to Computer Engineering – EECS 303

Boolean function minimization


- Algebraic simplification
 - Not systematic
 - How do you know when optimal solution has been reached?
- Optimal algorithm, e.g., Quine-McCluskey
 - Only fast enough for small problems
 - Understanding these is foundation for understanding more advanced methods
- Not necessarily optimal heuristics
 - Fast enough to handle large problems

Karnaugh maps

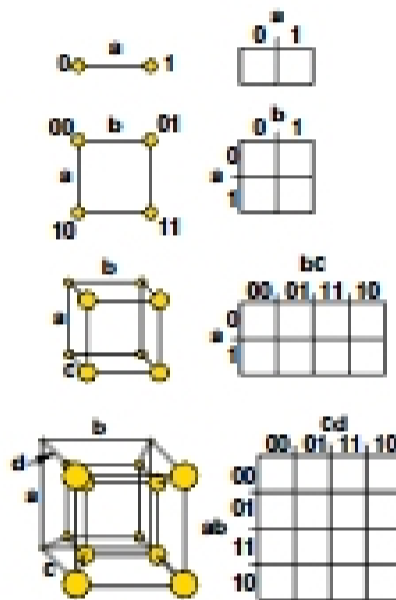


Sum of products (SOP) - KMap

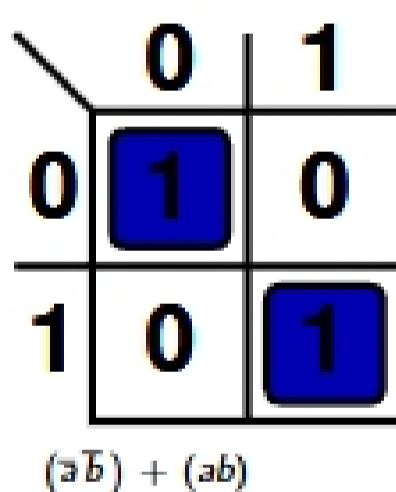Equivalent way of expressing the same function:



Implicants

For now, treat x as a "wildcard"

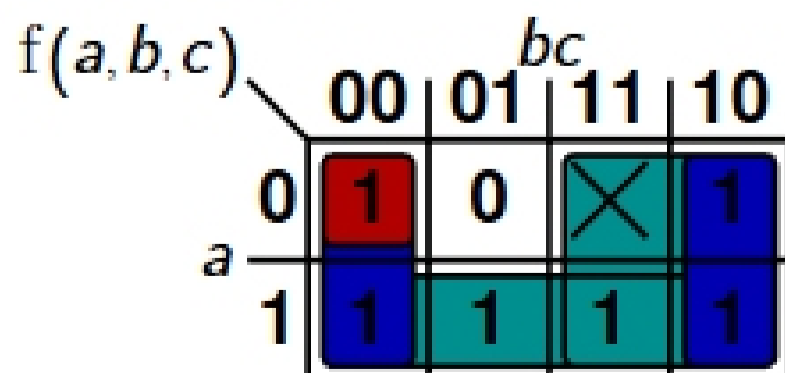

Prime implicants are not covered by other implicants Essential prime implicants uniquely cover minterms

Karnaugh maps (K-maps)

- Fundamental attribute is adjacency
- Useful for logic synthesis
- Helps logic function visualization
- General Idea: Circle groups of output values (typically 1's)
- Result: Circled terms correspond to minimized product terms

Sum of products (SOP) - Truth table

a	b	f
0	0	1
0	1	0
1	0	0
1	1	1

$$f = (\bar{a}\bar{b}) + (ab)$$

Some definitions

- implicant* - a product term (or sum term) which covers/includes one or more minterms (or maxterms)
- prime implicant* - implicant that cannot be covered by a more general implicant (i.e. one with fewer literals)
- essential prime implicants* - cover an output of the function that no other prime implicant (or sum thereof) is able to cover

K-map example

- Minimize $f(a, b, c, d) = \sum(1, 3, 8, 9, 10, 11, 13)$
- $f(a, b, c, d) = a\bar{b} + \bar{b}d + a\bar{c}d$