

Instructor: Robert Dick  
 Office: L477 Tech  
 Email: dickrp@northwestern.edu  
 Phone: 847-467-2298

TA: Neal Oza  
 Office: Tech. Inst. L375  
 Phone: 847-467-0033  
 Email: nealoz@u.northwestern.edu

TT: David Bild  
 Office: Tech. Inst. L470  
 Phone: 847-401-2083  
 Email: d-bild@northwestern.edu



NORTHWESTERN  
UNIVERSITY

Encoder example

Pressed ( $i_2, i_1, i_0$ )	Code ( $a_1, a_0$ )
000	00
001	01
010	10
011	XX
100	11
101	XX
110	XX
111	XX

Implementation?

Decoders

Need to map back from encoded signal to state

Pressed ( $i_1, i_0$ )	Code ( $a_3, a_2, a_1, a_0$ )
00	0001
01	0010
10	0100
11	1000

$a_0$  isn't always used. Why?  
 Most straightforward implementation?

Decoder implementation efficiency

- $n$  NOTs
- $n^2$   $n$ -input ANDS
- $\mathcal{O}(n^2)$
- Can't do this for large number of inputs!
- Instead, decompose into multi-level implementation

Encoders

- Assume you have  $n$  one-bit signals
- Only one signal can be 1 at a time
- How many states can you be in?
- How many signals are required to encode all those states?


Priority encoder

What if we want the highest-order high signal to dominate?

Pressed ( $i_3, i_2, i_1$ )	Code ( $a_1, a_0$ )
000	00
001	01
010	10
011	10
100	11
101	11
110	11
111	11

What impact on implementation efficiency?

Straight-forward decoder implementation

 

Multilevel decoder implementation

Starting point


- $a_0 = \bar{i}_2 \bar{i}_1 \bar{i}_0$
- $a_1 = \bar{i}_2 \bar{i}_1 i_0$
- $a_2 = \bar{i}_2 i_1 \bar{i}_0$
- $a_3 = \bar{i}_2 i_1 i_0$
- $a_4 = i_2 \bar{i}_1 \bar{i}_0$
- $a_5 = i_2 \bar{i}_1 i_0$
- $a_6 = i_2 i_1 \bar{i}_0$
- $a_7 = i_2 i_1 i_0$

### Multilevel decoder implementation

$$\begin{aligned}
 o_0 &= \bar{i}_2 (\bar{i}_1 \bar{i}_0) \\
 o_1 &= \bar{i}_2 (\bar{i}_1 i_0) \\
 o_2 &= \bar{i}_2 (i_1 \bar{i}_0) \\
 o_3 &= \bar{i}_2 (i_1 i_0) \\
 o_4 &= i_2 (\bar{i}_1 \bar{i}_0) \\
 o_5 &= i_2 (\bar{i}_1 i_0) \\
 o_6 &= i_2 (i_1 \bar{i}_0) \\
 o_7 &= i_2 (i_1 i_0)
 \end{aligned}$$

Reuse terms! Schematic?

### Logic gate MUX

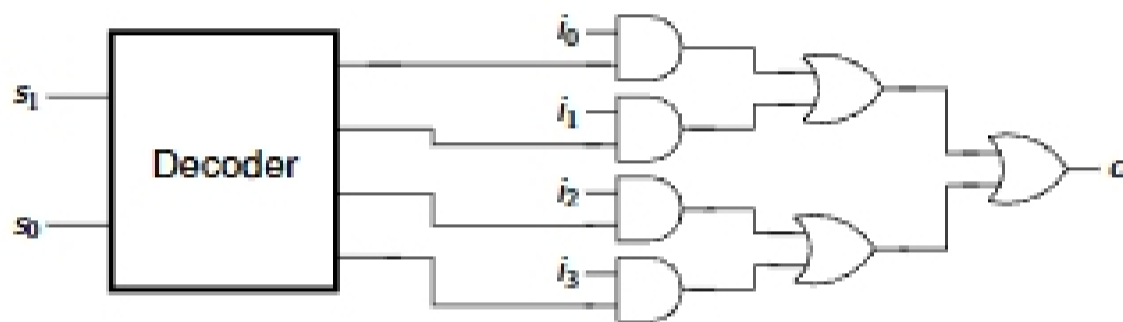


However, there is another way...

### MUX truth table

$i_1$	$i_0$	$C$	$Z$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

### Review: Other TG diagram

 


### Multiplexers or selectors

- Routes one of  $2^n$  inputs to one output
- $n$  control lines
- Can implement with logic gates


### MUX functional table

$C$	$Z$
0	$i_0$
1	$i_1$


### Review: CMOS transmission gate (TG)

 


### MUX

 


MUX using TGs

 

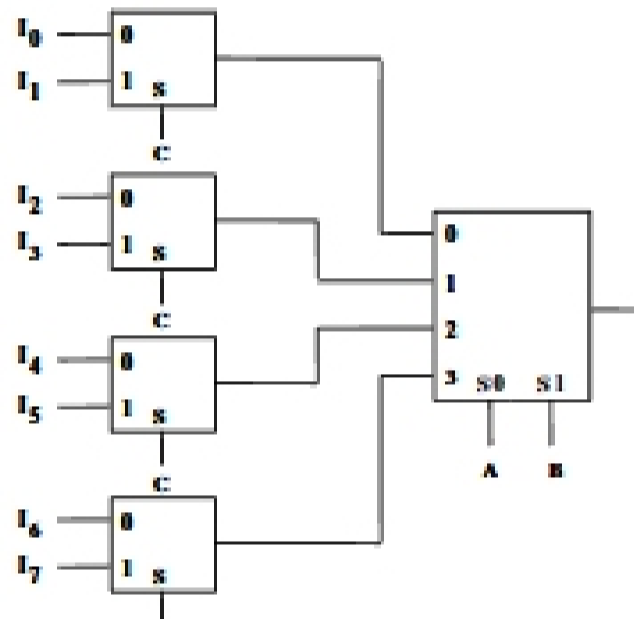Alternative hierarchical MUX implementation




MUX examples

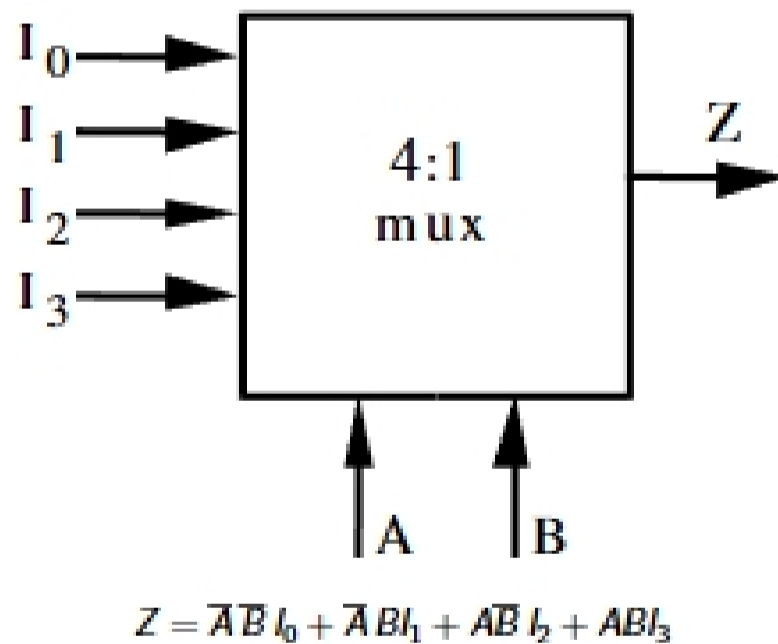


MUX properties

- A  $2^n : 1$  MUX can implement any function of  $n$  variables
- A  $2^{n-1} : 1$  can also be used
  - Use remaining variable as an input to the MUX


Hierarchical MUX implementation

 

MUX examples

 

MUX examples

 

MUX example

$$F(A, B, C) = \sum(0, 2, 6, 7) = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$