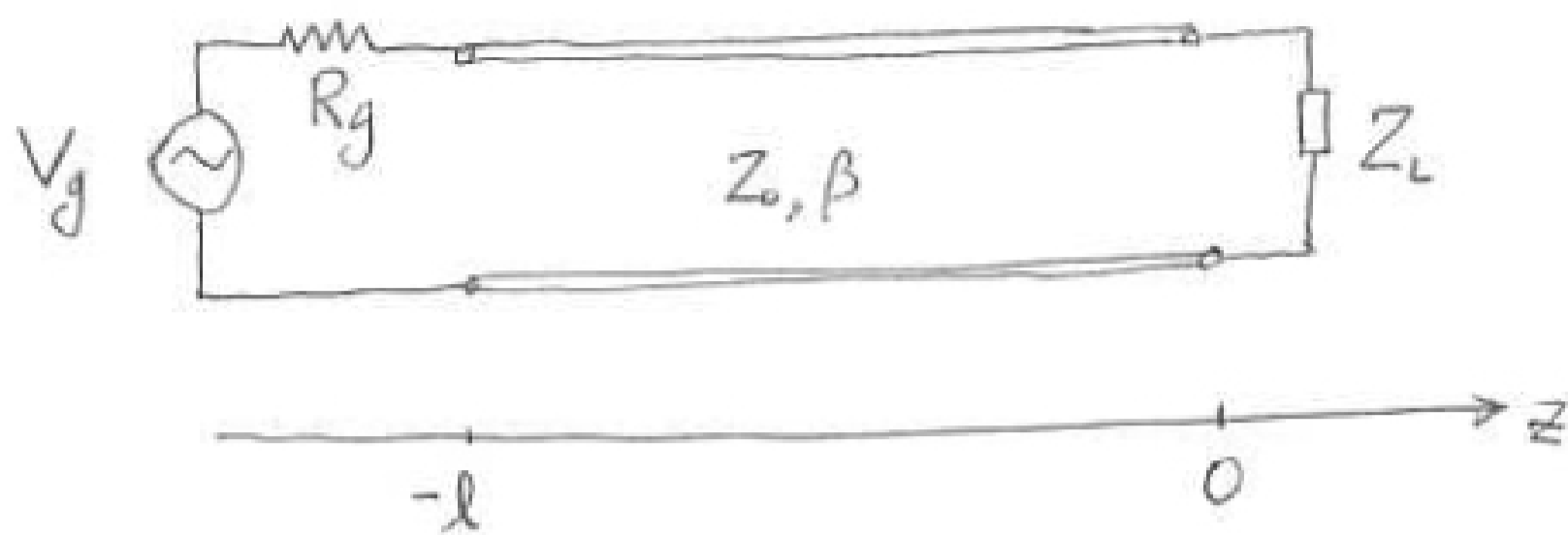


The following problems refer to this graph

①



$$V_g = 120 \text{ V}$$

$$R_g = 30 \Omega$$

$$Z_0 = 50 \Omega \quad \text{--- characteristic impedance of transmission line}$$

$$\beta = \frac{2\pi}{\lambda}, \quad \lambda = 8 \text{ cm}$$

$$l = 26.64$$

$$Z_L = 40 - j70 \Omega$$

1. Calculate Γ_L , Φ_L , VSWR, z_{vm}

$$\begin{aligned} \Gamma_L &= \text{Load reflection coefficient} \quad \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{40 - j70 - 50}{40 - j70 + 50} = 0.31 - j0.54 \\ &= |\Gamma_L| e^{j\Phi_L} = 0.62 e^{-j60.26^\circ} \\ \Phi_L &= -60.26^\circ \end{aligned}$$

VSWR = Voltage Standing Wave ratio

$$= \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \frac{1 + 0.62}{1 - 0.62} = 4.26$$

z_{vm} = distance of the first voltage min position to load


The phase of reflection coefficient

$$\Phi = \Phi_L + 2\beta z = \Phi_L - 2\beta |z|$$

When $\Phi = \pm\pi, \pm 3\pi, \dots$

Since $\Phi_L = -60.26^\circ = -1.05 \text{ (Rad)} < 0$
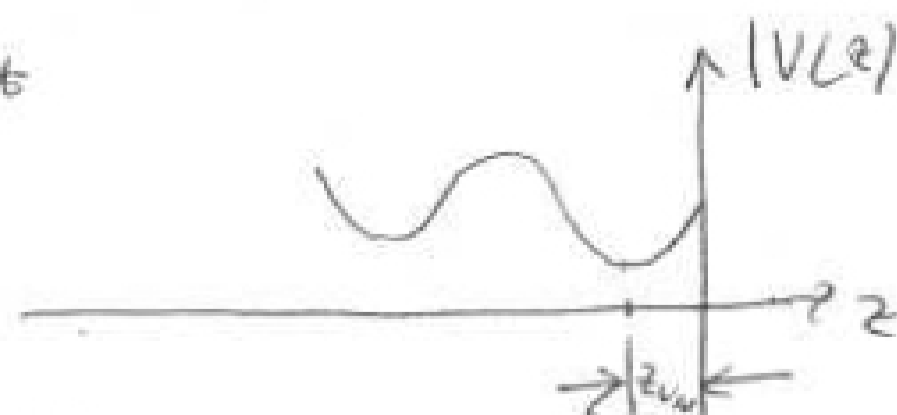
$$\text{Hence: } -1.05 - 2\beta(z_{vm}) = -\pi$$



Note: z_{vm} is a positive distance

(2)

$$-1.05 - 2 \cdot \frac{2\pi}{0.08} z_{vm} = -3.14 \Rightarrow 0.0267 \text{ m} \\ \text{or } 2.67 \text{ cm}$$

2. Calculate the input impedance $Z_{in}(-l)$ and the reflection coefficient $\Gamma(-l)$

$$\Gamma(z) = \Gamma_L e^{j2\beta z} = |\Gamma_L| e^{j\Phi_L - j2\beta|z|}$$

$$\Gamma(-l) = |\Gamma_L| e^{j\Phi_L - j2\beta l} = 0.62 e^{-j1.05 - j\frac{4\pi}{0.08} \cdot 0.02664} \\ = 0.62 e^{-j42.9} = 0.29 + j0.55$$

$$Z_{in} = Z_0 \frac{1 + \Gamma(-l)}{1 - \Gamma(-l)} = 50 \frac{1 + [0.29 + j0.55]}{1 - [0.29 + j0.55]} = 38.1 + j68.0 \Omega$$

or: Using impedance transformation equation

$$Z_{in} = Z_0 \frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l}$$

$$\beta l = \frac{2\pi \cdot 0.2664}{0.08} = 20.923, \quad \cos \beta l = -0.482 \\ \sin \beta l = 0.876$$

$$Z_{in} = 50 \frac{(40 - j70)(-0.482) + j50 \cdot 0.876}{50(-0.482) + j(40 - j70) \cdot 0.876} = 38.1 + j68.0 \Omega$$

The impedance transformation formula can also be written as


$$Z_{in}(-l) = Z_0 \frac{Z_L + j Z_0 \tan(\beta l)}{Z_0 + j Z_L \tan(\beta l)}$$

3. For what min value of $l > 0$, $Z_{in}(-l) = Z_L$?

when $\tan(\beta l) = 0$, we have $Z_{in}(-l) = Z_L$

$$\text{solve: } \beta l = \pi, \quad l = \frac{\lambda}{2} = 4 \text{ cm}$$

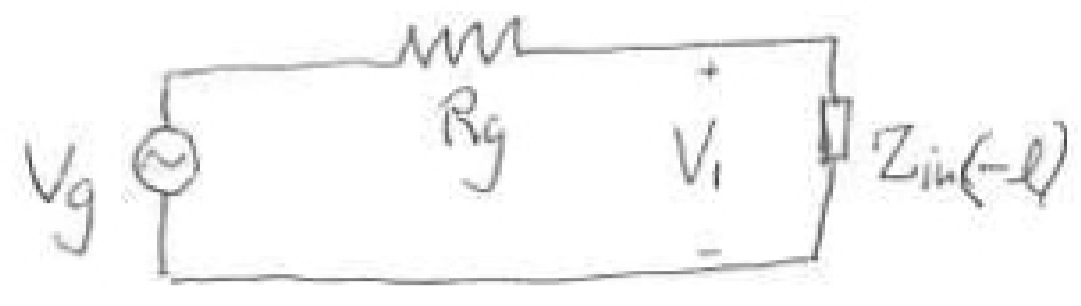4. Draw an equivalent circuit at $z = -l$ using $Z_{in}(l)$ to replace the transmission line and the load.



5. Using the equivalent circuit, calculate the voltage at the input to the transmission line (i.e. at $z = -l$)

Solution: it is marked as V_1 in 4 (above)

$$V_1 = \frac{Z_{in}(-l)}{Z_{in}(-l) + Z_0} V_g = \frac{38.1 + j68.0}{38.1 + j68.0 + 30} 120 = 93.6 + j26.4 \text{ (V)}$$

Exercise

Repeat the above for a) $Z_L = 30 + j40 \Omega$
 b) $Z_L = 60 - j10 \Omega$

Ans	Γ	Φ	VSWR	ϵ_{vm}	$\Gamma(-l)$	$Z_{in}(-l)$	V_1
a	$0 + j0.5$	90°	3	-0.03_m	$-0.42 - j0.27$	$17.9 - j12.8 \Omega$	$49.9 - j18.7 \text{ (V)}$
b	$0.098 - j0.082$	-39.8°	1.29	0.0156_m	$0.0165 + j0.017$	$50 + j12.9 \Omega$	$76.1 + j7.1 \text{ (V)}$

6. Using Smith Chart to perform operations for 1. and 2.

Solution: (a) The normalized $z_L = \frac{Z_L}{Z_0} = 0.8 - j1.4$

< See sketch on P. 4 >, (b) place z_L on chart at A.

(c) Read ANGLES of point A: $\Rightarrow \Phi_L$

(d) Measure $|\Gamma|$ Compare with bottom line $\Rightarrow |\Gamma|$

(e) Read VSWR

(f) $WTG(\Gamma) = 0.334$, $WTG(Z_{in}) = 0.334 + \frac{0.2664}{0.08} = 3.664 = 3.5 + \underline{0.164}$