

## Lecture 21


### OUTLINE

- Frequency Response
  - Review of basic concepts
  - high-frequency MOSFET model
  - CS stage
  - CG stage
  - Source follower
  - Cascode stage
- Reading: Chapter 11

EECS Spring 2008      Lecture 21, Slide 1      Prof. Wu, UC Berkeley
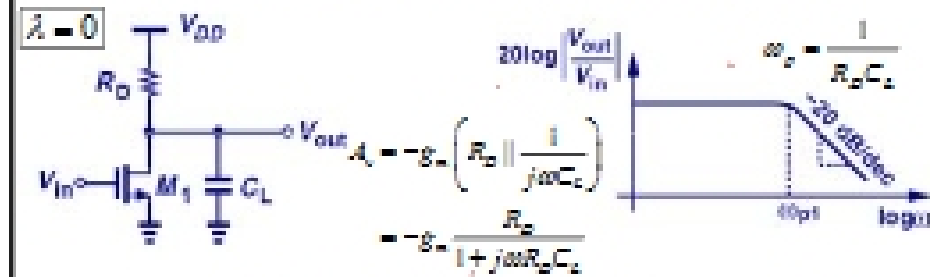
## $A_v$ Roll-Off due to $C_L$


- The impedance of  $C_L$  decreases at high frequencies, so that it shunts some of the output current to ground.



- In general, if node  $j$  in the signal path has a small-signal resistance of  $R_j$  to ground and a capacitance  $C_j$  to ground, then it contributes a pole at frequency  $(R_j C_j)^{-1}$


EECS Spring 2008      Lecture 21, Slide 2      Prof. Wu, UC Berkeley

## Pole Identification Example 1

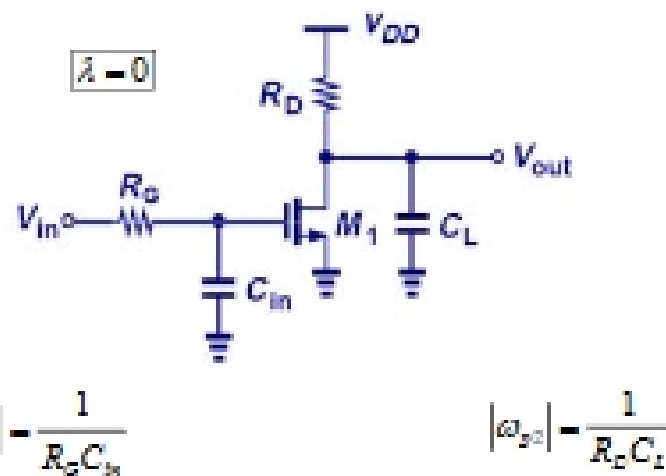

EECS Spring 2008      Lecture 21, Slide 3      Prof. Wu, UC Berkeley


## Pole Identification Example 2

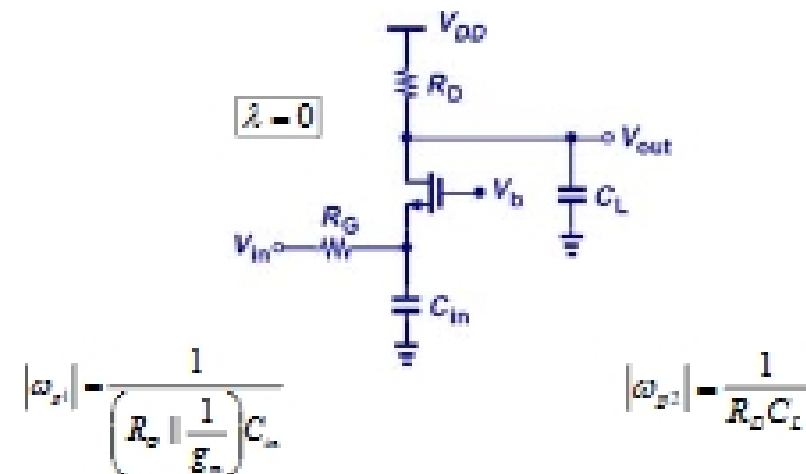

EECS Spring 2008      Lecture 21, Slide 4      Prof. Wu, UC Berkeley
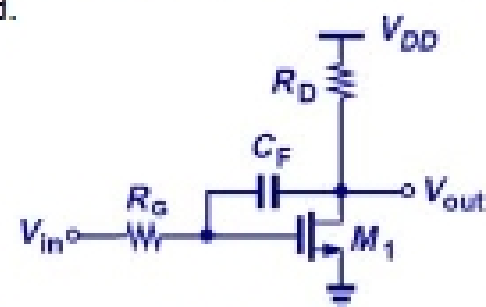
## Dealing with a Floating Capacitance


- Recall that a pole is computed by finding the resistance and capacitance between a node and (AC) GROUND.
- It is not straightforward to compute the pole due to  $C_F$  in the circuit below, because neither of its terminals is grounded.



EECS Spring 2008      Lecture 21, Slide 5      Prof. Wu, UC Berkeley
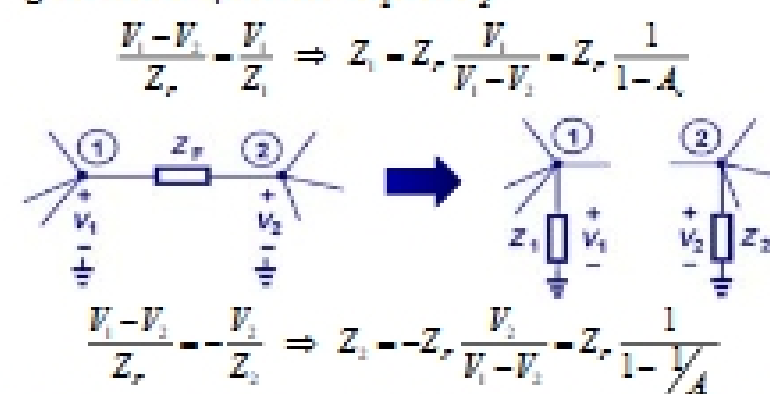
## Miller's Theorem

- If  $A_v$  is the voltage gain from node 1 to 2, then a floating impedance  $Z$ , can be converted to two grounded impedances  $Z_1$  and  $Z_2$ :



EECS Spring 2008      Lecture 21, Slide 6      Prof. Wu, UC Berkeley

### Miller Multiplication

- Applying Miller's theorem, we can convert a floating capacitance between the input and output nodes of an amplifier into two grounded capacitances.
- The capacitance at the input node is larger than the original floating capacitance.

$Z_i = \frac{Z_f}{1 - A_v}$ 
 $Z_o = \frac{Z_f}{1 - \frac{1}{A_v}}$

$C_{in} = C_f(1 - A_v)$ 
 $C_{out} = C_f(1 - \frac{1}{A_v})$

EE105 Spring 2008      Lecture 21, Slide 7      Prof. Wu, UC Berkeley

### Application of Miller's Theorem

$\lambda = 0$

$\frac{1}{Z_{in}} = \frac{1}{R_G} + j\omega C_{in}$ 
 $\frac{1}{Z_{out}} = \frac{1}{R_D} + j\omega C_{out}$

EE105 Spring 2008      Lecture 21, Slide 8      Prof. Wu, UC Berkeley

### MOSFET Intrinsic Capacitances

The MOSFET has intrinsic capacitances which affect its performance at high frequencies:

- gate oxide capacitance between the gate and channel,
- overlap and fringing capacitances between the gate and the source/drain regions, and
- source-bulk & drain-bulk junction capacitances ( $C_{SB}$  &  $C_{DB}$ ).

EE105 Spring 2008      Lecture 21, Slide 9      Prof. Wu, UC Berkeley

### High-Frequency MOSFET Model

- The gate oxide capacitance can be decomposed into a capacitance between the gate and the source ( $C_1$ ) and a capacitance between the gate and the drain ( $C_2$ ).
  - In saturation,  $C_1 \approx (2/3) \times C_{gate}$  and  $C_2 \approx 0$ . ( $C_{gate} = C_{ox}WL$ )
  - $C_1$  in parallel with the source overlap/fringing capacitance  $\rightarrow C_{GS}$
  - $C_2$  in parallel with the drain overlap/fringing capacitance  $\rightarrow C_{GD}$

EE105 Spring 2008      Lecture 21, Slide 10      Prof. Wu, UC Berkeley

### Example

...with MOSFET capacitances explicitly shown

Simplified circuit for high-frequency analysis

EE105 Spring 2008      Lecture 21, Slide 11      Prof. Wu, UC Berkeley

### Transit Frequency

- The "transit" or "cut-off" frequency,  $f_T$ , is a measure of the intrinsic speed of a transistor, and is defined as the frequency where the current gain falls to 1.

Conceptual set-up to measure  $f_T$

$I_{out} = g_m V_{in}$ 
 $\frac{I_{out}}{I_{in}} = |g_m Z_{in}| = \left| g_m \left( \frac{1}{j\omega C_{GS}} \right) \right| = 1$ 
 $\Rightarrow \omega_T = \frac{g_m}{C_{GS}}$ 
 $2\pi f_T = \frac{g_m}{C_{GS}}$

EE105 Spring 2008      Lecture 21, Slide 12      Prof. Wu, UC Berkeley

### Small-Signal Model for CS Stage

$\lambda = 0$

EECS Spring 2008      Lecture 11, Slide 14      Prof. Wu, UC Berkeley

### ... Applying Miller's Theorem

$V_{Thev} = V_{in}$   
 $R_{Thev} = R_G$   
 $C_X = C_{GD} (1 + g_m R_D)$   
 $C_Y = C_{GD} (1 + \frac{1}{g_m R_D})$

$\omega_{p,X} = \frac{1}{R_{Thev} (C_X + (1 + g_m R_D) C_{GD})}$   
 $\omega_{p,out} = \frac{1}{R_D (C_{out} + (1 + \frac{1}{g_m R_D}) C_{GD})}$

Note that  $\omega_{p,out} > \omega_{p,in}$

EECS Spring 2008      Lecture 11, Slide 14      Prof. Wu, UC Berkeley

### Direct Analysis of CS Stage

- Direct analysis yields slightly different pole locations and an extra zero:

$\omega_z = \frac{g_m}{C_{XY}}$

$\omega_{p1} = \frac{1}{(1 + g_m R_D) C_{XY} R_{Thev} + R_{Thev} C_{in} + R_D (C_{XY} + C_{out})}$

$\omega_{p2} = \frac{1}{R_{Thev} R_D (C_{in} C_{XY} + C_{out} C_{XY} + C_{in} C_{out})}$

EECS Spring 2008      Lecture 11, Slide 12      Prof. Wu, UC Berkeley

### I/O Impedances of CS Stage

$\lambda = 0$

$Z_{in} \approx \frac{1}{j\omega [C_{GS} + (1 + g_m R_D) C_{GD}]}$        $Z_{out} = \frac{1}{j\omega [C_{GD} + C_{DB}]} \parallel R_D$

EECS Spring 2008      Lecture 11, Slide 12      Prof. Wu, UC Berkeley

### CG Stage: Pole Frequencies

CG stage with MOSFET capacitances shown

$\lambda = 0$

$\omega_{p,X} = \frac{1}{(R_S \parallel \frac{1}{g_m}) C_X}$   
 $C_X = C_{GS} + C_{GD}$

$\omega_{p,Y} = \frac{1}{R_D C_Y}$   
 $C_Y = C_{GD} + C_{DB}$

EECS Spring 2008      Lecture 11, Slide 17      Prof. Wu, UC Berkeley

### AC Analysis of Source Follower

$\lambda = 0$

The transfer function of a source follower can be obtained by direct AC analysis, similarly as for the emitter follower

$\frac{V_{out}}{V_{in}} = \frac{1 + (j\omega) \frac{C_{GD}}{g_m}}{a(j\omega) + b(j\omega) + 1}$

$a = \frac{R_S}{g_m} (C_{GD} C_{DB} + C_{GD} C_{SB} + C_{DB} C_{SB})$   
 $b = R_S C_{GD} + \frac{C_{DB} + C_{SB}}{g_m}$

EECS Spring 2008      Lecture 11, Slide 18      Prof. Wu, UC Berkeley