

Steady state - all voltages and currents are constant but this occurs some time after the circuit has settled


\* Review of phasors

March 23, 2015

$$v(t) = A \cos(\omega t + \theta) \rightarrow V(j\omega) = A e^{j\theta} = A \cos \theta + j A \sin \theta = A \angle \theta$$

Rectangular                      polar

Ex.

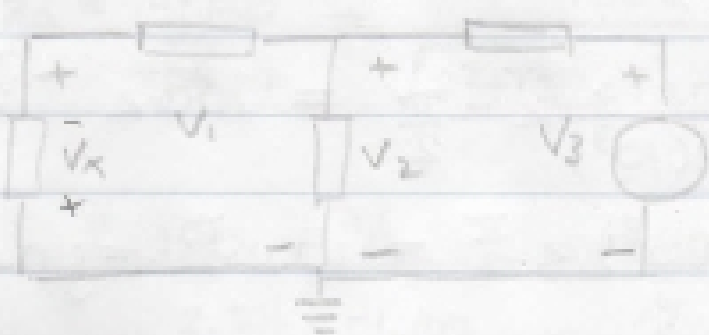

$$V_1 = 20 \angle 30^\circ, V_2 = 10 \angle 30^\circ, V_3 = 5 \angle 120^\circ$$

$$V_x + V_1 + V_2 = 0$$

KVL:

$$V_x + V_1 = 0 \rightarrow V_x = -V_1$$


$$V_x = 20 \angle 150^\circ$$

Impedance (z):

• Resistor  $\rightarrow R \angle 0^\circ$

Ex.

Find  $i_1$

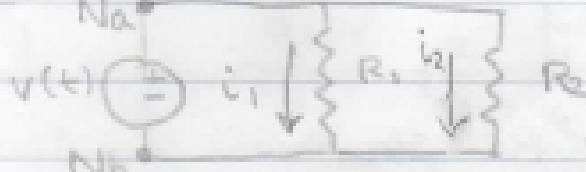

$$R_1 = R_2 = 100 \Omega$$

$$v(t) = 30 \cos(10t + \frac{\pi}{2}) \text{ V}$$

$$V(j\omega) = 30 \angle 90^\circ \text{ V}$$

$$I_1(j\omega) = \frac{V(j\omega)}{Z(j\omega)} = \frac{30 \angle 90^\circ}{R \angle 0^\circ} = \frac{30 \angle 90^\circ}{100 \angle 0^\circ} = 0.3 \angle 90^\circ \text{ A}$$

$$i_1(t) = 0.3 \cos(10t + \frac{\pi}{2}) \text{ A}$$

• Inductor  $\rightarrow \omega L \angle 90^\circ$


• Capacitor  $\rightarrow \frac{1}{\omega C} \angle -90^\circ$

The impedance equation:  $z = \frac{V}{I} \rightarrow V = ZI$

Summary

	(degrees)	(radians)	(Rectangular)
	Impedance	$Z(j\omega)$ in $\Omega$ Imp.	Imp.
Resistor	$R \angle 0^\circ$	$R \angle 0$	$R$
Inductor	$\omega L \angle 90^\circ$	$\omega L \angle \frac{\pi}{2}$	$j\omega L$
Capacitor	$\frac{1}{\omega C} \angle -90^\circ$	$\frac{1}{\omega C} \angle -\frac{\pi}{2}$	$\frac{-j}{\omega C}$

Ex.

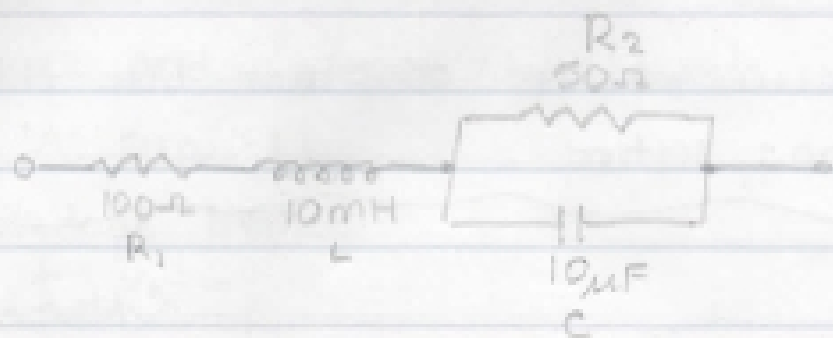

Find impedances!

$$\omega = 2\pi f = 159.15\pi = 1000 \text{ rad/sec}$$


$$Z_{R1} = 100 \angle 0^\circ$$

$$Z_{R2} = 50 \angle 0^\circ$$

$$Z_C = \frac{1}{\omega C} \angle -\frac{\pi}{2} = \frac{1}{(10 \times 10^{-6})(10^3)} \angle -\frac{\pi}{2} = 100 \angle -\frac{\pi}{2} = -j100 \Omega$$

$$Z_L = \omega L \angle \frac{\pi}{2} = (10 \times 10^{-3})(10^3) \angle \frac{\pi}{2} = 10 \angle \frac{\pi}{2} = j10 \Omega$$

Ex.

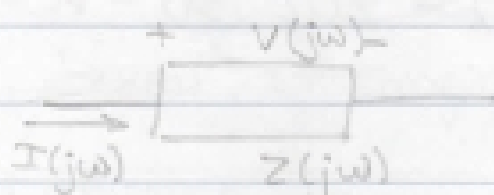

Given:  $V = 0.1 \angle 0^\circ \text{ V}$

Find Current:

- If  $Z = 100 \angle 0^\circ$

$$I = \frac{V}{Z} = \frac{0.1 \angle 0^\circ}{100 \angle 0^\circ} = 1 \angle 0^\circ \text{ mA} \rightarrow \text{Resistor}$$

- If  $Z = 10 \angle \frac{\pi}{2}$

$$I = \frac{0.1 \angle 0^\circ}{10 \angle \frac{\pi}{2}} = 10 \angle -\frac{\pi}{2} \text{ mA} \rightarrow \text{Inductor}$$

- If  $Z = 100 \angle -\frac{\pi}{2}$

$$I = \frac{0.1 \angle 0^\circ}{100 \angle -\frac{\pi}{2}} = 1 \angle \frac{\pi}{2} \text{ mA} \rightarrow \text{Capacitor}$$

\* Combining Impedance

- Series  $\rightarrow Z_{eq} = Z_1 + Z_2$


- Parallel  $\rightarrow Z_{eq} = \left( \frac{1}{Z_1} + \frac{1}{Z_2} \right)^{-1}$

Ex.



$$Z = Z_1 + Z_2$$
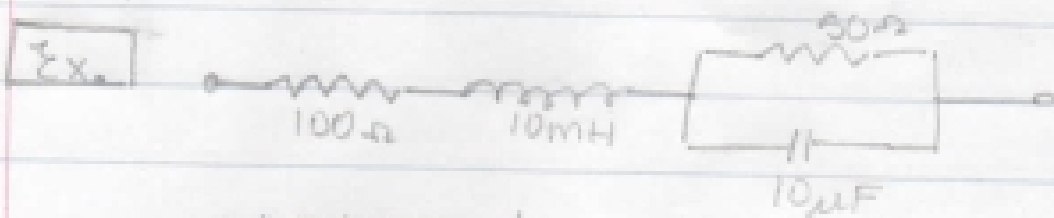
$$= \omega L \angle \frac{\pi}{2} + \frac{1}{\omega C} \angle -\frac{\pi}{2}$$



$$\omega = 1000 \text{ rad/s}$$

$$\frac{1}{Z_a} = \frac{1}{50} + \frac{1}{-j100} = \frac{-j2+1}{-j100}$$


$$Z_a = \frac{-j100}{-j2+1} = \frac{100 \angle -\pi/2}{\sqrt{2^2+1^2} \angle \tan^{-1}(-2)}$$

$$= \frac{100 \angle -\pi/2}{2.24 \angle -1.107} = \boxed{40 - j20 \Omega}$$

### \* Node Voltage Method

- Transform phasors + impedance

- Follow NVM from earlier in semester

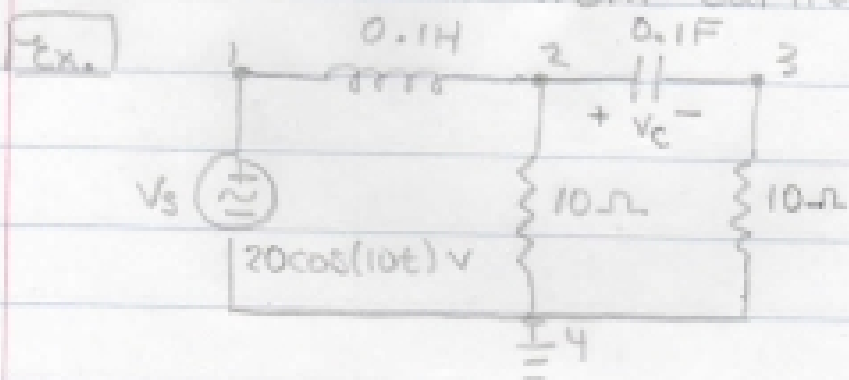

$$j\omega L = j1 \Omega$$

$$-j/\omega C = -\frac{j}{1} = -j \Omega^{-1}$$

$$V_s = 20 \angle 0^\circ \text{ V}$$

$$\omega = 10 \text{ rad/s}$$

$$m=1, n=4$$

$$\text{Out of node 2: } I_n = \frac{V_2 - V_1}{j1 \Omega} + \frac{V_2}{10 \Omega} + \frac{V_2 - V_3}{-j \Omega} = 0$$

$$\text{" " " 1: } I_n = \frac{V_3 - V_2}{-j \Omega} + \frac{V_3}{10 \Omega} = 0$$