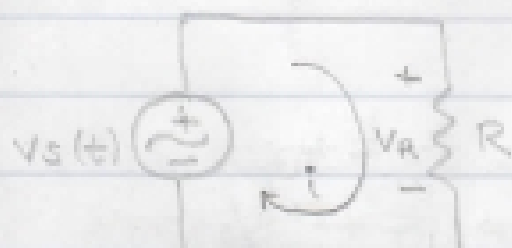


* Resistor in an AC Circuit



$$v_s(t) = V_{max} \cos(\omega t)$$


Using KVL:

$$\sum v = -v_s + iR = 0$$

$$i = \frac{v_s}{R} = \frac{V_{max}}{R} \cos(\omega t)$$

* v and i have same frequencies and phase angles, but different magnitudes

* Inductor in an AC Circuit

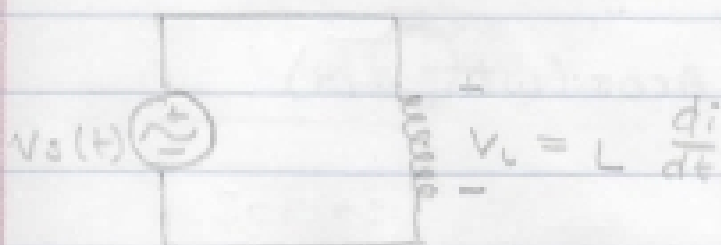

$$v_s(t) = V_{max} \cos(\omega t)$$

$$\text{KVL: } -v_s + L \frac{di}{dt} = 0$$


$$i = \frac{V_{max}}{\omega L} \cos(\omega t - \pi/2)$$

HW - Chapter #4

March 23, 2015

37, 38, 39, 43, 47, 54, 55, 69, 74, 82, 71, 73, 81

* Capacitor in an AC Circuit

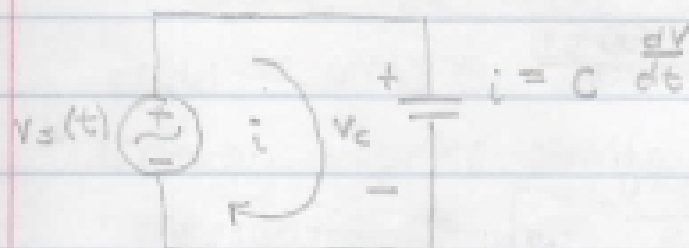

$$v_s(t) = V_{max} \cos(\omega t)$$

$$i = C \omega V_{max} \cos(\omega t + \pi/2)$$

$$I_{rms} = \frac{I_{max}}{\sqrt{2}}$$

* Average Value



$$i(t) = I_m \sin \omega t$$


$$\omega t = 0$$

$$I_{AV} = \frac{1}{T} \int_0^T i dt = \frac{1}{\pi} \int_0^{\pi} i dt = \frac{1}{\pi} \int_0^{\pi} I_m \sin \theta d\theta$$

$$= \frac{I_m}{\pi} \left[-\cos \theta \right]_0^{\pi}$$

$$= \frac{I_m}{\pi} [1 + 1]$$

$$= \frac{2}{\pi} I_m$$

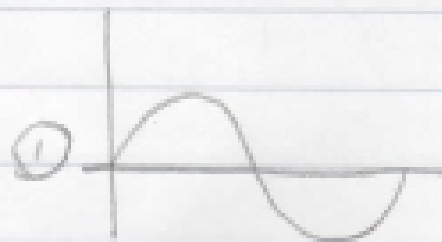


$$\frac{I_{AV}}{I_m} = \frac{2}{\pi}$$

$$\frac{I_{rms} (eff)}{I_m} = \frac{1}{\sqrt{2}}$$




$$\frac{I_{AV}}{I_m} = \frac{2}{\pi}$$
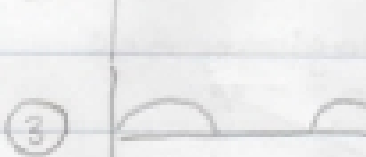
$$\frac{I_{rms} (eff)}{I_m} = \frac{1}{\sqrt{2}}$$




$$\frac{I_{AV}}{I_m} = \frac{1}{\pi}$$
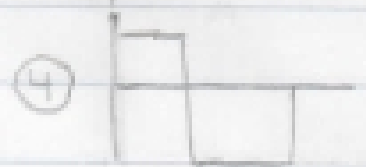
$$\frac{I_{rms} (eff)}{I_m} = \frac{2}{\sqrt{2}}$$



$$\frac{I_{AV}}{I_m} = I_m$$

$$\frac{I_{rms} (eff)}{I_m} = I_m$$

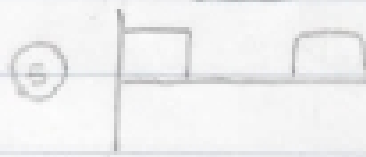

$$\frac{I_{AV}}{I_m} = \frac{I_m}{2}$$

$$\frac{I_{rms} (eff)}{I_m} = \frac{1}{\sqrt{2}}$$




$$\frac{I_{AV}}{I_m} = \frac{1}{2}$$

$$\frac{I_{rms} (eff)}{I_m} = \frac{1}{\sqrt{3}}$$



$$\frac{I_{AV}}{I_m} = \frac{1}{2}$$
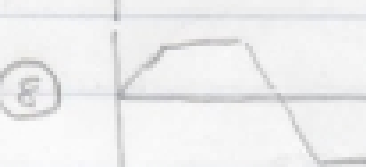
$$\frac{I_{rms} (eff)}{I_m} = \frac{1}{\sqrt{3}}$$



$$\frac{I_{AV}}{I_m} = \frac{1}{2}$$

$$\frac{I_{rms} (eff)}{I_m} = \frac{1}{\sqrt{3}}$$


° The Form Factor, $K_f = \frac{I_{rms}}{I_{AV}} = \frac{1/\sqrt{2}}{2/\pi} \approx 1.109$

° The Crest Factor, $C = \frac{I_m}{I_{rms}} = \frac{I_m}{I_m/\sqrt{2}} = \sqrt{2} = 1.414$

* Phasors and Complex Numbers

Solving AC Circuits:

- Node Voltage Method

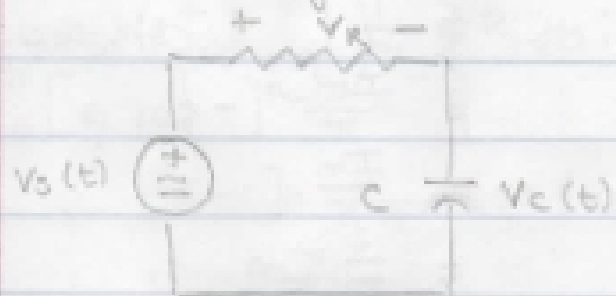

* Complex Numbers

$\sqrt{-1} = i = j$ → used instead of i

$x = A \pm jB$ → Rectangular Form
↳ Real ↳ Imaginary

$$C = \sqrt{A^2 + B^2}$$

$$\theta = \tan^{-1}(B/A)$$

$x = C e^{j\theta} = C \angle \theta$ → Polar Form

$$-180^\circ < \theta < 180^\circ \text{ or } -\pi < \theta < \pi$$

$x = C \cos \theta + jC \sin \theta$ → Back to rectangular form

Ex. $i = 10 + j20$

$$i = \sqrt{10^2 + 20^2} \angle \tan^{-1}(20/10)$$

$$= 22.36 \angle 63.4^\circ$$

Ex. $i = 10 \angle 5^\circ$

$$i = 10 \cos(5^\circ) + j10 \sin(5^\circ)$$

$$= 9.96 + j0.87$$

* can add, subtract, multiply, and divide complex numbers

* Complex Conjugate

- Reflect about the real axis

- change sign of angle/imaginary form

