

Combinational Logic (mostly review!)

- Logic functions, truth tables, and switches
 - NOT, AND, OR, NAND, NOR, XOR, . . .
 - Minimal set
- Axioms and theorems of Boolean algebra
 - Proofs by re-writing
 - Proofs by perfect induction
- Gate logic
 - Networks of Boolean functions
 - Time behavior
- Canonical forms
 - Two-level
 - Incompletely specified functions
- Two-level minimization

Possible Logic Functions of Two Variables

16 possible functions of 2 input variables:

$2^{(2^n)}$ functions of n inputs



		16 possible functions (F0-F15)																
X	Y	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1
0	0	0	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1
0	1	0	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0

Labels for the 16 functions (F0-F15) from left to right:

 0, X and Y, X, Y, X xor Y, X or Y, X = Y, X nor Y, not (X or Y), not Y, not X, X nand Y, not (X and Y), 1

Cost of Different Logic Functions

□ Some are easier, others harder, to implement

- Each has a cost associated with the number of switches needed
- 0 (F0) and 1 (F15): require 0 switches, directly connect output to low/high
- X (F3) and Y (F5): require 0 switches, output is one of inputs
- X' (F12) and Y' (F10): require 2 switches for "inverter" or NOT-gate
- X nor Y (F4) and X nand Y (F14): require 4 switches
- X or Y (F7) and X and Y (F1): require 6 switches
- $X = Y$ (F9) and $X \oplus Y$ (F6): require 16 switches

- Because NOT, NOR, and NAND are the cheapest they are the functions we implement the most in practice