

7/7/2014

8.4

HW Problem

$$v_1(t) = 4 \sin(377t + 25^\circ) \text{ V}$$

$$i_1(t) = 0.05 \cos(377t - 20^\circ) \text{ A}$$

$$v_2(t) = -0.1 \sin(377t + 45^\circ) \text{ A}$$

$$v_1(t) = 4 \cos(377t - 65^\circ) \text{ V}$$

$$i_1(t) = 0.05 \cos(377t - 20^\circ) \text{ A}$$

$$i_2(t) = 0.1 \cos(377t + 135^\circ) \text{ A}$$

$$v_1(t) \text{ leads } i_1(t) \text{ by } \phi_1 - \phi_2 = -65 - (-20) = -45^\circ$$


so i_1 leads v_1 by 45°

$$v_1(t) \text{ leads } i_2(t) \text{ by } \phi_1 - \phi_2 = -65 - 135 = -200^\circ$$


so i_2 leads v_1 by 200°

Resistor:


Time domain:

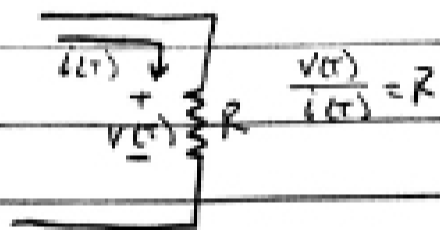


Phasor domain:

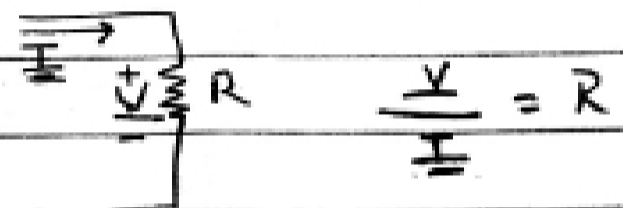


Inductor:

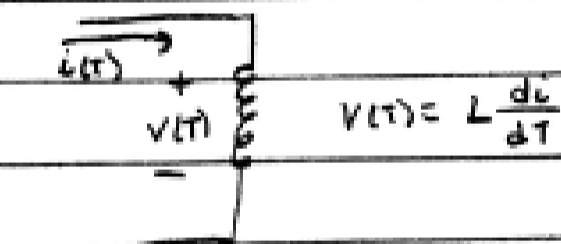

Impedance

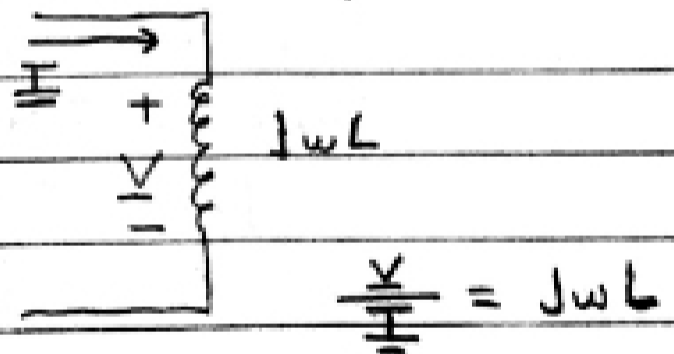

Capacitor:

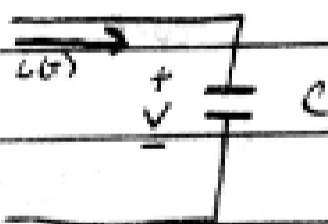

$$i(t) = C \frac{dv}{dt}$$



$$\frac{V}{I} = -j/\omega C$$

A. Impedance

1. The "resistance" of a network with R, L and C components
- HAS units of ohms (Ω)

2. Define as a ratio

$$\text{Impedance } \underline{Z} = \frac{V}{I} = \frac{V_m \angle \phi}{I_m \angle \theta}$$

3. $\underline{Z} = |Z| \angle \theta_z$

$$|Z| = \frac{V_m}{I_m}$$

$$\theta_z = \frac{\angle \phi}{\angle \theta} = \angle \phi - \theta$$

4. No Time domain correspondance

i.e. no $|Z| \cos(\omega t + \theta_z)$

5. Rectangular form of \underline{Z}

$$\underline{Z} = R + jX$$

Resistance
(Real)

Reactance
(Imaginary)

6. Converting to Polar form

$$|Z| = \sqrt{R^2 + X^2}$$


$$\theta_z = \tan^{-1} \frac{X}{R}$$

7. Converting to Rectangular

$$R = |Z| \cos \theta_z$$

$$X = |Z| \sin \theta_z$$

Impedance Triangle

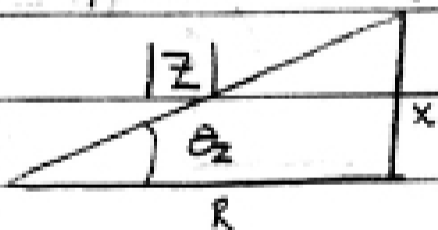

Example: The Terminal Voltage and current of a circuit are:


$$\underline{V} = 10 \angle 56.1^\circ \text{ V}$$

$$\underline{I} = 2 \angle 20^\circ \text{ A}$$

$$\therefore \underline{Z} = \frac{\underline{V}}{\underline{I}} = \frac{10 \angle 56.1^\circ}{2 \angle 20^\circ} = 5 \angle 36.1^\circ \Omega$$

$$R = 5 \cos(36.1^\circ) = 4$$
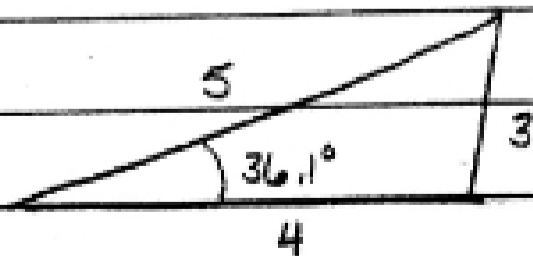
$$X = 5 \sin(36.1^\circ) = 3 \quad \therefore \underline{Z} = 4 + 3j \Omega$$



9. Reactance, X

$$\frac{V_L}{I_L} = j\omega L = jX_L \quad X_L = \omega L$$

↗ Inductive reactance

$$\frac{V_C}{I_C} = -j\frac{1}{\omega C} = -jX_C \quad X_C = \frac{1}{\omega C}$$

↗ Capacitive reactance

$$Z = R + j(X_L + X_C)$$

$$\frac{1}{R} = G \text{ Conductance}$$

$$= R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$\frac{1}{Z} = Y \text{ admittance}$$

$$Y = |Y| \angle \theta_Y$$

$$Z = R + jX$$

$$Y = G + jB$$

conductance susceptance (reciprocal of Reactance)

$$Z = R + jX$$


$$\frac{1}{Z} = \frac{1}{R + jX} \cdot \frac{R - jX}{R - jX} = \frac{R - jX}{R^2 + X^2} = \frac{R}{R^2 + X^2} - j\frac{X}{R^2 + X^2}$$

$$Y = G + jB$$

$$G = \frac{R}{R^2 + X^2}$$


$$B = \frac{-X}{R^2 + X^2}$$

Example

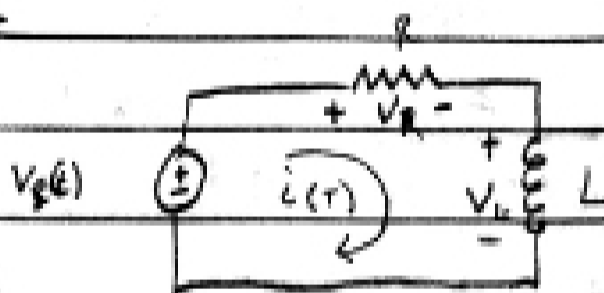

$$v_s(t) = V_m \cos(\omega t + \phi)$$

$$v_s(t) = v_R(t) + v_L(t)$$

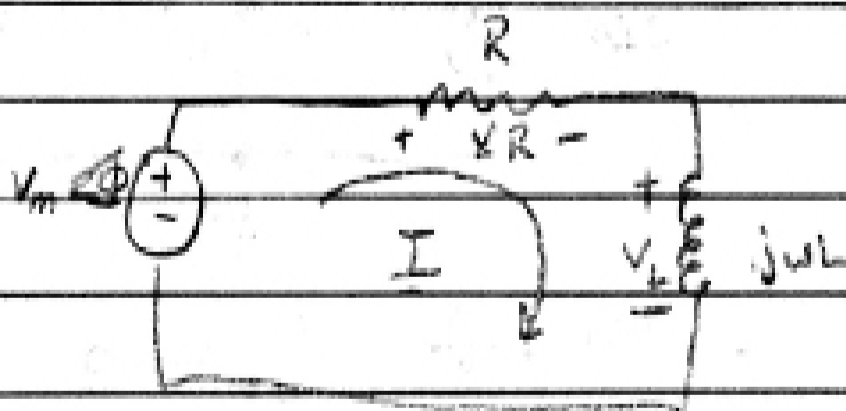

Find I

$$V_m \angle \phi = RI + j\omega L I$$

$$I [R + j\omega L] = V_m \angle \phi$$

$$I = \frac{V_m \angle \phi}{R + j\omega L}$$

$$I = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \angle \phi - \theta$$

$$= \frac{V_m \angle \phi}{\sqrt{R^2 + \omega^2 L^2}} \angle \theta$$

$$i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

$$\theta = \tan^{-1}\left(\frac{\omega L}{R}\right)$$