


Physics 202, Lecture 18

Today's Topics

- Reminder
 - RL Circuits
 - RC Circuits
 - LC (RLC) Circuits and Electromagnetic Oscillations
- AC Circuits with AC Source
 - Phasors

Turn on RL Circuit (reminder)


$$I = \frac{V_0}{R} (1 - e^{-t/L/R})$$

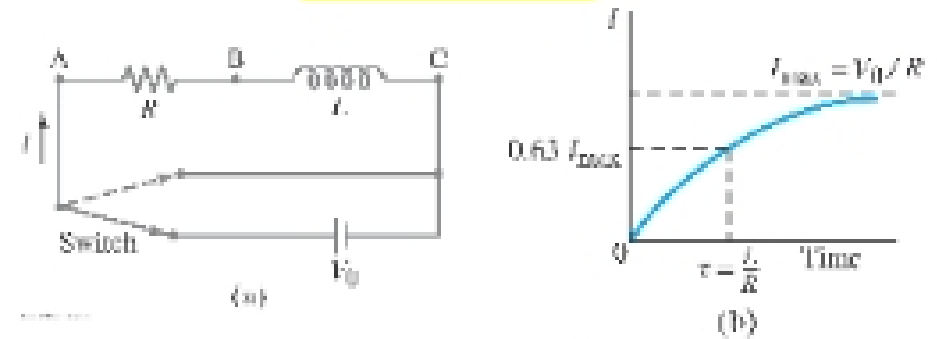

Note: the time constant is $\tau=L/R$


Turn off RL Circuit (reminder)

$$I = I_0 e^{-t/L/R}$$

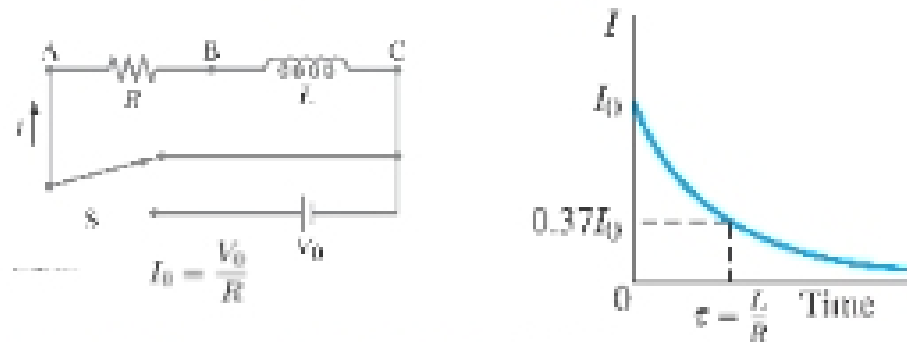

Note: the time constant is $\tau=L/R$

Charging a Capacitor in RC Circuit

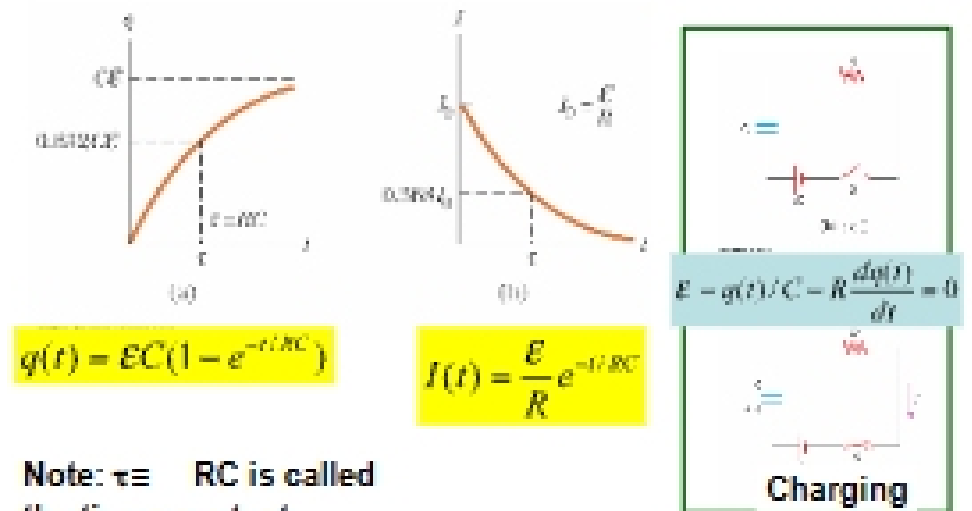

$$q(t) = EC(1 - e^{-t/RC})$$

$$I(t) = \frac{E}{R} e^{-t/RC}$$


Note: $\tau \equiv RC$ is called the time constant

Discharging a Capacitor in RC Circuit

$$q(t) = Qe^{-t/RC}$$

$$I(t) = -\frac{Q}{RC}e^{-t/RC}$$

Note the time constant $\tau=RC$

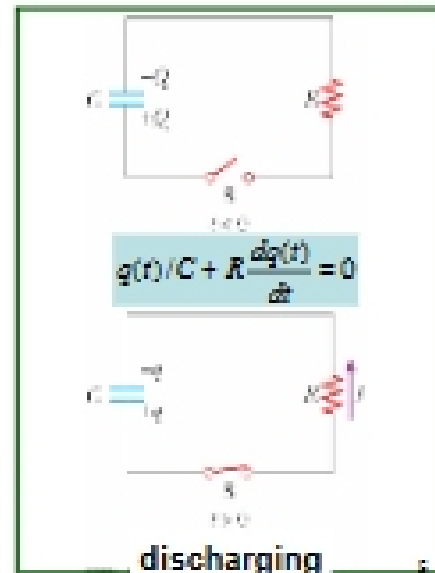

LC Circuit and Oscillation

□ Exercise: Find the oscillation frequency of a LC circuit

$$\rightarrow -q(t)/C - L \frac{dI(t)}{dt} = 0$$


$$\rightarrow q(t)/C + L \frac{d^2q(t)}{dt^2} = 0$$

$$q(t) + \frac{1}{\omega_0^2} \frac{d^2q(t)}{dt^2} = 0$$

$$\rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$$q = Q_{\max} \cos(\omega_0 t + \varphi)$$
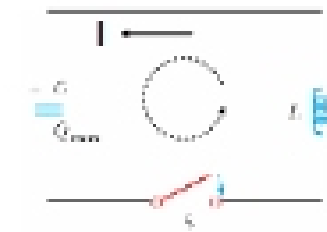
$$I = -\omega_0 Q_{\max} \sin(\omega_0 t + \varphi)$$



eq. of Harmonic Oscillation

Total Energy is conserved

Show that energy is conserved in LR circuit:


$$\begin{aligned} E &= \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} LI^2 \\ &= \frac{1}{2C} Q_0^2 \cos^2(\omega_0 t + \varphi) + \frac{1}{2} L [-\omega_0 Q_0 \sin(\omega_0 t + \varphi)]^2 \\ &= \frac{Q_0^2}{2C} \cos^2(\omega_0 t + \varphi) + \frac{1}{2} \omega_0^2 L Q_0^2 \sin^2(\omega_0 t + \varphi) \end{aligned}$$

Now use $\omega_0 = 1/\sqrt{LC}$

$$\begin{aligned} E &= \frac{Q_0^2}{2C} \cos^2(\omega_0 t + \varphi) + \frac{1}{2LC} L Q_0^2 \sin^2(\omega_0 t + \varphi) \\ &= \frac{Q_0^2}{2C} [\cos^2(\omega_0 t + \varphi) + \sin^2(\omega_0 t + \varphi)] \\ &= \frac{Q_0^2}{2C} \quad \text{independent of time} \end{aligned}$$


AC Power Source
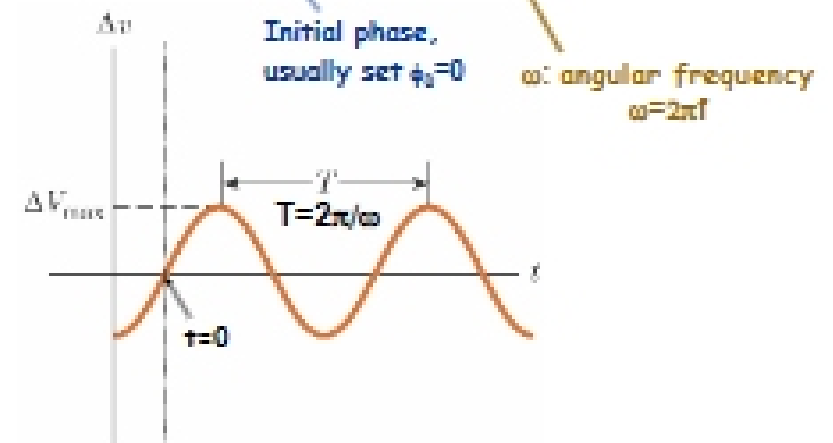
$$\square \Delta V = \Delta V_{\max} \sin(\omega t + \phi_0) = \Delta V_{\max} \sin(\omega t)$$



AC Circuit

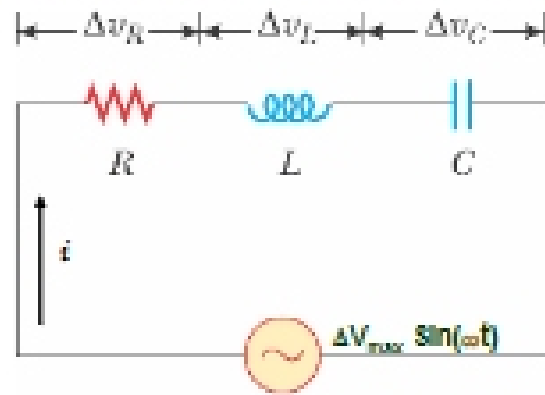□ Find out current i and voltage difference ΔV_R , ΔV_L , ΔV_C .




Notes:

- Kirchhoff's rules still apply !
- A technique called phasor analysis is convenient.


Phasor

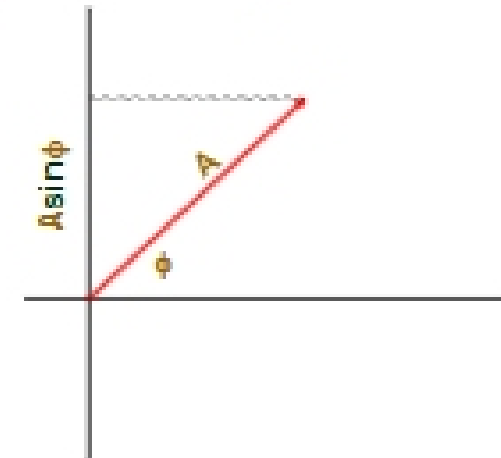□ A sinusoidal function $y = A \sin \phi$ can be represented graphically as a **phasor vector** with length A and angle ϕ (w.r.t. to horizontal)





Resistors in an AC Circuit

□ Ohm's Law: $\Delta V = IR$ at any time

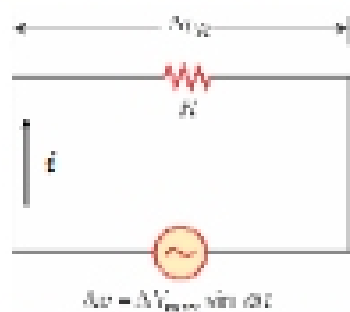


$$i_{\text{eff}} = \Delta V / R = i_{\text{max}} \sin \omega t, \quad i_{\text{max}} = \Delta V_{\text{max}} / R$$

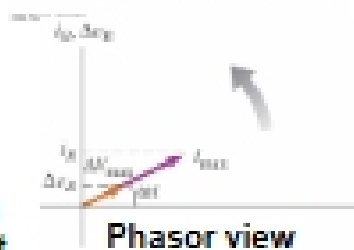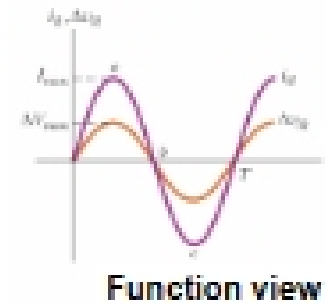→ The current through an resistor is **in phase** with the voltage across it



Inductors in an AC Circuit

□ $\Delta V - L di/dt = 0$

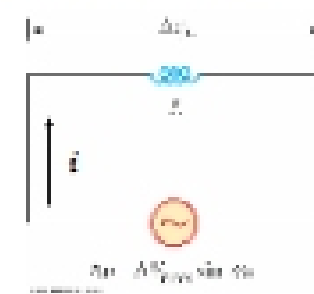

$$\rightarrow i_L = i_{\text{max}} \sin(\omega t - \pi/2)$$

$$i_{\text{max}} = \Delta V_{\text{max}} / X_L$$

$X_L = \omega L \rightarrow$ inductive reactance

→ The current through an inductor is **90° behind** the voltage across it.

