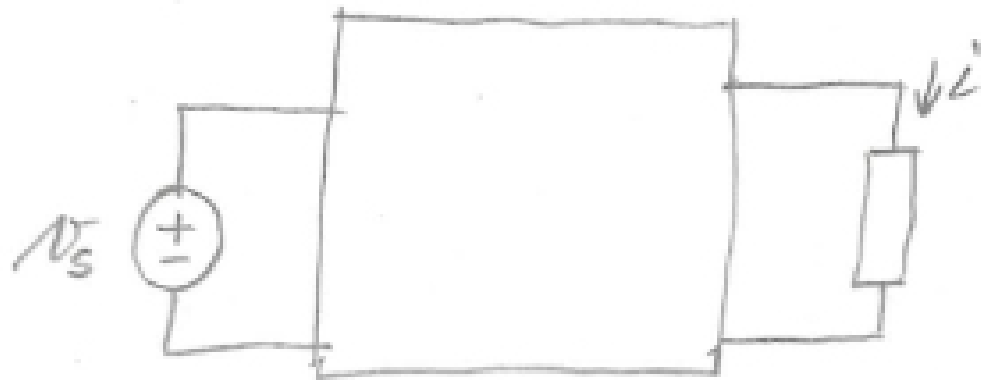


A. A linear circuit must satisfy two properties

1. The homogeneity property (<sup>scaling</sup> proportionality)
2. The additive property (superposition)

B. Homogeneity


1. If the input (excitation) of a circuit is multiplied by a constant
2. Then the output (response) of the circuit is multiplied by the same constant.



a) If  $v_s$  produces  $i$

b) Then  $k v_s$  produces  $k i$

c) Example

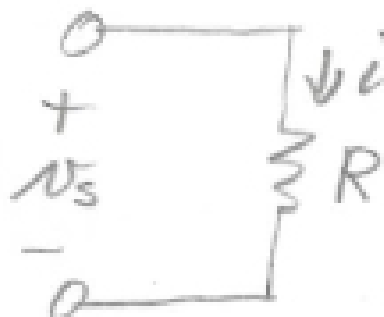

$$i = \frac{v_s}{R} = \frac{1}{R} v_s$$

$$k i = \frac{k v_s}{R}$$

C, Additive property

1. The response to a sum of inputs is the same as the sum of the responses due to the individual inputs.

a) For  $N_1$ :

$$\text{Let } i_1 = \frac{N_1}{R}$$

b) For  $N_2$ :

$$\text{Let } i_2 = \frac{N_2}{R}$$


c) Then for  $N_1 + N_2$

$$i = \frac{N_1 + N_2}{R} = \frac{N_1}{R} + \frac{N_2}{R} = i_1 + i_2$$

## G. Superposition


1. The complete response is the summation of the responses due to the individual independent sources.

2. Example:

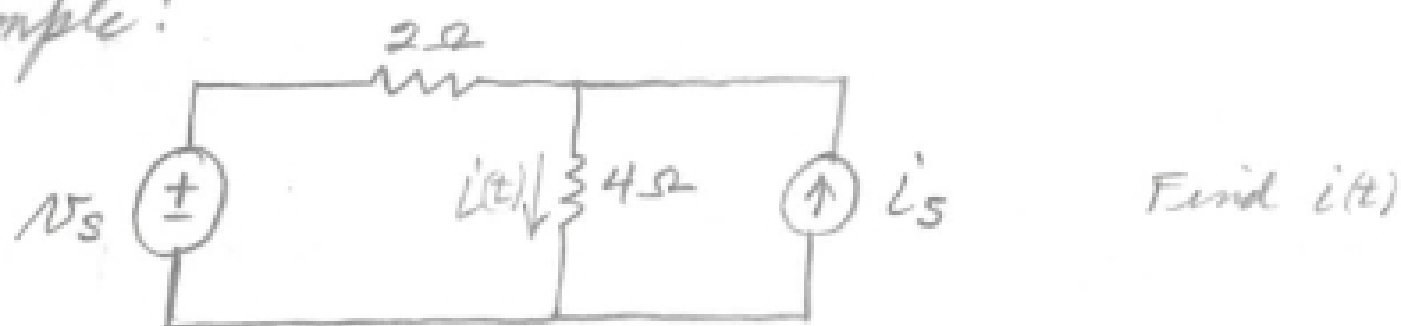

a) Open current source

$$a) \therefore i_s = 0$$

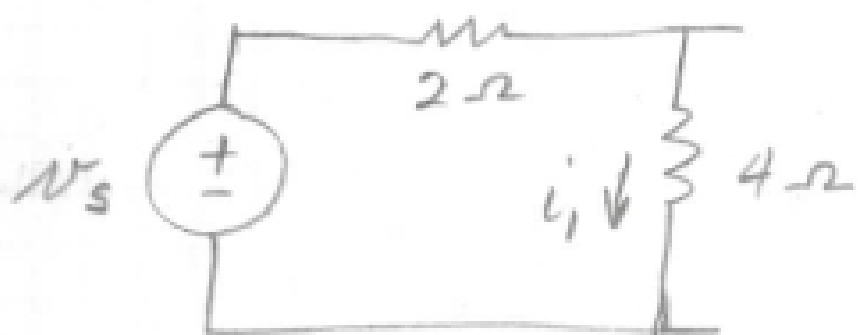


$$-V_s + 2i_1 + 4i_1 = 0$$

$$6i_1 = V_s$$

$$i_1 = \frac{V_s}{6}$$

b) Eliminate voltage source

a) 0 V is a short circuit

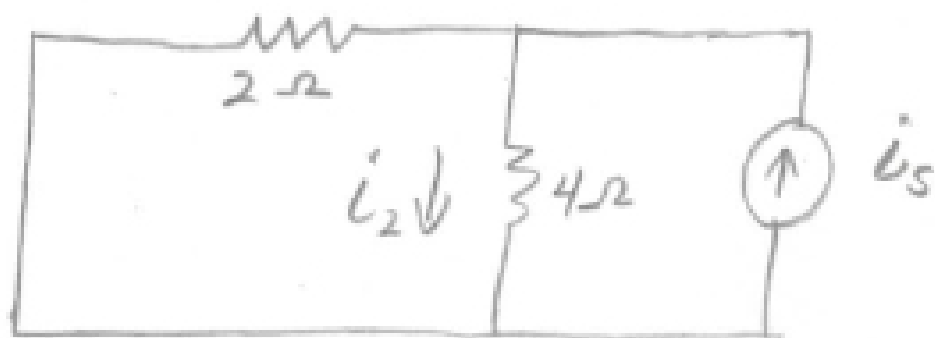

Current division:

$$i_2 = i_s \left( \frac{2}{2+4} \right)$$

$$= \frac{i_s}{3}$$

c) But  $i = i_1 + i_2$

$$\therefore i = \frac{V_s}{6} + \frac{i_s}{3}$$