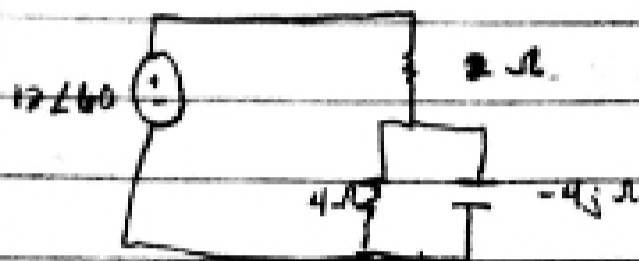


$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$P_{\text{resistor}} = \frac{V_m I_m}{2} = \frac{V_m^2}{2R} = \frac{I_m^2 R}{2}$$

Ex



Find average power absorbed by each resistor

for the 2Ω resistor

$$Z = 2 + (4 \parallel -j4)$$

$$Z = \frac{4(-j4)}{4-j4} \rightarrow Z = \frac{-j4}{1-j} = 2\angle 0^\circ + \frac{4\angle 90^\circ}{\sqrt{2}\angle 45^\circ}$$

$$Z = 2\sqrt{2}\angle 45^\circ$$

$$I = \frac{12\angle 60^\circ}{4-j4} = \frac{3\angle 60^\circ}{1-j} = 2.68\angle 86.6^\circ$$

$$P = \frac{I_m^2 R}{2} = \frac{(6.09)^2 \cdot 2}{2} = 7.2\text{W}$$

4Ω Resistor

Current division

$$I = \left[\frac{-j4}{4-j4} \right] (2.68\angle 86.6^\circ) = \frac{1\angle -90^\circ (2.68\angle 86.6^\circ)}{\sqrt{2}\angle -45^\circ} = 1.9\angle 41.6^\circ \text{ A}$$

$$P = \frac{(1.9)^2 \cdot 4}{2} = 7.21\text{W}$$

$$2.68\angle 86.6^\circ - 1.9\angle 41.6^\circ = 0.78\angle 45^\circ$$

$$(0.159 - j2.6751) - (1.42 + j1.26) = I_c = -1.26 + j1.242 \text{ A}$$

$$I_m = 1.9\angle 131.57^\circ \quad V_c = (1.9\angle 131.57^\circ)(4\angle -90^\circ) = 7.6\angle 41.57^\circ$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = \frac{(7.6)(1.9)}{2} \cos(41.57^\circ - 131.57^\circ)$$

short cut

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

RMS voltage or RMS current


or effective voltage or effective current

The effective value of a periodic current is equal to the DC current that delivers the same average power to a resistor as the periodic current does.


similar definition as current for voltage

2

set up in comparison

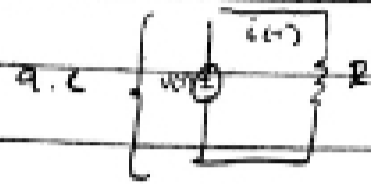
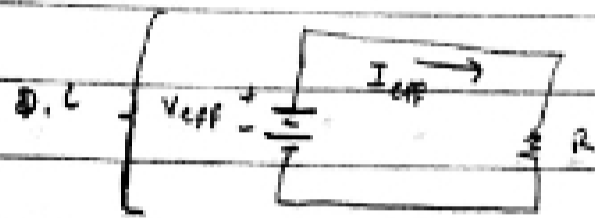
$$P = \frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) R dt$$



$$P = I_{eff}^2 R$$

$$I_{eff}^2 R = \frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) R dt \rightarrow I_{eff}^2 R = \frac{R}{T} \int_{t_0}^{t_0+T} i^2(t) dt$$

$$\sqrt{I_{eff}^2} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) dt}$$

$$I_{eff} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) dt}$$

RMS

$$i(t) = I_m \cos(\omega t + \theta_i)$$

$$i^2(t) = I_m^2 \cos^2(\omega t + \theta_i)$$

$$I_{eff} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} I_m^2 \cos^2(\omega t + \theta_i) dt}$$

$$\cos^2 = \frac{1}{2} (1 + \cos(2\omega t + 2\theta_i))$$

$$\left(\frac{I_m^2}{2T} \int_{t_0}^{t_0+T} dt + \int_{t_0}^{t_0+T} \cos(2\omega t + 2\theta_i) dt \right)^{1/2}$$

$$I_{eff} = \sqrt{\frac{I_m^2}{2T} (T) \Big|_{t_0}^{t_0+T}}$$

$$= \sqrt{\frac{I_m^2}{2}} = \frac{I_m}{\sqrt{2}} = I_{eff}$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i)$$

$$= V_{eff} I_{eff} \cos(\theta_v - \theta_i)$$

$$\frac{V_m}{\sqrt{2}} = V_{eff}$$

$$v(t) = \sqrt{2} V_{eff} \cos(\omega t + \theta_v)$$


Complex Power

A. Definition $S = \text{Complex Power}$

$$S = P + jQ$$

- S is the Complex Power, Units V.A Volt ampere
- P is the average (Real) Power, Units watts
- Q is Reactive Power, Units Volt ampere R or VAR
- $|S|$ is apparent power, V.A.

2. Power Triangle

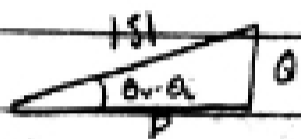

$$|S| = \sqrt{P^2 + Q^2} \quad (\theta_v - \theta_i) = \tan^{-1} \frac{Q}{P}$$

a) $(\theta_v - \theta_i)$ is power factor angle

$$\text{b) Power Factor, } PF = \cos(\theta_v - \theta_i) = \frac{P}{|S|}$$

Power Factor angle is angle by which the current leads the voltage

$$\cos(\theta_v - \theta_i) = \cos(-(\theta_v - \theta_i))$$

$$\theta_v - \theta_i = 26.6^\circ$$


$$\cos(26.6) = 0.894$$

$$\cos(-26.6) = 0.894$$

leading and lagging

ELI the ICE man
 ↑ ↑
 Lagging leading

Impedance Triangle

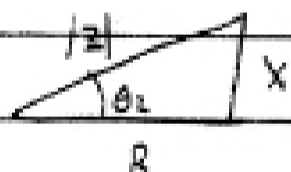

$$Z = R + jX$$

$$Z = \frac{V_m \angle \theta_v}{I_m \angle \theta_i} = \frac{V_m}{I_m} \angle \theta_v - \theta_i$$

B. Power Calculations

1. We know that:

$$\text{a) } P = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

$$\text{b) } Q = V_{rms} I_{rms} \sin(\theta_v - \theta_i)$$

2. We can write

$$S = P + jQ$$

$$= V_{rms} I_{rms} \cos(\theta_v - \theta_i) + j V_{rms} I_{rms} \sin(\theta_v - \theta_i)$$

$$= V_{rms} I_{rms} (\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i))$$

$$= V_{rms} I_{rms} \angle \theta_v - \theta_i$$

$$= V_{rms} \angle \theta_v (I_{rms} \angle -\theta_i)$$

$$\Rightarrow V_{rms} \underline{I}_{rms}^* = S = V_{eff} \underline{I}_{eff}^*$$

$$e^{j\theta} = |e| \angle \theta$$

$$e^{*j\theta} = |e| \angle -\theta$$

* : complex conjugate