

Exam Review

1/3 First Exam

1/3 Second Exam



1/3 New stuff - Chapter 9 - Power Factor correction

Norton Equation

Delta to Y equation will be given

Op - Amps

Non-inverting

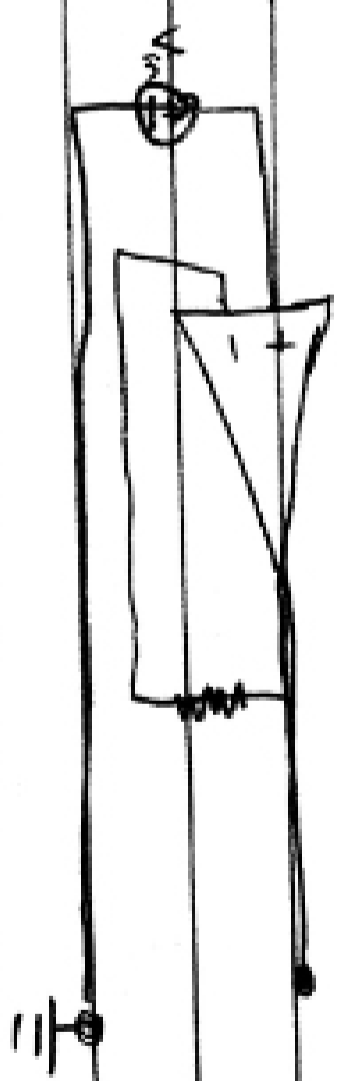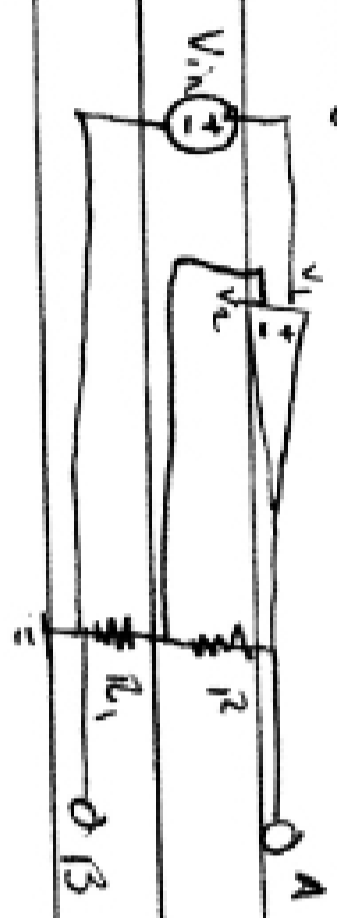

$$R_L < R_{th}$$

$$Z_L = Z_{in}$$

impedance

$$Y = \frac{1}{Z}$$

$$Z = |Z| \angle \theta_z$$

$$Y = |Y| \angle \theta_y$$

$$R + jX$$

$$G + jB = \frac{R - jX}{R^2 + X^2}$$

$$= \frac{R - jX}{R^2 + X^2} = \frac{R}{R^2 + X^2} - j \frac{X}{R^2 + X^2}$$

$$= \underbrace{G}_{\text{conductance}} + j \underbrace{B}_{\text{susptance}}$$

conductance