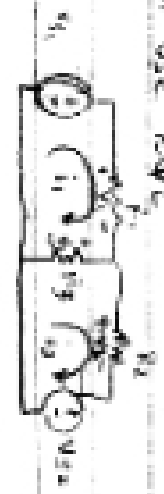


4. Mesh Analysis - Equivalent a voltage source

1. Draw the mesh possible instead of nodes or
2. keep it closed

3. Mark up with the mesh direction

4. Use KVL



$$M_1: -V_1 + V_1 + i_1 R_1 + i_1 R_2 = 0$$

$$i_1: R_1 + R_2$$

$$V_1 - V_2$$


$$M_2: -V_2 + V_2 + i_2 R_3 = 0$$

Use KVL

$$-R_3(i_2) + R_3 i_2 + V_2 = 0$$

$$R_3(i_2 - i_1) + R_3 i_2 + V_2 = 0$$
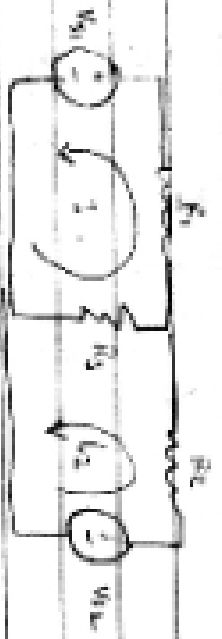
$$\begin{bmatrix} R_1 + R_2 & -R_3 \\ -R_3 & R_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} V_1 - V_2 \\ V_2 \end{bmatrix}$$



$$M_1: -V_1 + V_1 + R_1(i_1) + R_2(i_1 - i_2) + R_3(i_1 - i_2) = 0$$

$$M_2: -V_2 + V_2 + R_3(i_2 - i_1) + R_3 i_2 = 0$$

$$\begin{bmatrix} R_1 + R_2 + R_3 & -R_3 \\ -R_3 & R_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} V_1 - V_2 \\ V_2 \end{bmatrix}$$



$$M_1: -V_1 + V_1 + R_1 i_1 + R_2(i_1 - i_2) + R_3(i_1 - i_2) = 0$$

$$M_2: -V_2 + V_2 + R_3(i_2 - i_1) + R_3 i_2 = 0$$

$$\begin{bmatrix} R_1 + R_2 + R_3 & -R_3 \\ -R_3 & R_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} V_1 - V_2 \\ V_2 \end{bmatrix}$$

Find

Find W

$$i_1 = 6A \quad i_2 = 2A$$

$$P_1: 3i_1 + 3V + 6i_1(i_1 - i_2) = 0$$

$$P_2: 4i_2(i_2 - i_1) + 6i_2(i_2 - i_1) + 2i_2(2 - i_2) = 0$$

$$P_3: 6i_2 - 6i_1 i_2 = -3 \text{ W}$$

$$-6i_1 + 6i_1 i_2 = 8 \rightarrow -9i_2 + 15i_1 = 12 \text{ V}$$

$$9i_2 = 1 \quad i_2 = 1/9 A$$

$$9i_1 - 6(1/9) = 3 \quad 9i_1 = 3 + 2/3 \quad i_1 = 1/3 A$$

$$V = 6i_1(i_1 - i_2) = 6(1/3 - 1/9)$$

$$V = 2 = 1/4 \text{ W}$$

