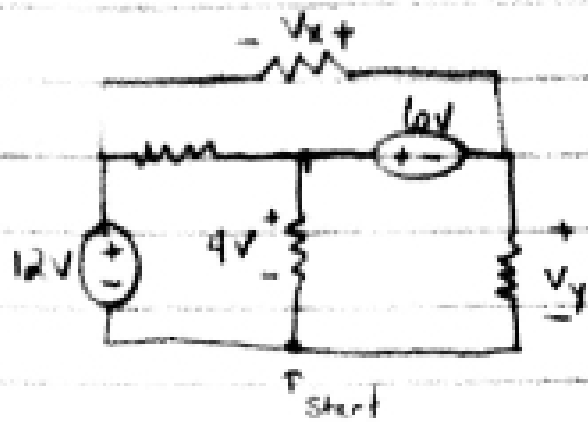


5/28/14

29



$$\text{KVL}_1: -4 + 6 + V_y = 0$$

$$V_y = -2V$$

$$\text{KVL}_2: -12 - V_x + V_y = 0$$

$$-12 - V_x - 2 = 0 \quad V_x = -14V$$

$$V_x = -14V \quad V_y = -2V$$


Resistors in series carry the same current and Different Voltages
 Resistors in Parallel carry the same voltage and Different Currents

F. Delta to Y transformation



1. Delta - (or P.) network




Rearranged

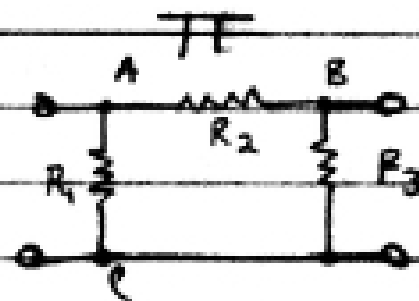

2. Y (Wye) - Tee Network

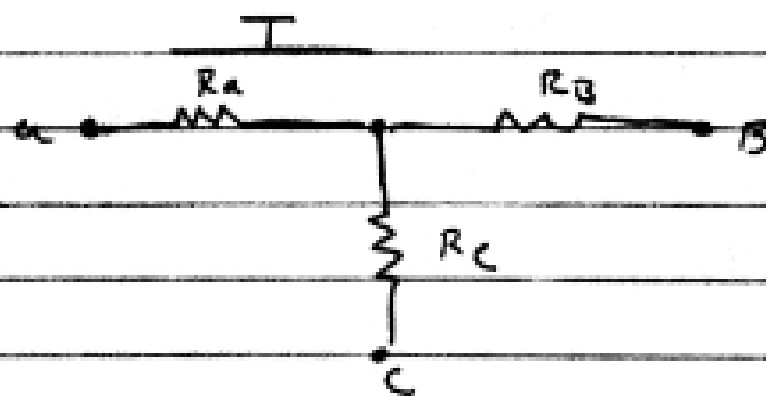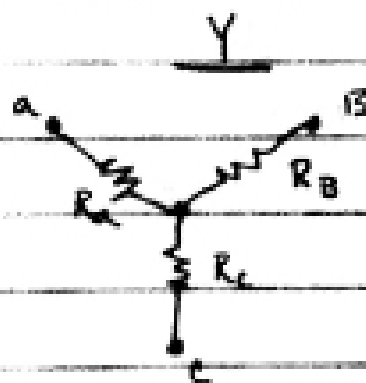

3. Delta-Y

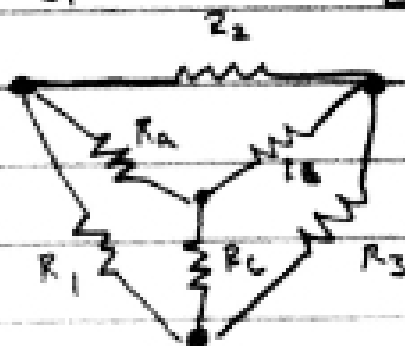

$$R_{ac} = R_1 \parallel (R_2 + R_3) = R_a + R_c$$

$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$


$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

Chapter 3

A. Basic Nodal Analysis

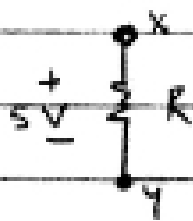1. Use KCL
2. Determine node voltages
3. Voltage - potential between two points




Y as reference - Point X is 5V more Positive than Point Y

X as ref - Point Y is 5V more Negative than Point X

4. $\frac{1}{R} = \text{Reference}$

$I = i$

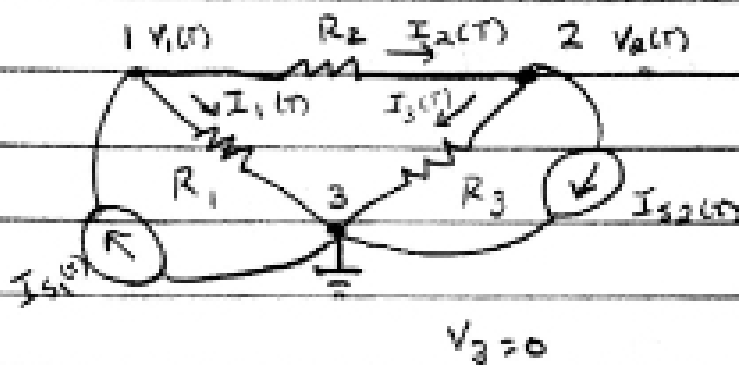

@ 1: $\pm = i$ going out

$$-I_{s1}(t) + I_1(t) + I_2(t) = 0$$

$$I_1(t) = \frac{V_1 - V_3}{R_1} = \frac{V_1}{R_1}$$

$$I_2(t) = \frac{V_1 - V_2}{R_2}$$

$$\textcircled{1} \quad -I_{s1}(t) + \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} = 0$$

@ 2: $-I_2(t) + I_3(t) + I_{s2}(t) = 0$

$$I_3(t) = \frac{V_2(t) - V_3(t)}{R_3} = \frac{V_2(t)}{R_3}$$

2 Equations 2 unknowns

$$-\left(\frac{V_1 - V_2}{R_2}\right) + \frac{V_2}{R_3} + I_{s2}(t) = 0$$

$$\textcircled{2} \quad \frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3} + I_{s2}(t) = 0$$

$$\frac{V_1}{R_1} + \frac{V_1}{R_2} - \frac{V_2}{R_2} = I_{s1}(t)$$

$$\frac{V_2}{R_2} - \frac{V_1}{R_2} + \frac{V_2}{R_3} = -I_{s2}(t)$$

A Matrix

B Matrix

= C Matrix

$$\begin{bmatrix} \left(\frac{1}{R_1} + \frac{1}{R_2}\right) & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \left(\frac{1}{R_2} + \frac{1}{R_3}\right) \end{bmatrix} \begin{bmatrix} V_1(t) \\ V_2(t) \end{bmatrix} = \begin{bmatrix} I_{s1}(t) \\ -I_{s2}(t) \end{bmatrix}$$

$$A \quad \downarrow \quad B \quad = \quad C$$