

## Lecture 5

### Circuits

Topics: KVL, KCL, Op=Amps, Thevenin equivalents


Lab Exercise: build robot "head"

- Motor servo controller (rotating "neck")
- Phototransistor (robot "eyes")
- Integrate to make a light tracking system

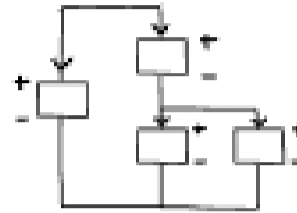
### The Circuit Abstraction

Circuits represent systems as connection of elements

- Through while currents (through variables) flow
- Across while voltages (across variables) develop



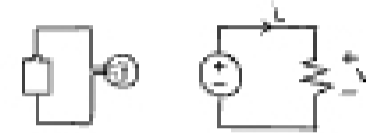We can represent the flashlight as a voltage source, a battery, connected to a resistor, a light bulb  
The voltage source generates a voltage  $v$  across the resistor and a current  $i$  through the resistor



We can represent the flow of water by a circuit

Flow of water into and out of tank are represented as "through variables"  $r$  and  $r'$  respectively

Hydraulic pressure at bottom of tank is represented by the "across variable"  $P = \rho gh$



Circuits are important for two very different reasons:

- As a physical system
  - Power—from generators and transformers to power lines
  - Electronics—from cell phones to computers
- As models of complex systems
  - Neurons
  - Brain
  - Cardiovascular system
  - Hearing

Circuits are the basis of the enormously successful semiconductor industry

Circuits as models of complex systems: myelinated neuron.

The primitives are the elements:

- Sources, capacitors, resistors

The rules of combination are the rules that govern

- Flow of current (through variable)
- Development of voltage



### Analyzing Circuits

We will start with the simplest elements: resistors and sources

Analyzing simple circuits is straightforward

Example 1: The voltage source determines the voltage across the resistor,

$v = 1V$ , so the current through the resistor is  $i = v/R = 1A$

Example 2: The current source determines the current through the resistor,

$i = 1A$ , so the voltage across the resistor is  $v = iR = 1V$

Example One




Example Two



Check yourself: Analyzing simple circuits

Correct answer: 1

The current through the resistor is 1A

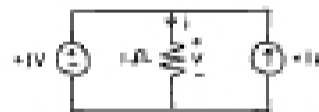


More complex circuits can be analyzed by systematically applying Kirchhoff's voltage law (KVL) and Kirchhoff's current law (KCL)

### Analyzing Circuits: KVL

The sum of the voltages around any closed path is zero

Example:  $-v_1 + v_2 + v_3 = 0$

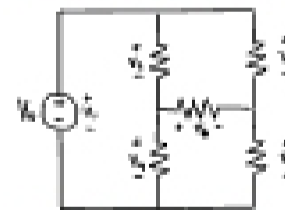

Check yourself: Kirchhoff's Voltage Law

Correct answer: 5

How many KVL relations are there for this circuit? There are 7 loops

Planar circuits can be characterized by their inner loops

KVL equations for the inner loops are independent


$$A: -v_1 + v_2 + v_3 = 0$$

$$B: -v_2 + v_3 - v_4 = 0$$

$$C: -v_3 + v_4 + v_5 = 0$$

All possible KVL equations for planar circuits can be generated by combinations of the inner loops

$$A + B = 0$$

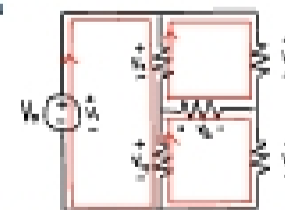

One KVL equation can be written for every closed path in a circuit

Sets of KVL equations are not necessarily linearly independent

KVL equations for the inner loops of planar circuits are linearly independent

**Analyzing Circuits: KCL**


The flow of electrical current is analogous to the flow of incompressible fluid, such as water  
 Current  $i_1$  flows into a node and two currents  $i_2$  and  $i_3$  flow out

$$i_1 = i_2 + i_3$$



The net flow of electrical current into or out of a node is zero  
 The net current out of the top node must be zero

$$i_1 + i_2 + i_3 = 0$$


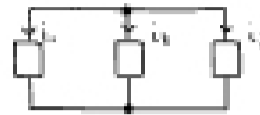


Electrical currents cannot accumulate in elements, so current that flows into a circuit element also flows out

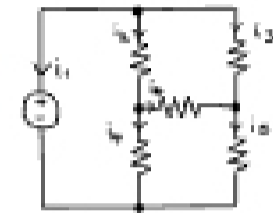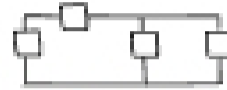**Check yourself: Kirchhoff's Current Law**

Correct answer: 2

There are three equations that can be written but only two of them are linearly independent KCL equations



**Check yourself: Kirchhoff's Current Law**

Correct answer: 1

There are three linearly independent KCL equations

General form: the number of linearly independent KCL equation is the number of nodes minus one

The net current out of any closed surface (which can contain multiple nodes) is zero

**KVL, KCL, and Constitutive Equations**


Circuits can be analyzed by combining

- All linearly independent KVL equations
- All linearly independent KCL equations
- One constitutive equation for each element

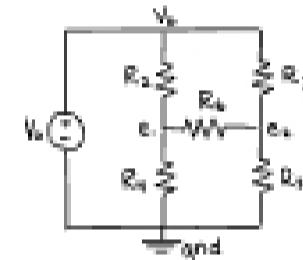**Node Voltages**

The "node" method is one of many ways to systematically reduce the number of circuit equations and unknowns


- Label all nodes except one: ground = 0 V
- Write KCL for each node whose voltage is not unknown
- Solve for the unknowns



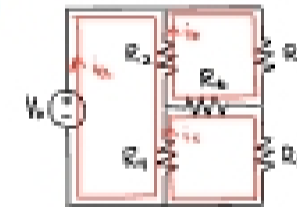**Loop Currents**

The "loop current" method is another way to systematically reduce the number of circuit equations and unknowns


- Label all the loop currents
- Write KVL for each loop
- Solve for the unknowns



**Check yourself: Current**

Correct answer: 3

The current in the circuit is -1A

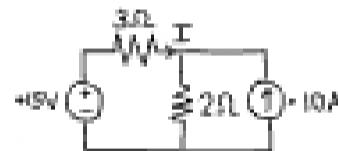

**Common Patterns**

Circuits can be simplified when two or more elements behave as a single element

A "one-part" is a circuit that can be represented as a single element

A one-part has two terminals



Current enters one terminal (+) and exits another (-), producing a voltage (v) across the terminals



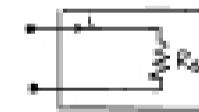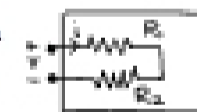**Series Combinations**

The series combination of two resistors is equivalent to a single resistor whose resistance is the sum of the two original resistances:  $R_S = R_1 + R_2$


The resistance of a series combination is always larger than either of the original resistances



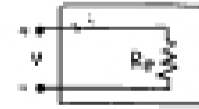**Parallel Combinations**

The parallel combination of two resistors is equivalent to a single resistor whose conductance (1/resistance) is the sum of the two original conductances


The resistance of a parallel combination is always smaller than either of the original resistances



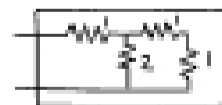**Check yourself: Equivalent Resistance**

Correct answer: 3

The equivalent resistance of the one-part is 2 ohms



**Voltage Divider**

Resistors in series act as voltage dividers




**Current Divider**

Resistors in parallel act as current dividers



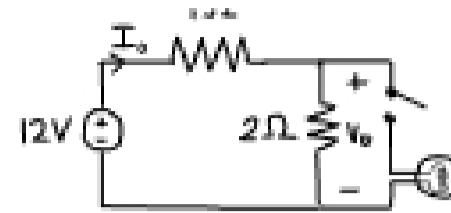**Interaction of Circuit Elements**

Circuit design is complicated by interactions among the elements  
 Adding an element change voltages and currents throughout the circuit  
 Example: closing a switch is equivalent to adding a new element



Check yourself: Closing a switch

Correct answer: 2

Closing the switch cause  $V_0$  to decrease and  $I_0$  to increase

**One Ports:**

If a circuit connects to the world via just two terminals, then that circuit can be represented by a single generalized element called a one-port, regardless of how many components are in the circuit

This is analogous to

- replacing delays, gains and adders with a system function
- combining a sequence of operations in a procedure call
- combining diverse data in a list


These representations are compositional—they replace multiple elements with a single element that can be used in the same way that primitives are used

**Current-Voltage Relations**

Current-voltage relations for resistors and sources are straight lines

Current-voltage relations are analogous to system functionals

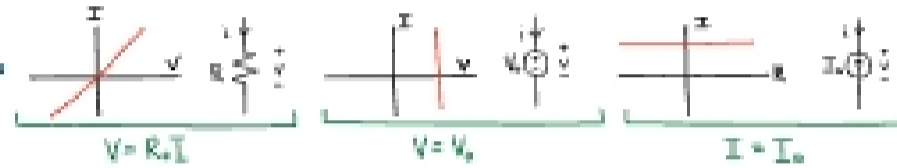They summarize the behavior of a one-port



**Parallel One-Ports**

If the  $i-v$  curves for two one-ports are both straight lines, then the  $i-v$  curve for the parallel combination is a straight line

This is because the sum of two straight lines is a straight line


**Series One-Ports**

If the  $i-v$  curves for two one-ports are both straight lines, then the  $i-v$  curve for the series combination is a straight line

This is because the horizontal sum of two straight lines is a straight line

Check yourself: Current-Voltage

Correct answer: 1

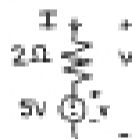

**Summary**

Circuits represent systems as connection of elements

- Through which currents (through variables) flow
- Across while voltages (across variables) develop

We have seen three (of many) methods for analysing circuits, each one based on a different set of variables

- currents and voltages for each element
- node voltages
- loop currents

We can simplify analysis by recognizing common patterns

- series and parallel combinations
- voltage and current dividers

We have seen our first major abstraction: the one-port and a representation to characterize it—the current-voltage relation.