

PROBLEMS

Section 11.2—Transmission Line Parameters

- 11.1 An air-filled planar line with  $w = 30$  cm,  $d = 1.2$  cm,  $t = 3$  mm has conducting plates with  $\sigma_s = 7 \times 10^7$  S/m. Calculate  $R$ ,  $L$ ,  $C$ , and  $G$  at 990 MHz.
- 11.2 A coaxial cable has an inner conductor of radius  $a = 0.8$  mm and an outer conductor of radius  $b = 2.6$  mm. The conductors have  $\sigma_s = 5.28 \times 10^7$  S/m,  $\mu_s = \mu_0$ , and  $\epsilon_s = \epsilon_0$ ; they are separated by a dielectric material having  $\sigma = 10^{-12}$  S/m,  $\mu = \mu_0$ ,  $\epsilon = 3.5 \epsilon_0$ . At 60 MHz, calculate the line parameters  $L$ ,  $C$ ,  $G$ , and  $R$ .
- 11.3 The copper leads of a diode are 16 mm in length and have a radius of 0.3 mm. They are separated by a distance of 2 mm as shown in Figure 11.44. Find the capacitance between the leads and the ac resistance at 10 MHz.

Section 11.3—Transmission Line Equations

- \*11.4 In Section 11.3, it was mentioned that the equivalent circuit of Figure 11.5 is not the only possible one. Show that eqs. (11.4) and (11.6) would remain the same if the  $\Pi$ -type and  $T$ -type equivalent circuits shown in Figure 11.45 were used.

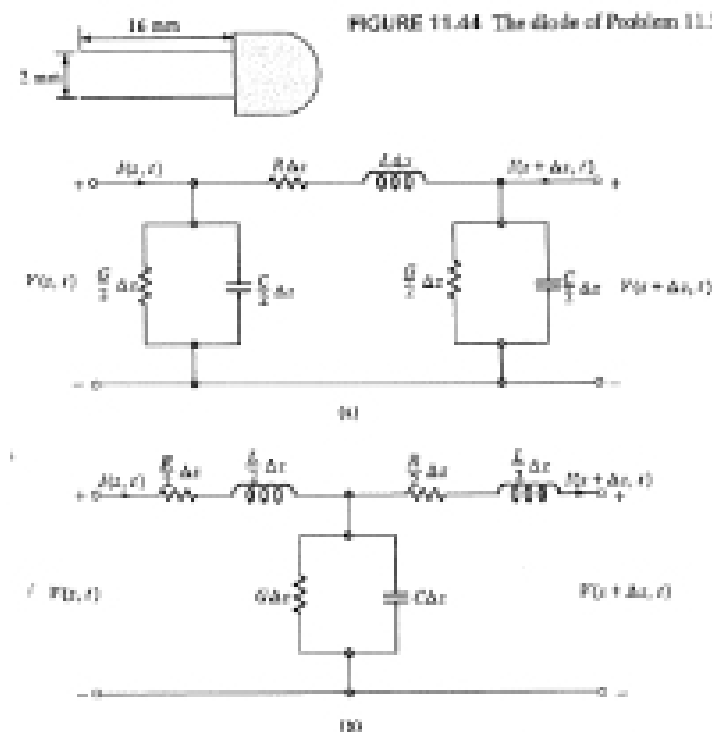


FIGURE 11.45 Equivalent circuits for Problem 11.4: (a)  $\Pi$ -type, (b)  $T$ -type.

- 11.5 (a) Show that at high frequencies ( $R \ll \omega L$ ,  $G \ll \omega C$ ),

$$\gamma = \left( \frac{R}{2} \sqrt{\frac{C}{L}} + \frac{G}{2} \sqrt{\frac{L}{C}} \right) + j\omega \sqrt{LC}$$

- (b) Obtain a similar formula for  $Z_0$ .
- 11.6 A lossless cable has parameters  $L = 0.42$   $\mu$ H/m and  $C = 80$  pF/m. Find the velocity and the characteristic impedance of the cable.
- 11.7 At 60 MHz, the following characteristics of a lossy line are measured:

$$Z_0 = 50\Omega, \quad \alpha = 0.04 \text{ dB/m}, \quad \beta = 2.5 \text{ rad/m}$$

Calculate  $R$ ,  $L$ ,  $C$ , and  $G$  of the line.

- 11.8 A 75  $\Omega$  lossless planar line was designed but did not meet a requirement. What fraction of the width of the strip should be added or removed to get the characteristic impedance of 75  $\Omega$ ?
- 11.9 A telephone line operating at 1 kHz has  $R = 6.8$   $\Omega$ /mi,  $L = 3.4$  mH/mi,  $C = 8.4$  nF/mi, and  $G = 0.42$   $\mu$ S/mi. Find (a)  $Z$  and  $\gamma$ , (b) phase velocity, (c) wavelength.
- 11.10 A lossless transmission line has  $L = 6.5$   $\mu$ H/m and  $C = 40$  nF/m. Calculate the velocity ratio  $u/c$  for this case.
- 11.11 A distortionless line operating at 120 MHz has  $R = 20$   $\Omega$ /m,  $L = 0.9$   $\mu$ H/m, and  $C = 43$  pF/m. (a) Determine  $\gamma$ ,  $\alpha$ , and  $Z_0$ . (b) How far will a voltage wave travel before it is reduced to 20% of its initial magnitude? (c) How far will it travel to suffer a 45° phase shift?
- 11.12 A coaxial cable has its conductors made of copper ( $\sigma_s = 5.8 \times 10^7$  S/m) and its dielectric made of polyethylene ( $\epsilon_s = 2.25$ ,  $\mu_s = 1$ ). If the radius of the outer conductor is 3 mm, determine the radius of the inner conductor so that  $Z_0 = 75\Omega$ .

- 11.13 For a lossless two-wire transmission line, show that

(a) The phase velocity  $u = c = \frac{1}{\sqrt{LC}}$

(b) The characteristic impedance  $Z_0 = \frac{120}{\sqrt{\epsilon_s}} \cosh^{-1} \frac{d}{2a}$

Is part (a) true of other lossless lines?

- 11.14 A twisted line, which may be approximated by a two-wire line, is very useful in the telephone industry. Consider a line comprising two copper wires of diameter 0.12 cm that have a 0.32 cm center-to-center spacing. If the wires are separated by a dielectric material with  $\epsilon = 3.5\epsilon_0$ , find  $L$ ,  $C$ , and  $Z_0$ .

- 11.15 On a distortionless line, the voltage wave is given by

$$V(z') = 120e^{j2000z'} \cos(10^7t + 2z') + 60e^{-j4000z'} \cos(10^7t - 2z')$$

where  $z'$  is the distance from the load. If  $Z_L = 300 \Omega$ , find (a)  $\alpha$ ,  $\beta$ , and  $u$ , (b)  $Z_0$ , and  $R(z')$ .

11.16 The voltage on a line is given by

$$V(\ell) = 80e^{-\alpha\ell} \cos(2\pi \times 10^8 t + 0.01\ell) + 60e^{-\alpha\ell} \cos(2\pi \times 10^8 t + 0.01\ell + \pi)$$

where  $\ell$  is the distance from the load. Calculate  $\gamma$  and  $\alpha$ .

11.17 A distortionless transmission line satisfies  $RC = LG$ . If the line has  $R = 10 \text{ m}\Omega/\text{m}$ ,  $C = 82 \text{ pF/m}$ , and  $L = 0.6 \text{ }\mu\text{H/m}$ , calculate its characteristic impedance and propagation constant. Assume that the line operates at 80 MHz.

11.18 A coaxial line 5.6 m long has distributed parameters  $R = 6.5 \text{ }\Omega/\text{m}$ ,  $L = 1.4 \text{ }\mu\text{H/m}$ ,  $G = 8.4 \text{ mS/m}$ , and  $C = 21.5 \text{ pF/m}$ . If the line operates at 2 MHz, calculate the characteristic impedance and the end-to-end propagation time delay.

#### Section 11.4—Input Impedance, Standing Wave Ratio, and Power

11.19 (a) Show that a transmission coefficient may be defined as

$$\tau_1 = \frac{V_1}{V_2} = 1 + \Gamma_1 = \frac{2Z_2}{Z_2 + Z_1}$$

(b) Find  $\tau_1$  when the line is terminated by (i) a load whose value is  $nZ_0$ , (ii) an open circuit, (iii) a short circuit, (iv)  $Z_2 = Z_0$  (matched line).

11.20 A standing wave has a minimum field of  $20 \text{ }\mu\text{V/m}$  and a maximum field of  $120 \text{ }\mu\text{V/m}$ . Calculate (a) the standing wave ratio, (b) the reflection coefficient.

11.21 A lossy transmission line has  $R = 3.5 \text{ }\Omega/\text{m}$ ,  $L = 2 \text{ }\mu\text{H/m}$ ,  $C = 120 \text{ pF/m}$ , and  $G = 0$ . At 400 MHz, determine  $\alpha$ ,  $\beta$ ,  $Z_0$ , and  $\nu$ .

11.22 Show that a lossy transmission line of length  $\ell$  has an input impedance  $Z_{in} = Z_0$  with  $\gamma\ell$  when shorted and  $Z_{in} = Z_0 \coth \gamma\ell$  when open. Confirm eqs. (11.41) and (11.42).

11.23 Find the input impedance of a short-circuited coaxial transmission line of Figure 11.46 if  $Z_0 = 68 + j33 \text{ }\Omega$ ,  $\gamma = 0.7 + j2.5/\text{m}$ ,  $\ell = 0.8 \text{ m}$ .

11.24 A 50- $\Omega$  transmission line of length  $\ell$  is open-circuited. If the input impedance is  $-j82 \text{ }\Omega$ , determine  $\ell$  in terms of  $\lambda$ .

11.25 Refer to the lossless transmission line shown in Figure 11.47. (a) Find  $\Gamma$  and  $\alpha$ . (b) Determine  $Z_0$  at the generator.

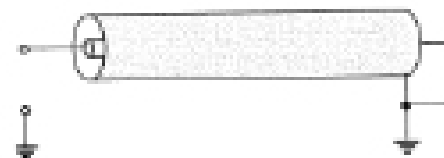


FIGURE 11.46 For Problem 11.23.

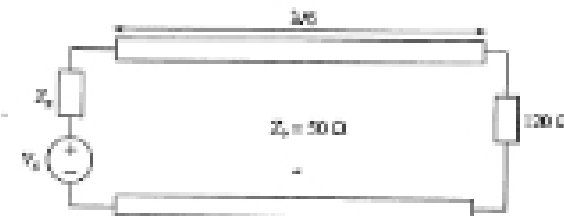


FIGURE 11.47 For Problem 11.25.

11.26 A 60- $\Omega$  lossless line is connected to a source with  $V_g = 10\sqrt{2} \text{ V}_{\text{rms}}$  and  $Z_g = 50 - j40 \text{ }\Omega$  and terminated with a load of  $j40 \text{ }\Omega$ . If the line is 100 m long and  $\beta = 0.25 \text{ rad/m}$ , calculate  $Z_0$  and  $V$  at:

- The sending end
- The receiving end
- 4 m from the load
- 3 m from the source

11.27 A lossless transmission line with a characteristic impedance of 75  $\Omega$  is terminated by a load of 120  $\Omega$ . The length of the line is 1.25 $\lambda$ . If the line is energized by a source of 100 V (rms) with an internal impedance of 50  $\Omega$ , determine (a) the input impedance and (b) the magnitude of the load voltage.

11.28 Consider the two-port network shown in Figure 11.48(a). The relation between the input and output variables can be written in matrix form as

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

For the lossy line in Figure 11.48(b), show that the ABCD matrix is

$$\begin{bmatrix} \cosh \gamma\ell & Z_0 \sinh \gamma\ell \\ \frac{1}{Z_0} \sinh \gamma\ell & \cosh \gamma\ell \end{bmatrix}$$

11.29 A 100- $\Omega$  line is terminated in a load. If the reflection coefficient is  $\Gamma_L = 0.68 + j0.15$ , calculate (a) the load impedance, (b) the standing wave ratio.

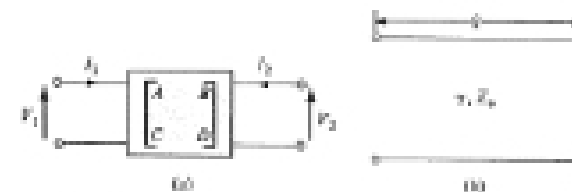


FIGURE 11.48 For Problem 11.28: (a) network, (b) lossy line.

## Section 11.5—The Smith Chart

- 11.30 A quarter-wave lossless  $100\ \Omega$  line is terminated by a load  $Z_L = 210\ \Omega$ . If the voltage at the receiving end is  $80\ \text{V}$ , what is the voltage at the sending end?
- 11.31 A  $50\ \Omega$  transmission line is terminated by a  $100 + j150\ \Omega$  load. How far from the load will the line impedance be  $50 + j100\ \Omega$ ?
- 11.32 Two lines are cascaded as shown in Figure 11.49. Determine:  
 (a) The input impedance  
 (b) The standing wave ratio for sections XY and YZ  
 (c) The reflection coefficient at Z
- 11.33 A  $50\ \Omega$  lossless line is  $4.2\ \text{m}$  long. At the operating frequency of  $300\ \text{MHz}$ , the input impedance at the middle of the line is  $80 - j60\ \Omega$ . Find the input impedance at the generator and the voltage reflection coefficient at the load. Take  $n = 0.8$ .
- 11.34 A lossless transmission line, with characteristic impedance of  $50\ \Omega$  and electrical length of  $\ell = 0.27\lambda$ , is terminated by a load impedance  $40 - j25\ \Omega$ . Determine  $\Gamma_V$ ,  $s$ , and  $Z_{in}$ .
- 11.35 A  $75\ \Omega$  lossless transmission line is  $132\ \text{cm}$  long, with a dielectric constant  $n_r = 3.62$ . If the line operates at  $400\ \text{MHz}$  with an input impedance of  $Z_{in} = 40 + j5\ \Omega$ , use the Smith chart to determine the terminating load.
- 11.36 The distance from the load to the first minimum voltage in a  $50\ \Omega$  line is  $0.12\lambda$  and the standing wave ratio  $s = 4$ .  
 (a) Find the load impedance  $Z_L$ .  
 (b) Is the load inductive or capacitive?  
 (c) How far from the load is the first maximum voltage?
- 11.37 A lossless  $50\ \Omega$  line is terminated by a load  $Z_L = 75 + j60\ \Omega$ . Using a Smith chart, determine (a) the reflection coefficient  $\Gamma$ , (b) the standing wave ratio  $s$ , (c) the input impedance at  $0.2\lambda$  from the load, (d) the location of the first minimum voltage from the load, (e) the shortest distance from the load at which the input impedance is purely resistive.
- 11.38 A transmission line is terminated by a load with admittance  $Y_L = (0.6 + j0.8)/Z_0$ . Find the normalized input impedance at  $\lambda/8$  from the load.
- 11.39 For a transmission line,  $f = 100\ \text{MHz}$ ,  $\mu = 2 \times 10^{-7}\ \text{mH/m}$ ,  $\ell = 1.2\ \text{m}$ , and  $Z_0 = 50\ \Omega$ . If the line is terminated in a load  $Z_L = 150 + j200\ \Omega$ , determine the input impedance.

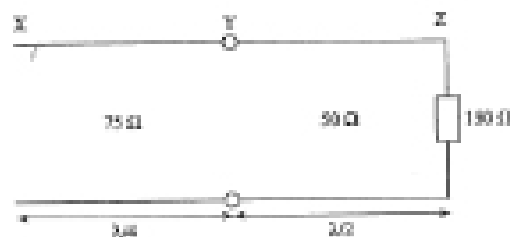


FIGURE 11.49 For Problem 11.32.

- 11.40 An  $80\ \Omega$  transmission line operating at  $12\ \text{MHz}$  is terminated by a load  $Z_L$ . At  $22\ \text{m}$  from the load, the input impedance is  $100 - j120\ \Omega$ . If  $n = 0.8$ ,  
 (a) Calculate  $\Gamma_V$ ,  $Z_{V,max}$ , and  $Z_{V,min}$ .  
 (b) Find  $Z_L$ ,  $s$ , and the input impedance at  $28\ \text{m}$  from the load.  
 (c) How many  $Z_{V,max}$  and  $Z_{V,min}$  are there between the load and the  $100 - j120\ \Omega$  input impedance?
- 11.41 An antenna, connected to a  $150\ \Omega$  lossless line, produces a standing wave ratio of  $2.6$ . If measurements indicate that voltage maxima are  $120\ \text{cm}$  apart and that the last maximum is  $40\ \text{cm}$  from the antenna, calculate  
 (a) The operating frequency  
 (b) The antenna impedance  
 (c) The reflection coefficient (assume that  $n = 1$ ).
- 11.42 An  $80\ \Omega$  lossless line has  $Z_L = j80\ \Omega$  and  $Z_{in} = j40\ \Omega$ . (a) Determine the shortest length of the line. (b) Calculate  $s$  and  $\Gamma_V$ .
- 11.43 A  $75\ \Omega$  lossless line is terminated by an unknown load impedance  $Z_L$ . If at a distance  $0.2\lambda$  from the load the voltage is  $V_r = 2 + j\ \text{V}$  while the current is  $10\ \text{mA}$ , find  $Z_L$  and  $s$ .
- 11.44 Two  $\lambda/4$  transformers in tandem are to connect a  $50\ \Omega$  line to a  $75\ \Omega$  load as in Figure 11.50.  
 (a) Determine the characteristic impedance  $Z_{01}$  if  $Z_{02} = 50\ \Omega$  and there is no reflected wave to the left of A.  
 (b) If the best results are obtained when

$$\left[ \frac{Z_{01}}{Z_{02}} \right]^2 = \frac{Z_{01}}{Z_{02}} = \left[ \frac{Z_{01}}{Z_L} \right]^2$$

determine  $Z_{01}$  and  $Z_{02}$  for this case.

- 11.45 Two identical antennas, each with input impedance  $74\ \Omega$ , are fed with three identical  $50\ \Omega$  quarter-wave lossless transmission lines as shown in Figure 11.51. Calculate the input impedance at the source end.

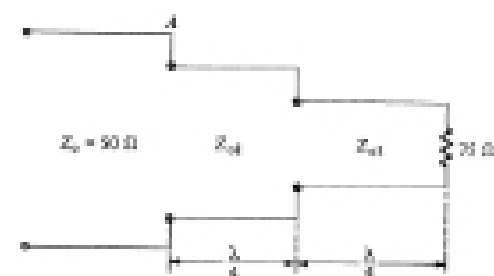


FIGURE 11.50 Double section transformer of Problem 11.44.