

Electronic Circuits Laboratory


EE462G

Lab #8

BJT Common Emitter Amplifier


npn Bipolar Junction Transistor

BJT in a common-emitter configuration

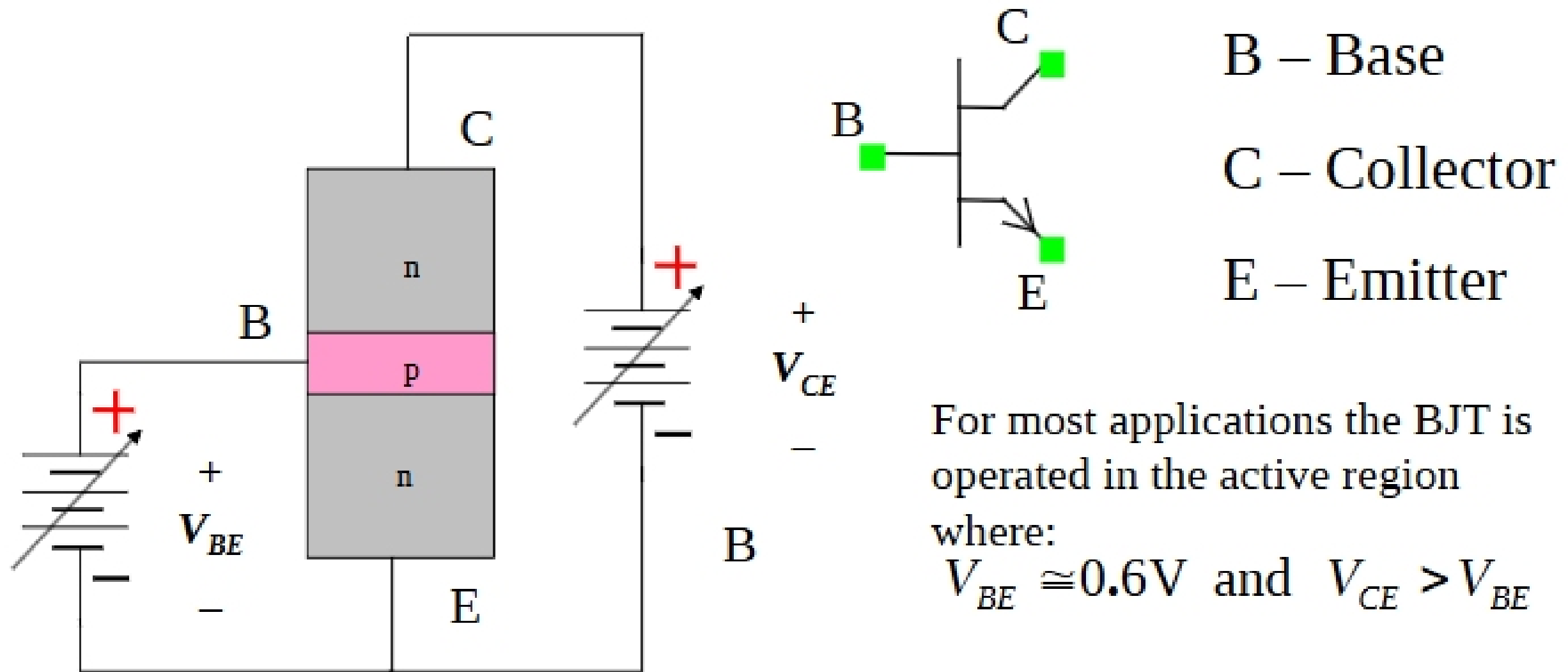

nnp BJT Operation

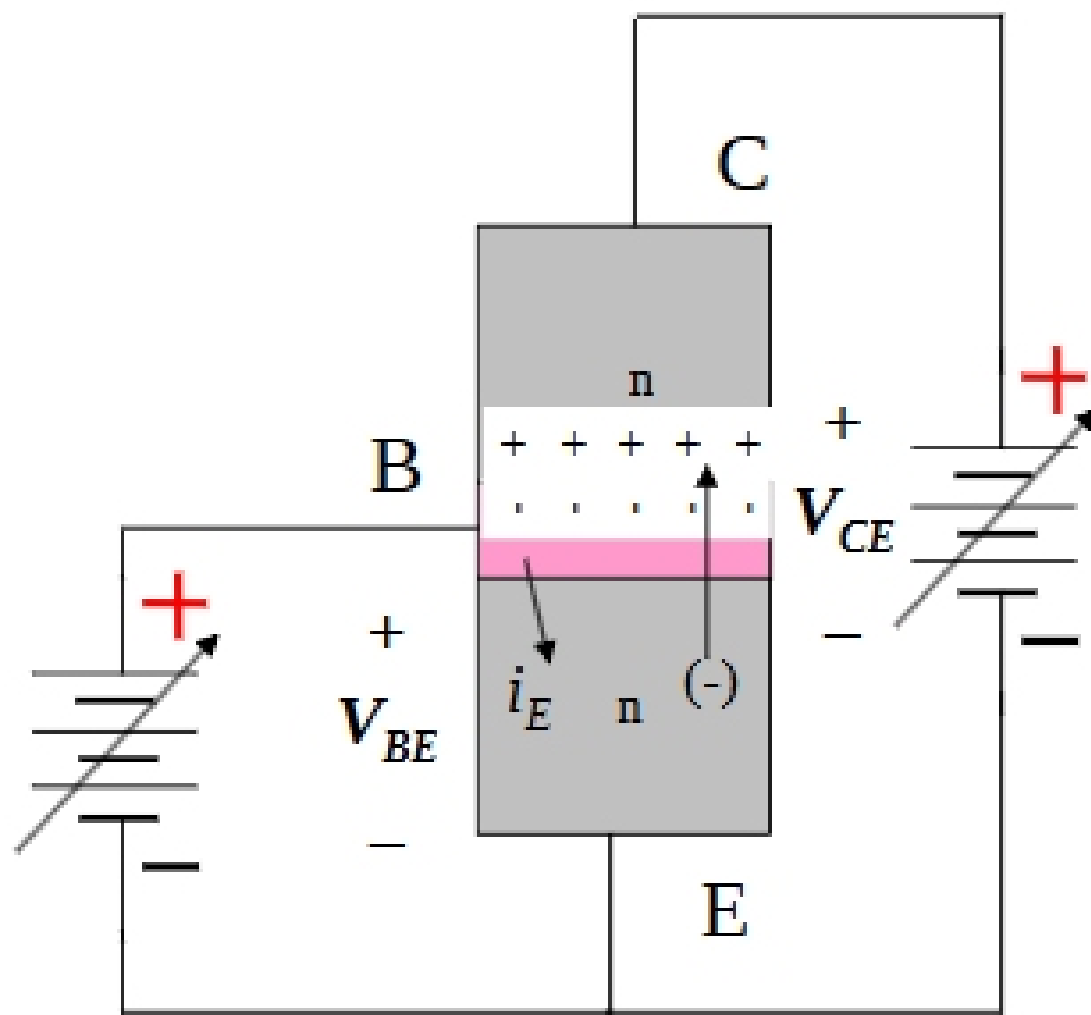BJT in a common-emitter configuration in active region ($V_{CE} > V_{BE} \sim .6V$):



The *pn* junction for V_{BE} is forward biased and current i_{BE} flows according to the Shockley equation:

$$i_E = I_{ES} \left[\exp \left(\frac{V_{BE}}{V_T} \right) - 1 \right]$$

where $V_T \cong .26 \text{ mV}$ and I_{ES} ranges from 10^{-12} to 10^{-17} .

Electrons from the emitter flow into the base and are pulled into the depletion region of the reversed biased collector-base junction.