

Introduction to Interface Electronics

- **Lumped Circuit Elements**
- **General Amplifiers**
- **Operational Amplifiers**

 Reading: Senturia, Chapter 14, p.353-395

- Linear 1-port (2-terminal) passive devices
 - Resistor: energy dissipation
 - Capacitor: energy storage
 - Inductor: energy storage

<i>Parameter</i>	<i>Basic Relationship</i>	<i>Voltage-Current Relationships</i>	<i>Energy</i>
R $G = \frac{1}{R}$	$v = Ri$	$v_R = Ri_R$ $i_R = Gv_R$	$w_R = \int_{-\infty}^t v_R i_R dt$
L (or M)	$\psi = Li$	$v_L = L \frac{di_L}{dt}$ $i_L = \frac{1}{L} \int_{-\infty}^t v_L dt$	$w_L = \frac{1}{2} Li^2$
C $D = \frac{1}{C}$	$q = Cv$	$v_C = \frac{1}{C} \int_{-\infty}^t i_C dt$ $i_C = C \frac{dv_C}{dt}$	$w_C = \frac{1}{2} Cv^2$


- Non-linear 1-port (2-terminal) passive devices
 - P/N junction diode
 - Nonlinear I-V characteristic

$$i_D = I_S \left(e^{\frac{qv_D}{kT}} - 1 \right)$$

Note: Diode voltage, $v_D = V_D + v_d$

$$DC : I_D = I_S \left(e^{\frac{qV_D}{kT}} - 1 \right)$$
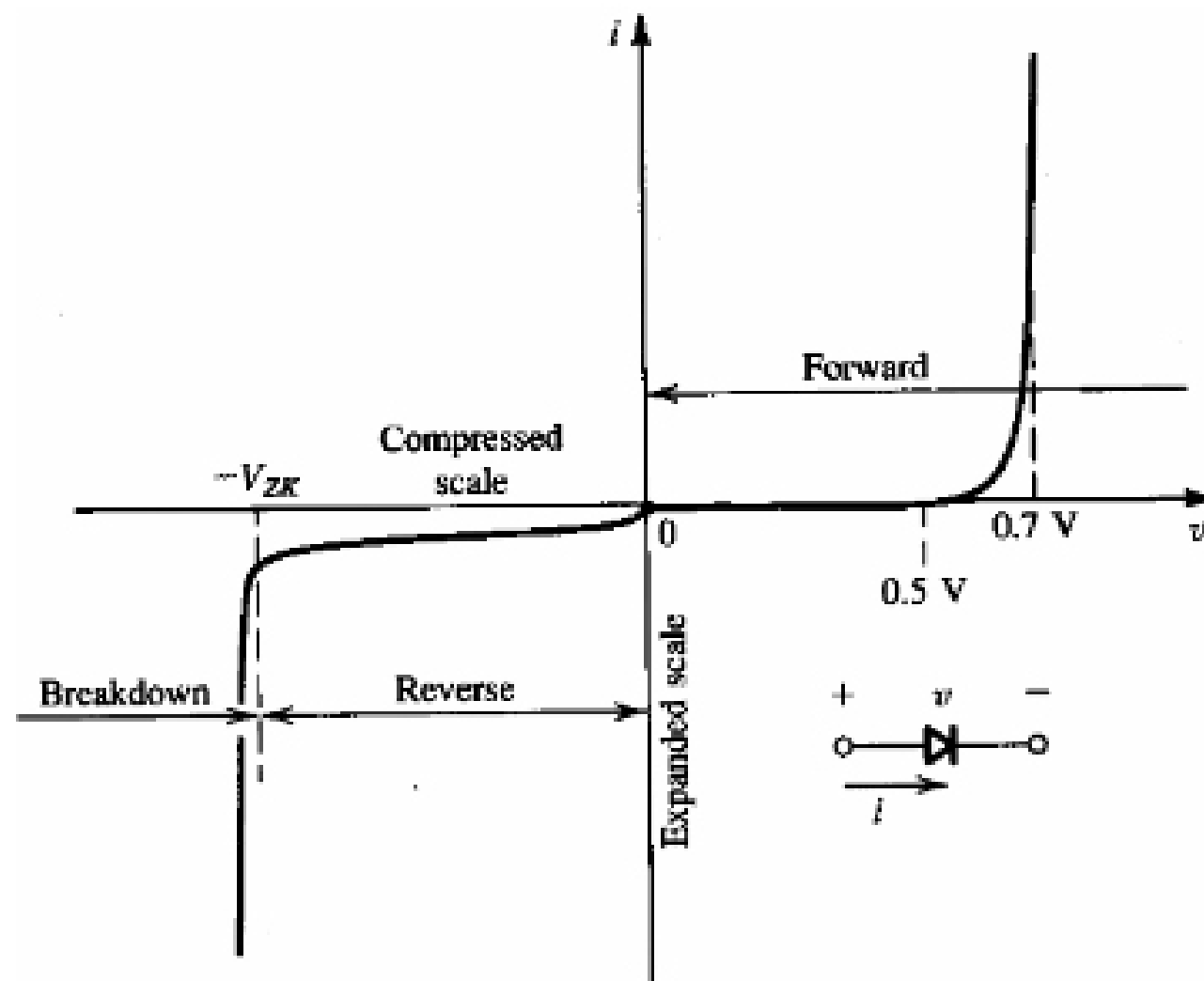
$$Small - signal : i_d = \left(\frac{qI_D}{kT} \right) v_d = \frac{1}{r_d} v_d$$



Ref. Sedra and Smith, Microelectronic Circuits, p. 132.