
 



State Elements

 


RS latch
 R,S control mode (reset, set, storage)
 Q,Q' track R and S
 R=1, S=1 invalid



 D latch
 C controls mode (0=latched, 1=transparent)
 D is data input ("copied" during transparent)
 Signal value triggered: Q,Q' track D when C=1
 Guarantees R=1,S=1 can not be done




 D flip-flop (falling or negative edge triggered)
 Two cascaded D latches
 C=1 means 1st latch transparent, 2nd latched
 C=0 means 1st latch latched, 2nd transparent
 Output changes on falling edge (C: 1=>0)




D flip-flop (rising or positive edge triggered)
 Same as falling edge triggered
 Output changes on rising edge (C: 0=>1)


Signaling Behavior

 


Signaling Behavior

 


Signaling Behavior

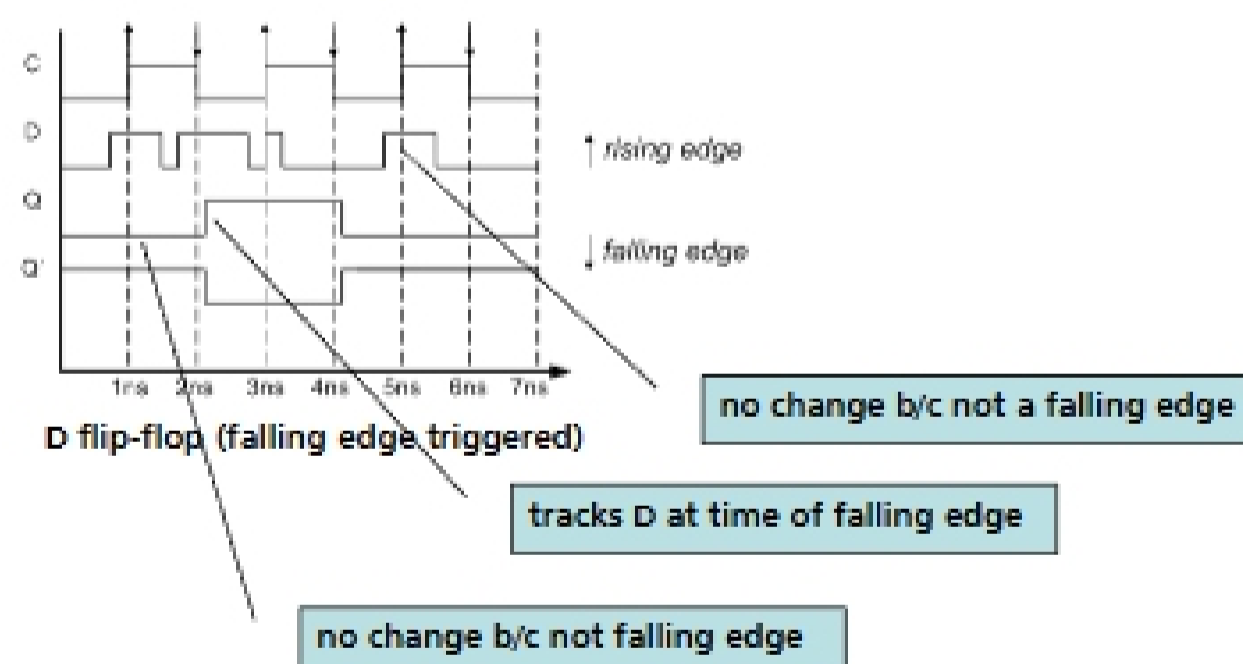


Signaling Behavior

 

RS latch behavior

 

D latch behavior

 

D flip-flop (falling edge triggered)

Example circuits and clocking

- Suppose we want to:
 - 1-bit value A stored in a D flip-flop
 - 1-bit value B stored in a D flip-flop
 - 1-bit value C stored in a D flip-flop
 - Do addition of A and B, producing C
- $C = A + B$
 - What is the circuit?
 - Need three D flip-flops
 - Need one 1 bit adder