

## **EE468G NOTES (8B)**

Reading assignment: Chapter 11

Contents: Transmission line: time harmonic analysis

## Time harmonic wave on transmission line

The transmission line equation in frequency domain can be obtained by replacing  $\partial/\partial t$  with  $j\omega$ :

$$\frac{\partial V}{\partial z} = -RI - j\omega LI = -(R + j\omega L)I$$

$$\frac{\partial I}{\partial z} = -GV - j\omega CV = -(G + j\omega C)V$$

In the above,  $V$  and  $I$  are complex functions of “z”.

$$\text{Lossless case: } \begin{cases} \frac{\partial V}{\partial z} = -j\omega L I, & (1) \\ \frac{\partial I}{\partial z} = -j\omega C V, & (2) \end{cases}$$

Take  $\partial/\partial z$  on both sides of eq. (1),

$$\begin{aligned} \frac{\partial^2 V}{\partial z^2} &= -j\omega L \frac{\partial I}{\partial z} \quad \leftarrow \text{use eq.(2) to replace } \frac{\partial I}{\partial z} \\ &= -j\omega L (-j\omega C V) = -\omega^2 LC V \end{aligned}$$

Let  $\beta^2 = \omega^2 LC$ ,  $\beta = \omega\sqrt{LC}$  [1/m] is the wavenumber. The equation for the voltage function  $V(z)$ :

$$\frac{\partial^2 V}{\partial z^2} + \beta^2 V = 0$$

General solution:

$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$$

Using eq.(1), we get the solution for the current  $I(z)$ :

$$\begin{aligned} I(z) &= \frac{1}{-j\omega L} \frac{\partial V}{\partial z} = \frac{-j\beta}{-j\omega L} [V^+ e^{-j\beta z} - V^- e^{j\beta z}] \\ &= \frac{1}{Z_0} [V^+ e^{-j\beta z} - V^- e^{j\beta z}], \quad Z_0 = \frac{\omega L}{\beta} \end{aligned}$$

Parameters of a *lossless* transmission line:

$$\text{Characteristic impedance: } Z_0 = \frac{\omega L}{\beta} = \frac{\omega L}{\omega \sqrt{LC}} = \sqrt{\frac{L}{C}}, \quad [\Omega]$$

$$\text{Wavenumber: } \beta = \frac{2\pi}{\lambda} = \omega \sqrt{LC} \quad [\text{rad/m}] \text{ or } [1/\text{m}]$$

$$\text{Phase velocity: } u_p = \frac{\omega}{\beta} = \frac{\omega}{\omega \sqrt{LC}} = \frac{1}{\sqrt{LC}}$$

$$\text{Group velocity: } u_g = \frac{d\omega}{d\beta}$$

Special case for lossless TEM line:  $LC = \mu\epsilon$

For lossy line: the general solution can be written as:

$$V(z) = V^+ e^{-\alpha z} e^{-j\beta z} + V^- e^{\alpha z} e^{j\beta z}$$

$\alpha$  is the attenuation constant, its unit is  $[1/\text{m}]$  or  $[\text{Np/m}]$  (Np = Nepper). Sometimes, the attenuation constant is expressed in the unit of  $[\text{dB/m}]$ . The relation of the two units are:

$$\alpha \text{ [dB/m]} = 8.686 \times \alpha \text{ [Np/m]}$$

$$\alpha \text{ [Np/m]} = 0.1151 \text{ [dB/m]}$$

The attenuation constant is important for long-distance transmission. For example, if a cable has an attenuation constant of  $0.3 \text{ [dB/km]}$ , then the attenuation would be  $30 \text{ [dB]}$  at  $100 \text{ km}$  distance away. This means the signal power is reduced by a factor of 1000.