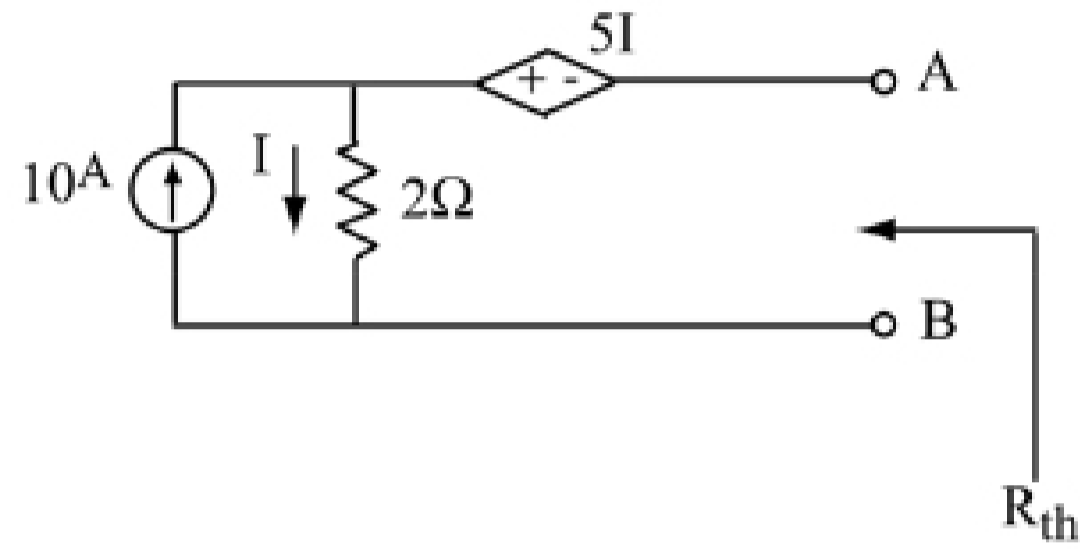


Problem 1

Find the Thevenin equivalent resistance R_{th} for the circuit below at terminals A-B.


- (a) -7Ω (b) -3Ω (c) 2Ω (d) 3Ω (e) 7Ω



Problem 2

For the circuit below, the short-circuit current I_{sc} in the Norton equivalent circuit is


- (a) 1 A (b) 2 A (c) 3 A (d) 4 A (e) 5 A

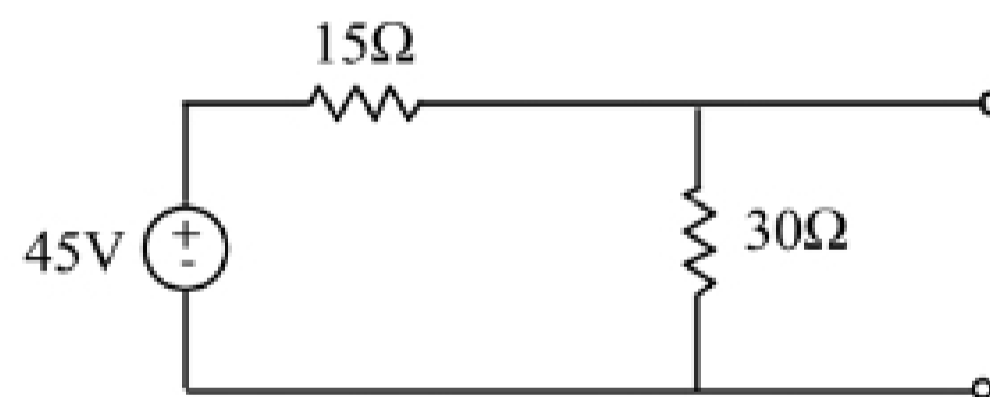

Problem 3

For the inductor circuit below, $i_L(0^-) = 0$. The inductor current $i_L(t)$, in A, is


- (a) $2 - 2e^{-5t}$ (b) $10 - 10e^{-5t}$ (c) $10e^{-5t} - 10$ (d) $2e^{-5t} - 2$ (e) $50e^{-5t} - 50$

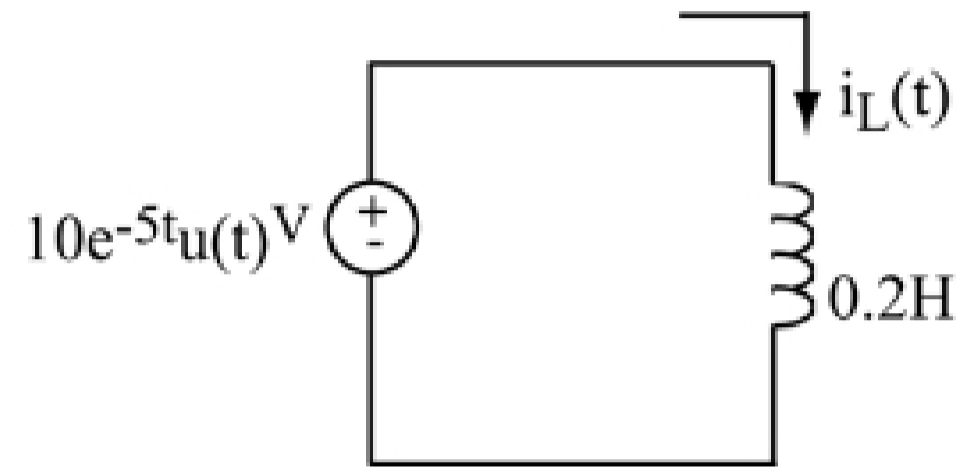

Problem 4

The equivalent capacitance C_{eq} for the circuit below is


- (a) 1 F (b) 2 F (c) 3 F (d) 4 F (e) 5 F

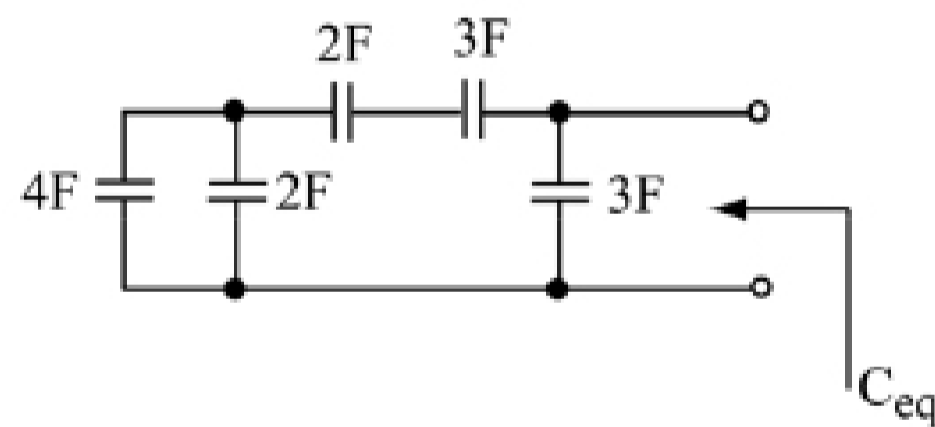

Problem 5

The maximum amount of power is transferred to the load resistor R_L when $R_L =$


- (a) 5Ω (b) 7.5Ω (c) 10Ω (d) 40Ω (e) 55Ω

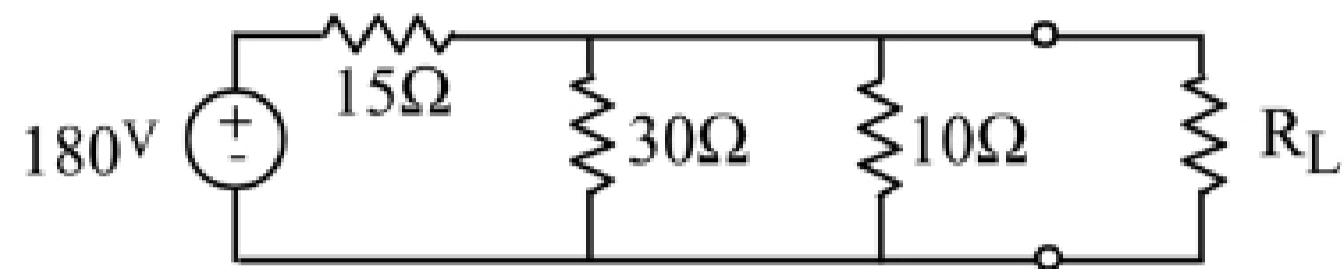

Problem 6

Two sets of measurements were taken for the linear resistive network shown below (see table below). If $V_{s1} = 2V$ and $I_{s2} = 4A$, then $V_x =$

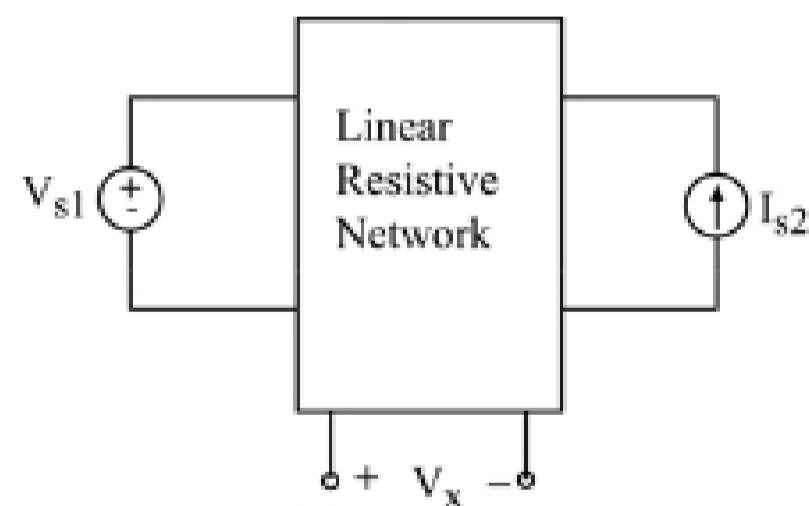- (a) $-2 V$ (b) $0 V$ (c) $2 V$ (d) $5 V$ (e) $20 V$



V_{s1}	I_{s1}	V_x
10 V	0 A	-20 V
0 V	5 A	5 V