

University of California
Berkeley
College of Engineering
Department of Electrical Engineering
and Computer Science


Robert W. Brodersen
EECS140

Analog Circuit Design

Lectures ON FEEDBACK

Feedback

FB-1

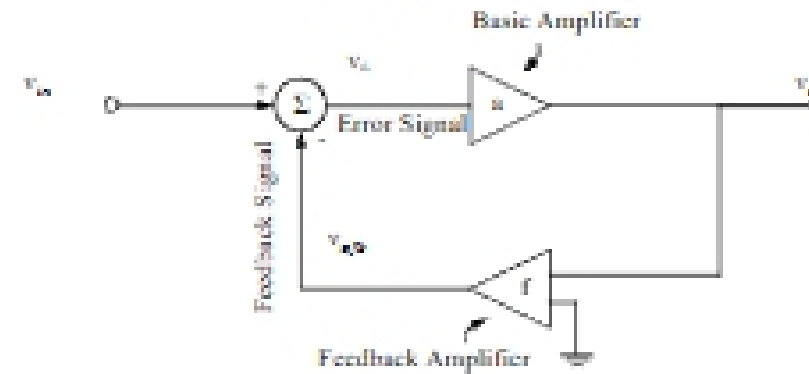

f = gain of feedback amplifier

a = gain of basic amplifier

Feedback (Cont.)

FB-2

$$v_i = v_e - v_{fb}$$

$$v_{fb} = f \cdot v_o$$

$$v_i = v_e - f \cdot v_o$$

$$v_o = a \cdot v_e$$

$$A_{cl} = v_o / v_i = \frac{a}{(1 + a \cdot f)} = \frac{1}{f} \cdot \left(\frac{\mathcal{T}}{1 + \mathcal{T}} \right) \leftarrow \text{Closed loop gain}$$

$$\mathcal{T} = \text{Loop Gain} = a \cdot f$$

a = Open Loop Gain

f = Feedback Factor

$$A_{cl} \approx \frac{1}{f} \quad \mathcal{T} \gg 1$$

Feedback (Cont.)

FB-3


There are 4 basic kinds of Feedback Circuits :

(Type of Feedback)		(Type of Sensing)
1) Series (Voltage)	-	Shunt (Voltage)
2) Shunt (Current)	-	Shunt (Voltage)
3) Shunt (Current)	-	Series (Current)
4) Series (Voltage)	-	Series (Current)

Series-Shunt (v_{out}/v_{in})


FB-6

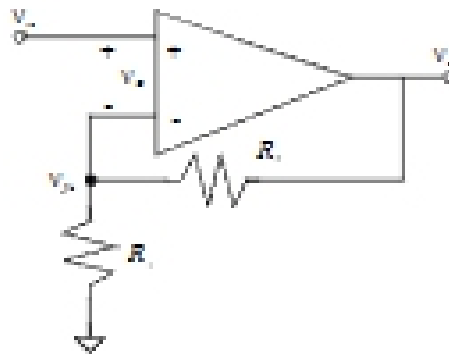This is a voltage amplifier, a typical example is the well known configuration shown below :



Series-Shunt (Cont.)

FB-7

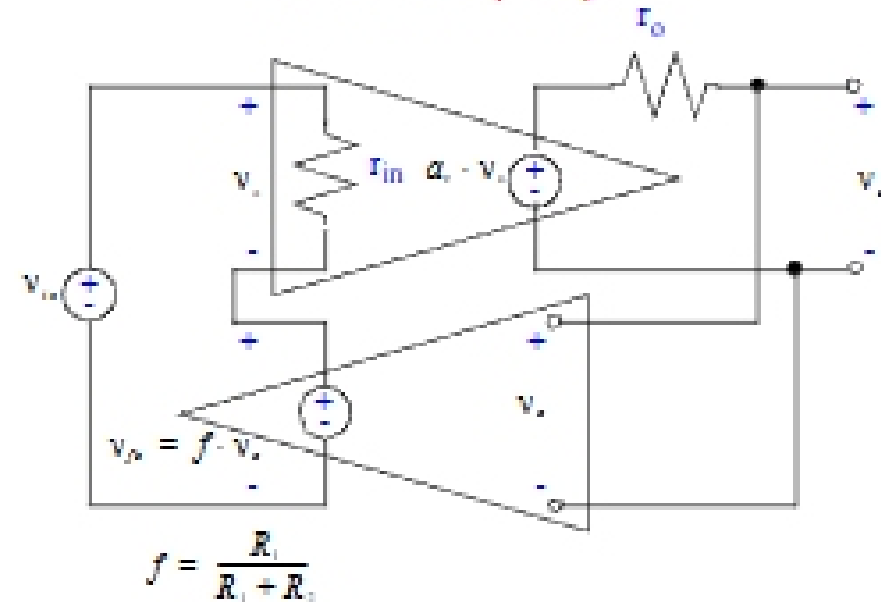

Series-Shunt (Cont.)

FB-8

Gain Calculation :

$$v_o = a_1 \cdot v_i$$

$$v_s = f \cdot v_o$$

$$v_i = v_o + v_s = \frac{v_o}{a_1} + f \cdot v_o$$

$$\frac{v_o}{v_i} = \frac{1}{f} \cdot \left(\frac{f}{1 + f} \right) = A, \quad \text{Closed Loop Gain}$$

$$v_o = \frac{v_i \cdot a_1}{1 + a_1 \cdot f}$$

$$v_o = v_i \cdot (1 + a_1 \cdot f)$$

Series-Shunt (Cont.)

FB-9

Rout Calculation (Closed Loop Output Resistance) :

$$R_{out} = \frac{v_o}{i_o}$$

Drive output with v_{in} , measure i_o .


$$i_o = \frac{v_o - a_1 \cdot v_i}{r_o}$$

$$v_o + f \cdot v_o = v_o = 0 ; v_i = -f \cdot v_o$$

$$v_i = 0$$

$$i_o = \frac{v_o + a_1 \cdot f \cdot v_o}{r_o}$$
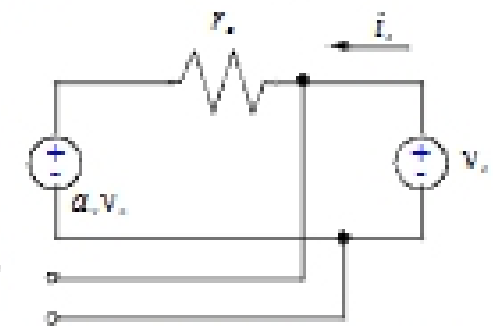
$$\frac{v_o}{i_o} = R_{out} = \frac{r_o}{1 + a_1 \cdot f} = \frac{r_o}{1 + f}$$



$$A = 10 \quad f = 0.1 \quad a_1 = 50,000$$

$$f = 0.1 \cdot 50,000 = 5000 \quad r_o = 100\Omega$$

$$R_{out} = \frac{r_o}{1 + f} = 0.02 \Omega$$

Series-Shunt (Cont.)

FB-10

Gain Calculation :

$$R_{in} = \frac{v_o}{i_i}$$


$$v_o = (1 + \mathcal{F}) \cdot v_i$$

$$i_i = \frac{v_i}{r_c} = \frac{v_o}{(1 + \mathcal{F}) \cdot r_c}$$

$$R_{in} = \frac{v_o}{i_i} = (1 + \mathcal{F}) \cdot r_c$$

Shunt-Shunt (Transresistance v_{out}/i_{in})

FB-11

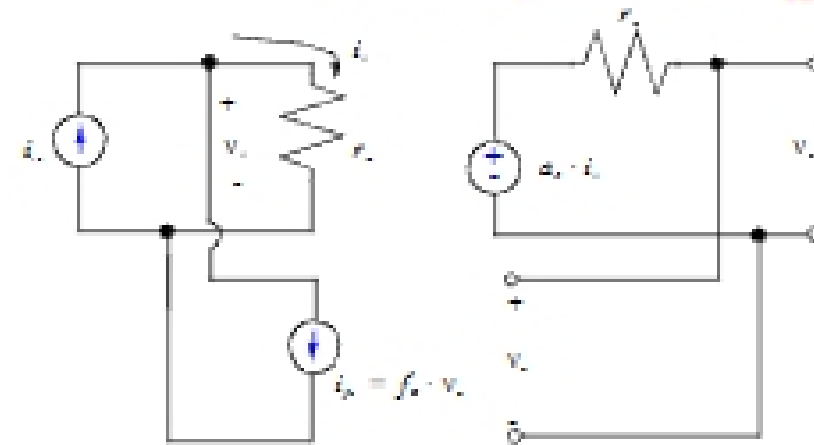

Shunt-Shunt (Cont.)

FB-13

Gain Calculation :

$$i_o = f_o \cdot v_o$$

$$f_o = \frac{i_o}{v_o}$$

$$i_i = i_c - i_o$$

$$v_o = a_o \cdot i_i$$

a_o has units of resistance

$$v_o = a_o \cdot (i_c - \underbrace{f_o \cdot v_o}_{i_o})$$

$$\frac{v_o}{i_c} = \frac{1}{f_o} \cdot \left(\frac{\mathcal{F}}{1 + \mathcal{F}} \right)$$

Shunt-Shunt (Cont.)

FB-14

