


**Filters:**


---

Since capacitors and inductors result in frequency dependent impedance elements, it is possible to create circuits that filter out (or pass) signal energy over a specified frequency region.

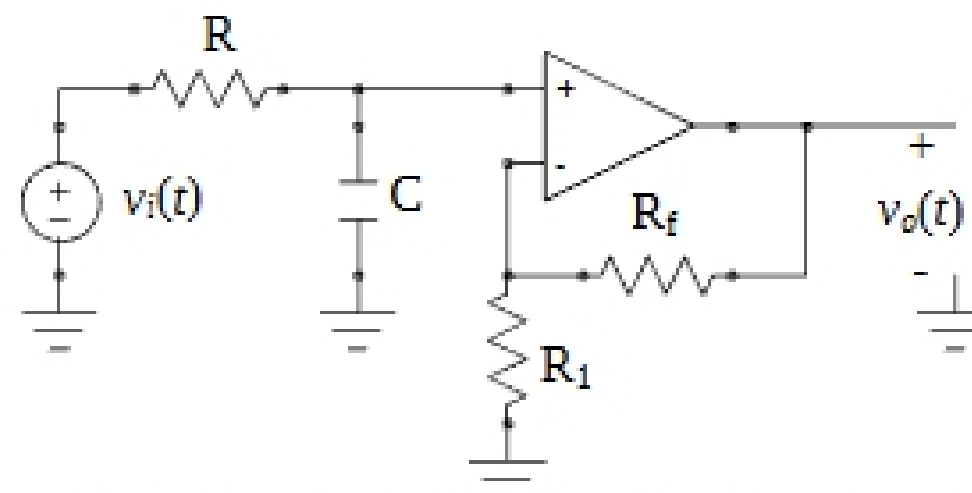**Example:**

Find the transfer function for the circuit below and sketch magnitude of the transfer function. Describe the filtering properties of this circuit with input  $v_i(t)$  and output  $v_o(t)$ :



Show that this filter can be described as a low-pass filter.

(i.e. as  $\omega \rightarrow \infty$ , then  $|H(j\omega)| \rightarrow 0$ , and as  $\omega \rightarrow 0$ , then  $|H(j\omega)| \rightarrow \text{Gain at DC} > 0$ ).

**Filtering Properties of Capacitive and Inductive Elements:**

---

Consider the impedance magnitudes of the capacitor and inductor as a function of  $\omega$ :

Capacitor:  $|\hat{X}_C| = \frac{1}{\omega C}$

Inductor:  $|\hat{X}_L| = \omega L$

- For higher frequencies the capacitor impedance acts more like a short circuit while the inductor impedance acts more like an open circuit.
- For lower frequencies the inductor impedance acts more like a short circuit while the capacitor impedance acts more like an open circuit.

*Describe the capacitor impedance at DC.*

*Describe the inductor impedance at DC.*

*What kind of filtering goes on for current passing through a capacitor?*

*What kind of filtering goes on for a voltage drop across a capacitor?*

*What kind of filtering goes on for current passing through an inductor?*

*What kind of filtering goes on for a voltage drop across an inductor?*

**Four Basic Filter Types:**

---

**The most common types of filters are listed below:**

- Low-pass
- High-pass
- Band-pass
- Band-reject (or notch)

### **Filter Terms:**

The **passband** of the filter refers to a range of frequencies that pass through the filter relatively unimpeded. The **stopband** of the filter refers to a range of frequencies that pass through the filter with relatively strong attenuation.

The **cut-off frequency** refers to a frequency that determines the end of the passband region. For the band-pass and band-reject filters there are 2 cut-off frequencies. The **3 dB cut-off (or half power) frequency** defines a cut-off frequency as the point where the magnitude to of the transfer function is 3 dB down from the maximum value of the transfer function.

### **Construction and Critical Design Parameters for the Four Basic Filter Types:**

---

**For all examples below assume voltage-input and voltage-output circuits:**