

Lecture 09: Filter Networks

Vijay Singh*

February 10, 2003

Abstract

Discussion of Low-pass filters, High-pass filters, Band-pass filters, Band-rejection filters.

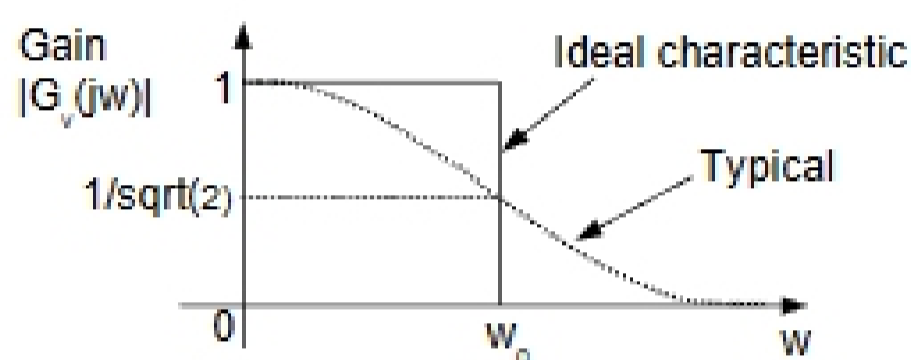


Figure 1: Low-pass filter.

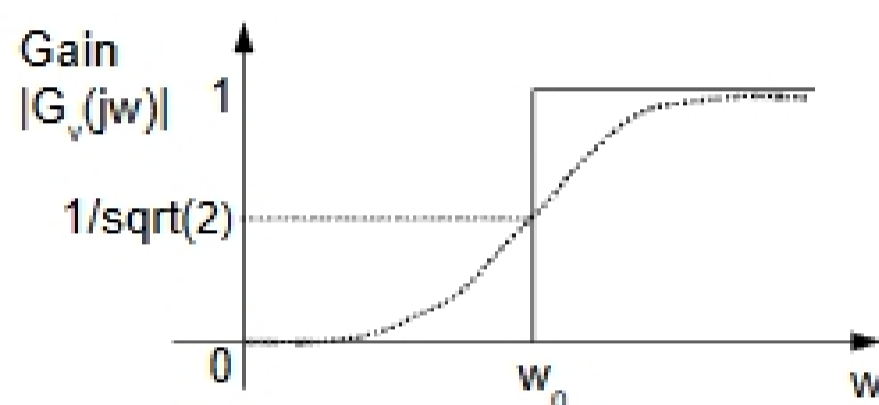


Figure 2: High-pass filter.

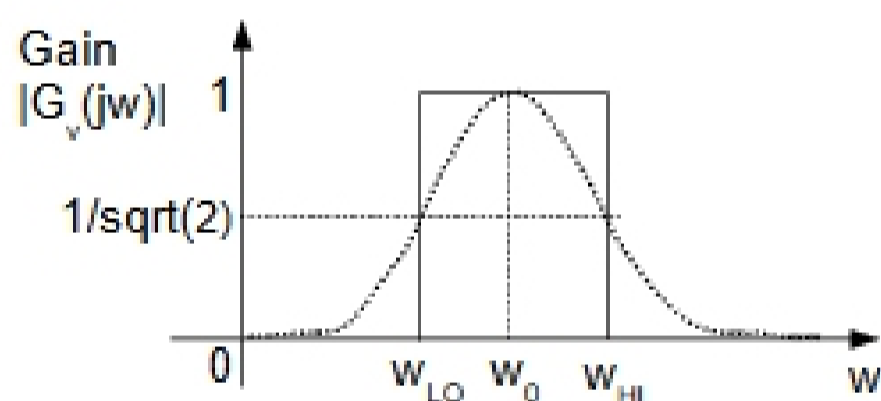


Figure 3: Band-pass filter.

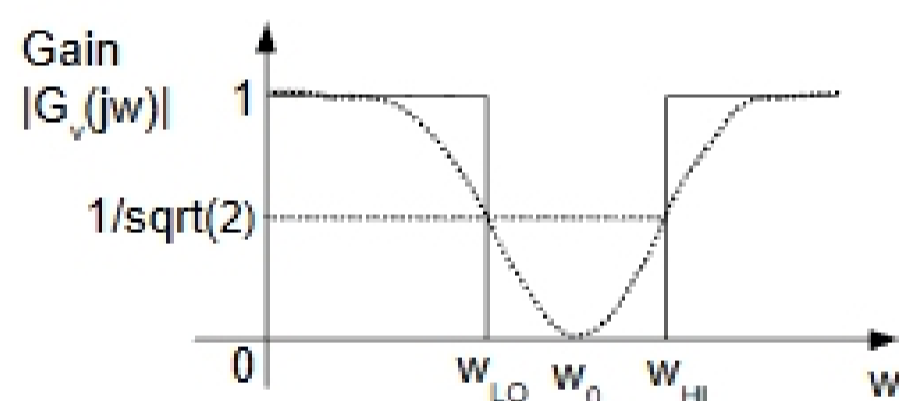


Figure 4: Band-rejection filter.

1 Low-pass filter network

A simple low-pass filter:

$$G_v(j\omega) = \text{gain} = \frac{V_O}{V_I} = \frac{1}{\frac{1}{j\omega C} + R}$$

*Professor and Chairman, Department of Electrical & Computer Engineering, University of Kentucky, Lexington, KY, USA. E-mail: vsingh@engr.uky.edu Lecture presented on February 10, 2003. Typeset in L^AT_EX

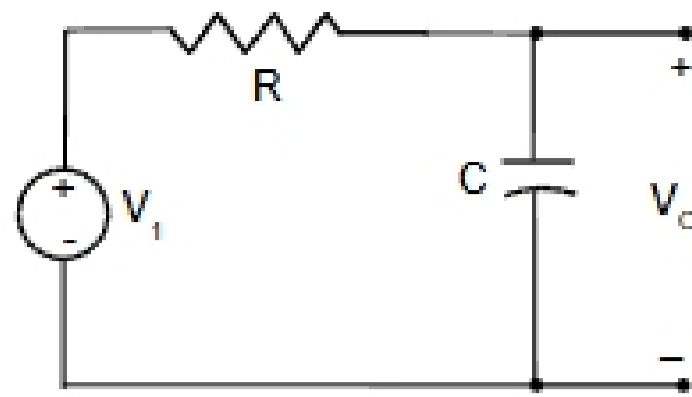


Figure 5: Low-pass filter.

$$G_V(j\omega) = \frac{1}{1 + j\omega RC} \quad (1)$$

$$= \frac{1}{1 + j\omega\tau} \quad (2)$$

where,

$$\tau = RC$$

$$\text{Amplitude: } M(\omega) = \frac{1}{\sqrt{1 + (\omega\tau)^2}} \quad (3)$$

$$\text{Phase: } \Phi(\omega) = -\arctan(\omega\tau) \quad (4)$$

At **break frequency** (also called **half-power frequency**), $\omega_b\tau = 1$, $\omega_b = \frac{1}{\tau}$

$$(M)_{\omega=\omega_b} = \frac{1}{\sqrt{2}} \quad (5)$$

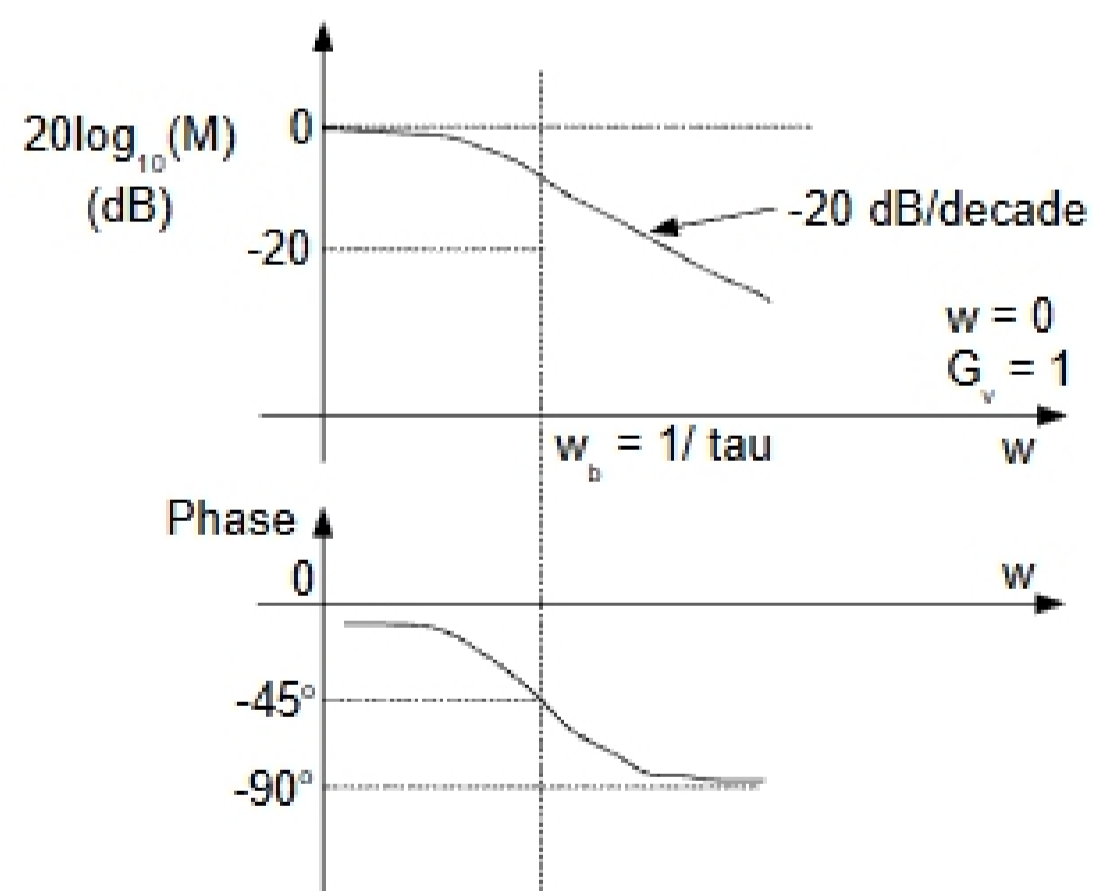


Figure 6: Low-pass filter characteristics.

2 High-pass filter network

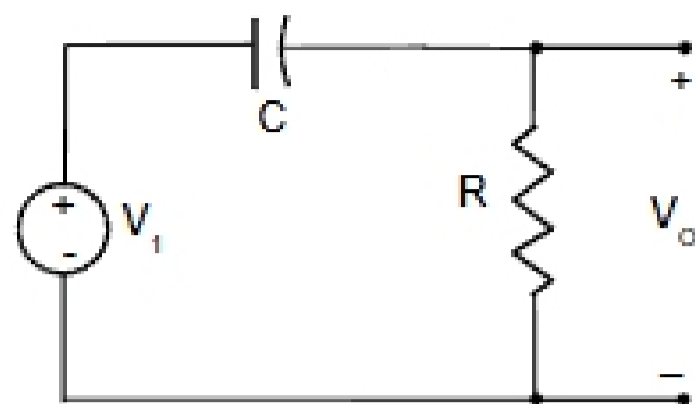


Figure 7: High-pass filter.

$$\begin{aligned} G_v(j\omega) &= \frac{R}{R + \frac{1}{j\omega C}} \\ &= \frac{j\omega RC}{1 + j\omega RC} \\ &= \frac{j\omega\tau}{1 + j\omega\tau}; \quad \tau = RC \\ M(\omega) &= \frac{\omega\tau}{\sqrt{1 + (\omega\tau)^2}} \end{aligned}$$

$$\Phi(\omega) = \frac{\pi}{2} - \arctan(\omega\tau)$$

$$\text{Half-power frequency} = \omega_b = \frac{1}{\tau}$$

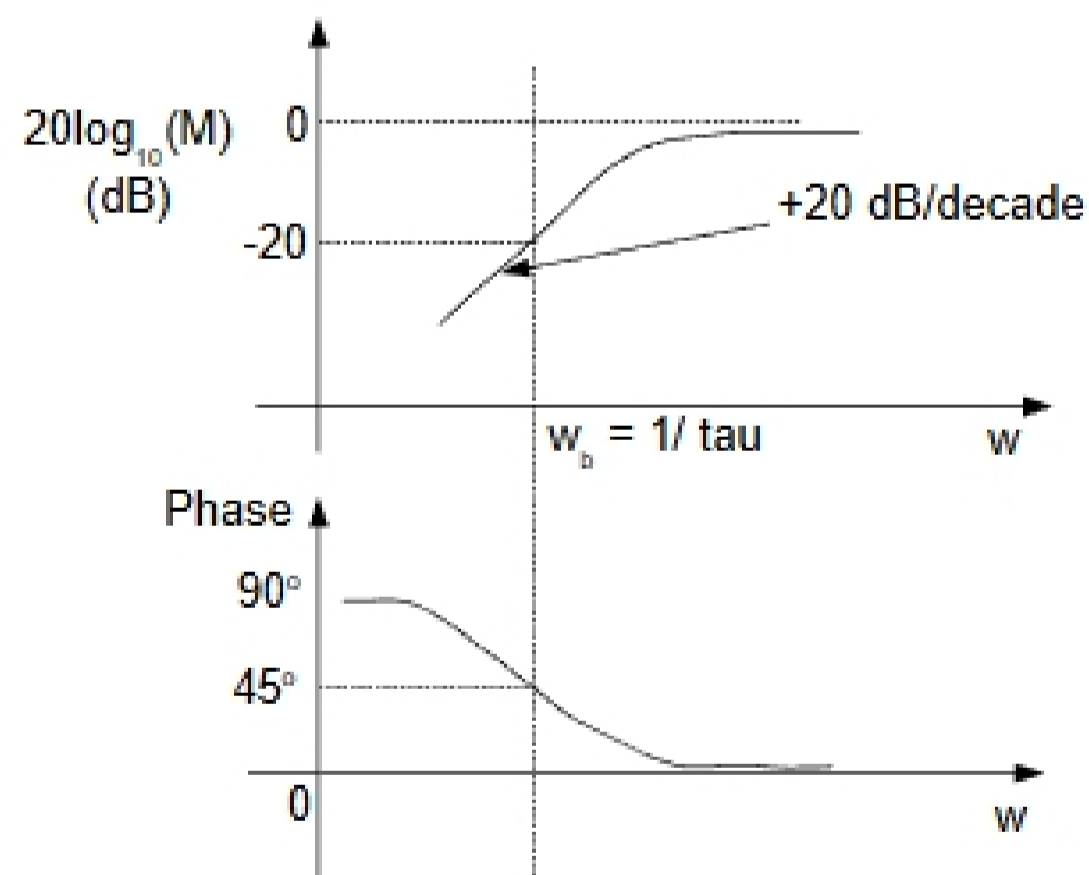


Figure 8: High-pass filter characteristics.