

Design Project #1: Matching Transformers

In this project you will design and test **three** matching networks:

- a) A Quarter-wave transformer
- b) A 4-section Binomial transformer
- c) A 4-section Chebychev transformer

PROJECT SCOPE

In this design, we will attempt to match a real load of $R_L = 120\Omega$ to a transmission line with a 50Ω characteristic impedance at a frequency of 4.0 GHz.

The **bandwidth** of the 4-section transformers is defined by $\Gamma_m = 0.2$.

Assume TEM wave propagation in the transmission lines, and the transmission line dielectric constant is $\epsilon_r = 16.0$.

PROJECT TASKS

- 1) **Design** each of the three matching networks, determining both the **characteristic impedance** and **physical length** (in cm) of each section.
- 2) Use the design equations in your notes/book to **determine** the **expected bandwidth** for each design.
- 3) **Implement** each design on **ADS** software. **Analyze** the circuit by evaluating $\Gamma_{in}(\omega)$ from **0 to 8 GHz**. **Display** the results as (make sure you use **enough frequency points—at least 100**—in the analysis!):
 - a) a Smith Chart plot of $\Gamma_m(\omega)$. Note this is a **parametric** plot of reflection coefficient Γ_m as a function of **frequency**—not as a function position (i.e., **not** $\Gamma(z)$!).

b) a Cartesian plot of $|\Gamma_{in}(\omega)|$ versus frequency (i.e., linear scale).

c) a Cartesian plot of $10 \log_{10} |\Gamma_{in}(\omega)|^2$ versus frequency (i.e., dB scale). Make sure that you use a log scale that makes sense (e.g., 50 dB from top to bottom).

Q1: Do the plots indicate that your designs are correct? Explain why you think so. Give specific numerical examples.


Q2: Observe the parametric plot $\Gamma_{in}(\omega)$ on the Smith Chart. Use the adjustable markers to determine at what frequencies the curve is far from the center of the chart, and at what frequencies the curve is near the center. Explain why this result makes sense.

Q3: Likewise determine the frequencies at which the parametric Smith Chart plot of $\Gamma_{in}(\omega)$ is precisely at the center of the chart (i.e., the curve intersects the center point). Explain why this result makes sense. Locate these same frequencies on the Cartesian plots. What are the values of $|\Gamma_{in}(\omega)|$ and $10 \log_{10} |\Gamma_{in}(\omega)|^2$ at these frequencies? Explain why this result makes sense.

4) Use the adjustable markers on the plots to determine the bandwidth of each design.

Q4: You will find that the bandwidths of your design will not be exactly the bandwidths predicted by the design equations. Explain why that is. Hint: It is not because "ADS has errors"!

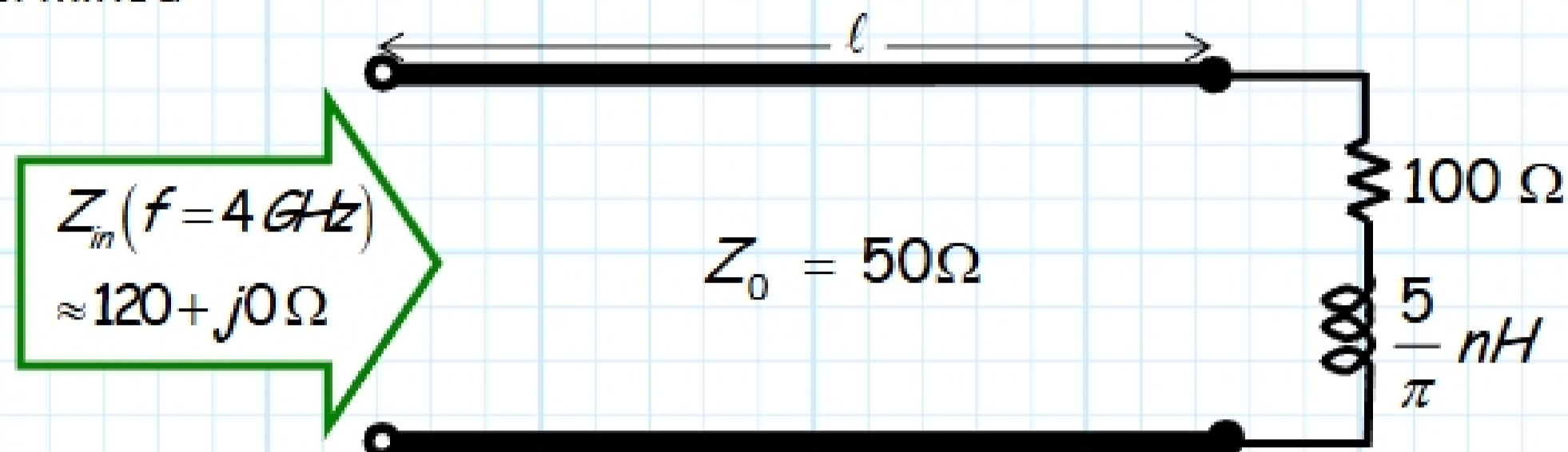5) You will find that at $f = 4 \text{ GHz}$, the following device has an input impedance of approximately $Z_{in} \approx 120 + j0 \Omega$ if the length ℓ is properly determined:



6) **Determine** the proper value for line length ℓ . Now **replace** the 120Ω resistor with this 120Ω "load" shown above, and **reanalyze** (with ADS) each matching transformer design.

7) **Display** the results of this new load on the same three plots (with the same scale!) as described in step 3.

Q5: *Compare and contrast these results with the 120 Ohm resistor plots. How are the results different? Determine the frequencies where the value of $\Gamma_{in}(\omega)$ is precisely the same for the two cases. Explain why is this true.*

PROJECT REPORT

1. You basically should view the project report as a **lab report**. **Show how** and why the design parameters were determined. "Construct" the circuits in ADS, and then "measure" the circuits in ADS. Provide the results of these "measurements" in report. **Discuss** your results, and include the answers to the questions posed earlier (put particular emphasis on the answers to questions with the word "why"!).

2. Assume your audience is a **knowledgeable microwave engineer** (i.e., me!) Thus, you do not need to provide a long (or even short) discussion about what matching networks are, or why they are so great, or what their general characteristics are, or a multiple reflection analysis of