

Lecture 3: State Machine Review


- Sequential Logic
- Control and data interaction
- ASM Chart
- Examples
- Mealy vs Moore

Announcement


- Project 0 posted on sakai, flowchart and question answers due next Monday
- Please send your group information to lubo@udel.edu

Sequential Logic

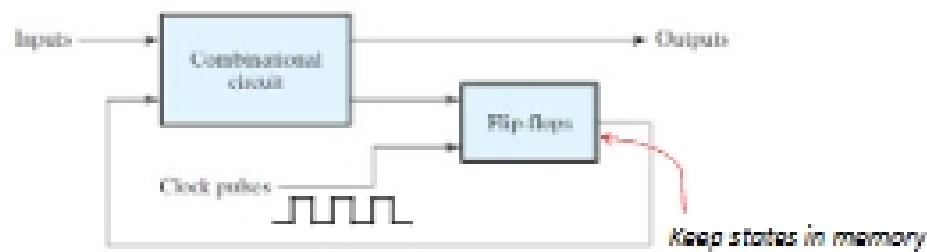Synchronous circuit = clocked sequential circuit




EX: CLK

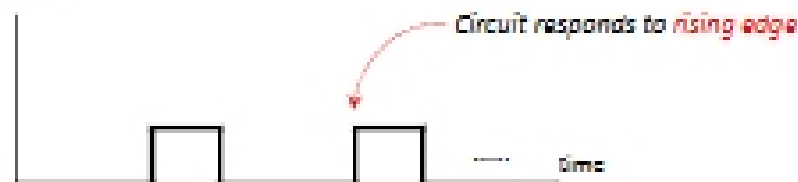

Control and data interaction

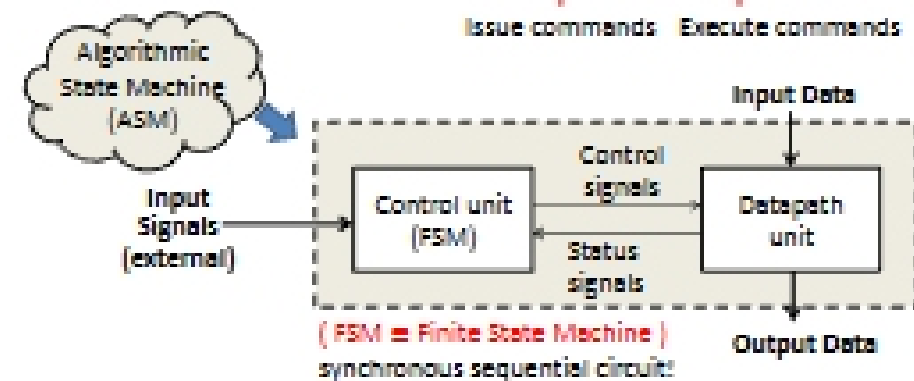
➤ Digital systems use binary info for either **control** or **data processing**



- ① Control logic { Sends commands
Receives status } "Master"
- ② Datapath logic { Executes commands
Reports status } "Slave"

How to Design Your System?

Basic idea:

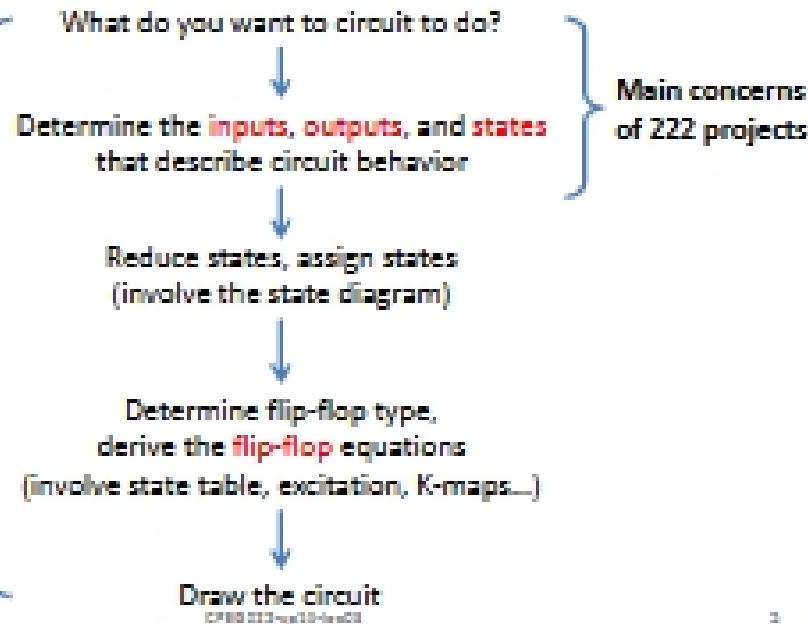


Sequential logic synthesis covered in 202

Serial 2's complemter

Example Serial 2's complemter (Mealy version) ...10100 → ...01100

- 2's complement is formed by :
- (1) Until first 1 occurs, output = input
 - (2) When first 1 occurs, output = input'
- Two STATES


State Diagram

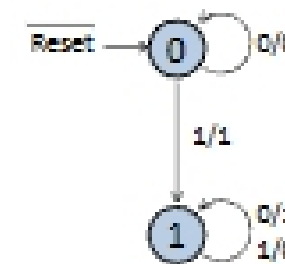

Algorithm


- No toggle state (initial state)
If $x = 0$, stay in state and $y = x$
If $x = 1$, go to toggle state
- Toggle state
Stay in state and $y = x'$

Flow chart

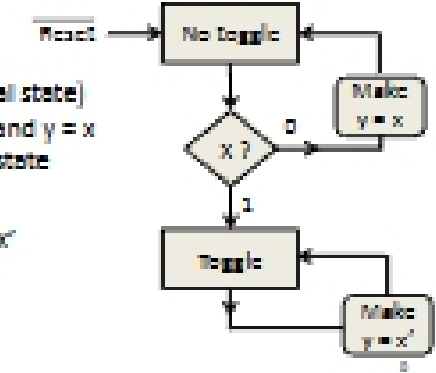

ASM Chart

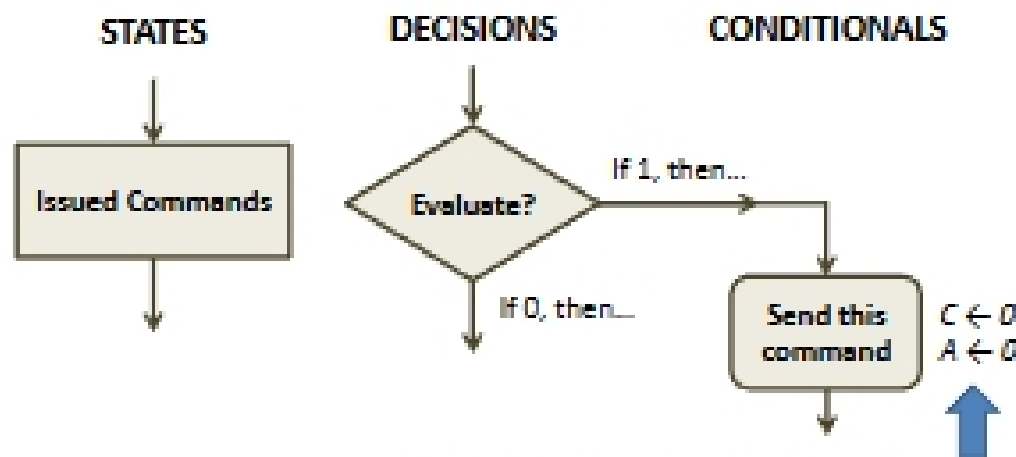➤ ASM chart is basically a flow chart with details of :




The **datapath** actions are written on the side

Robot Controller

Another example Robot controller

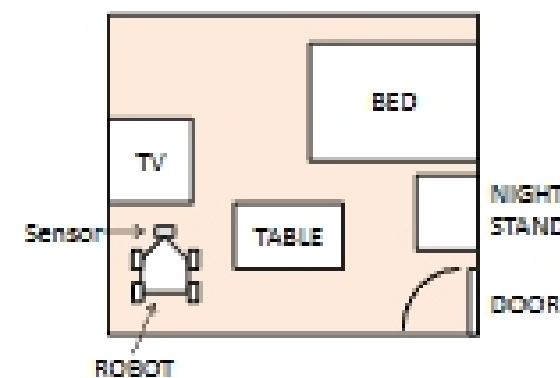Design problem: Design a finite state controller for a robot so that it overcomes obstacles.




Requirements:

- Sensor output = 1 if there is an obstacle
- Control lines $\left\{ \begin{array}{l} L = 1 \text{ (Left)} \\ R = 1 \text{ (Right)} \end{array} \right.$
- When an obstacle is detected, the robot should turn **right** until no obstacle is detected.
The next time an obstacle is detected, turn **left** until no obstacle is detected.
And so on...

Robot Controller

➤ **STEP 1:**

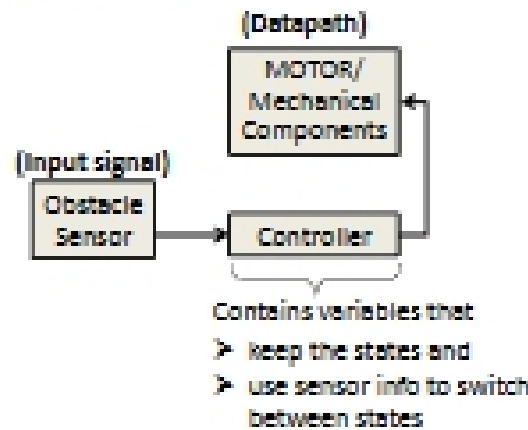Good place to start is the **block diagram** for the robot operation



From requirements, the robot requires **4** states:


- (A) Straight (previous turn = left)
- (B) Turn right
- (C) Straight (previous turn = right)
- (D) Turn left

- Input is $S = 0$ or 1 ← Obstacle detected
- Outputs are $L = 0$ or 1 ← Turn left
- $R = 0$ or 1 ← Turn right

Robot Controller


➤ **STEP 2:**

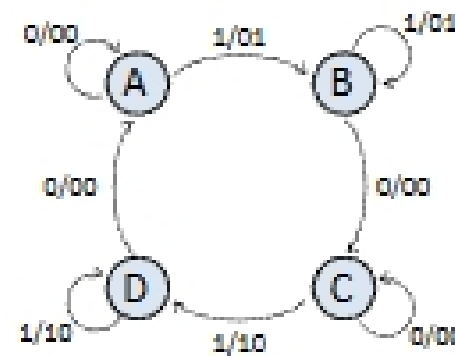Now that we have our states, construct the state diagram



Is this **Mealy** or **Moore**?

Algorithmic State Machine

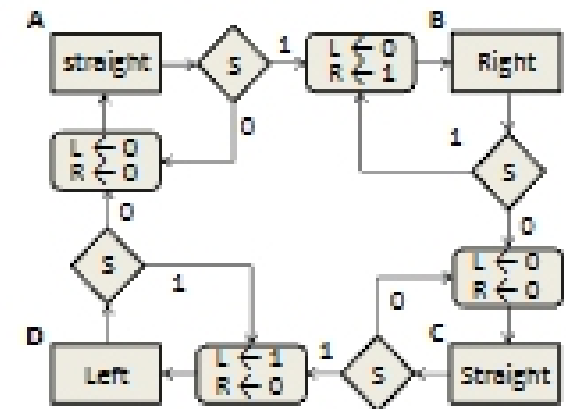

Notation: $L \leftarrow 0$ means "0" appears at the output of "L"

Mealy vs. Moore

Mealy & Moore: 2 different types of sequential systems

