
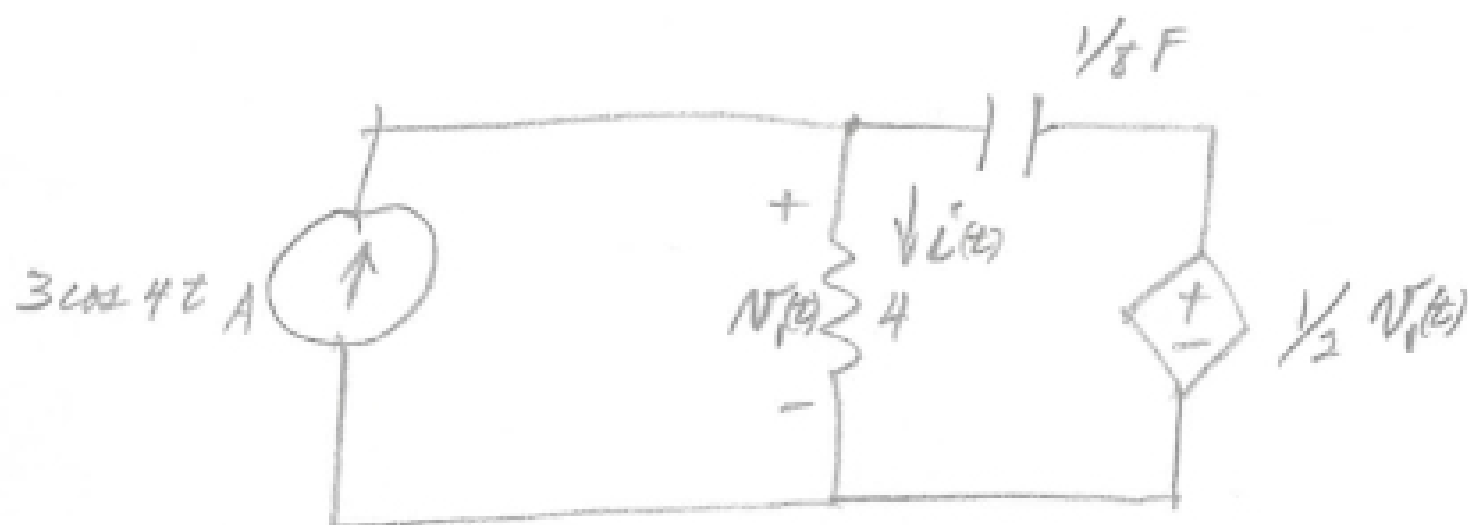


## Circuits with dependent sources

find  $i(t)$ :

a) Get phasor circuit

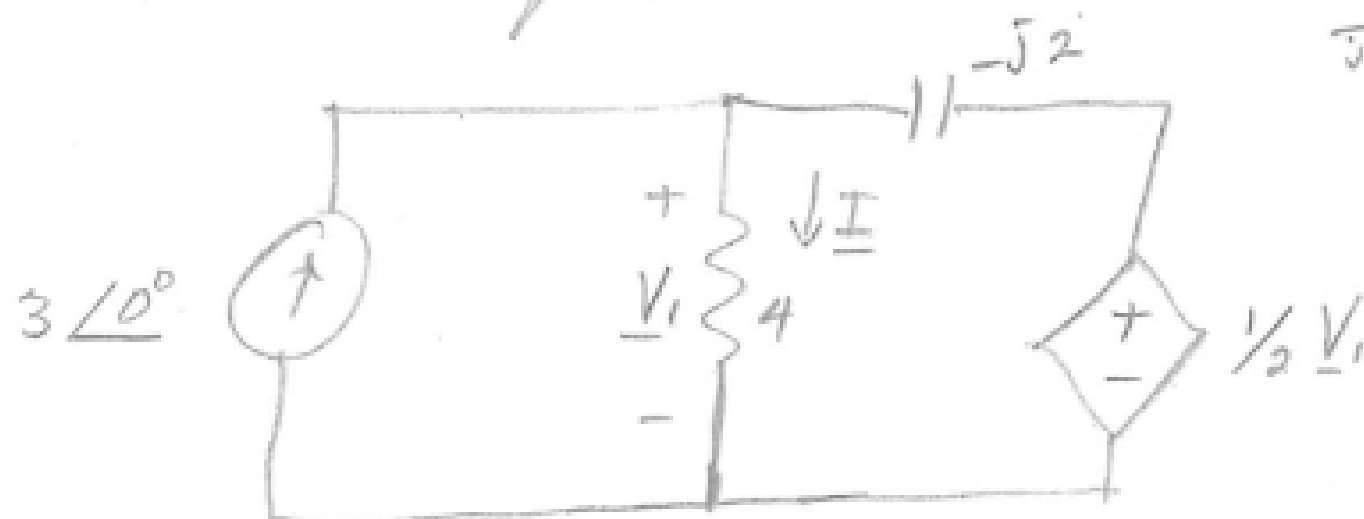

$$\frac{1}{j\omega C} = \frac{1}{j(4)\frac{1}{8}} = -j2$$

$$\text{KCL: } -3 \angle 0 + \underline{I} + \frac{V_1 - \frac{1}{2} V_1}{-j2} = 0$$

$$\text{also } \underline{V}_1 = 4 \underline{I}$$

$$\therefore \underline{I} + \frac{2 \underline{I}}{-j2} = 3 \angle 0^\circ$$

$$(1 + j1) \underline{I} = 3 \angle 0^\circ$$


$$\underline{I} = \frac{3 \angle 0^\circ}{\sqrt{2} \angle 45^\circ} = \frac{3}{\sqrt{2}} \angle -45^\circ$$

$$\therefore i(t) = \frac{3}{\sqrt{2}} \cos(4t - 45^\circ) \text{ A}$$

11.1


# Example of nodal analysis

1.

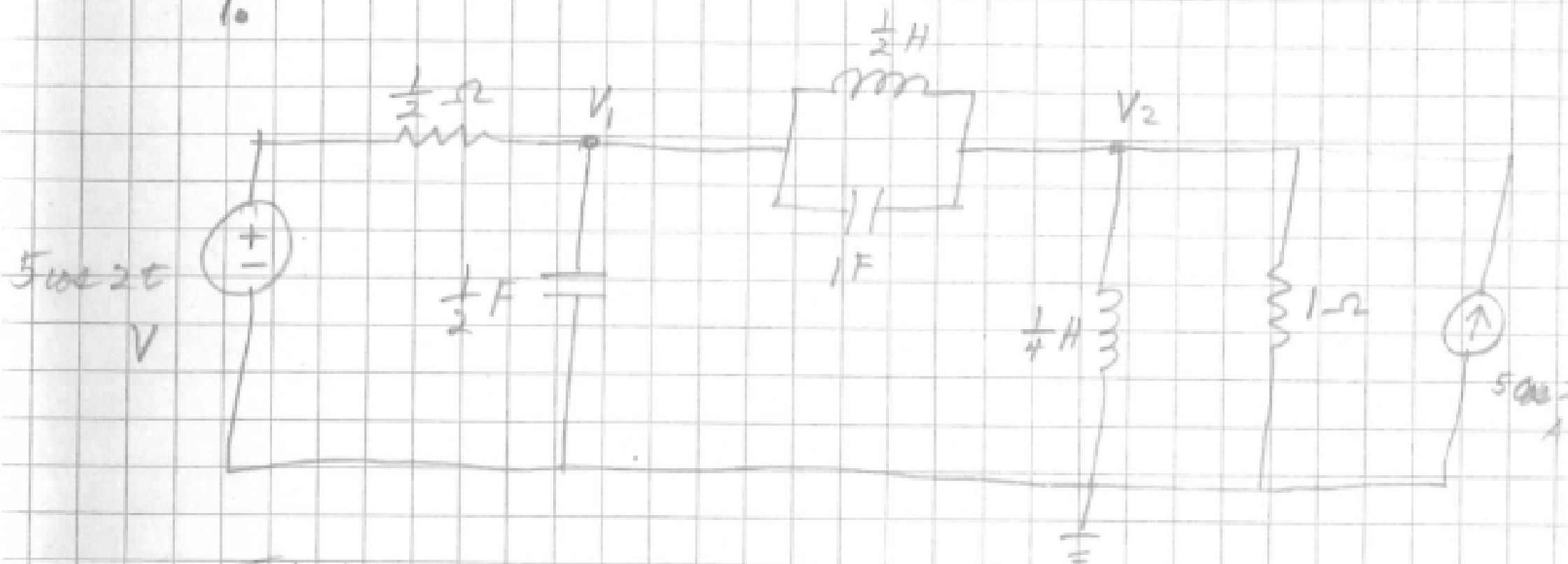


Find  $i_1(t)$  and  $v_2(t)$

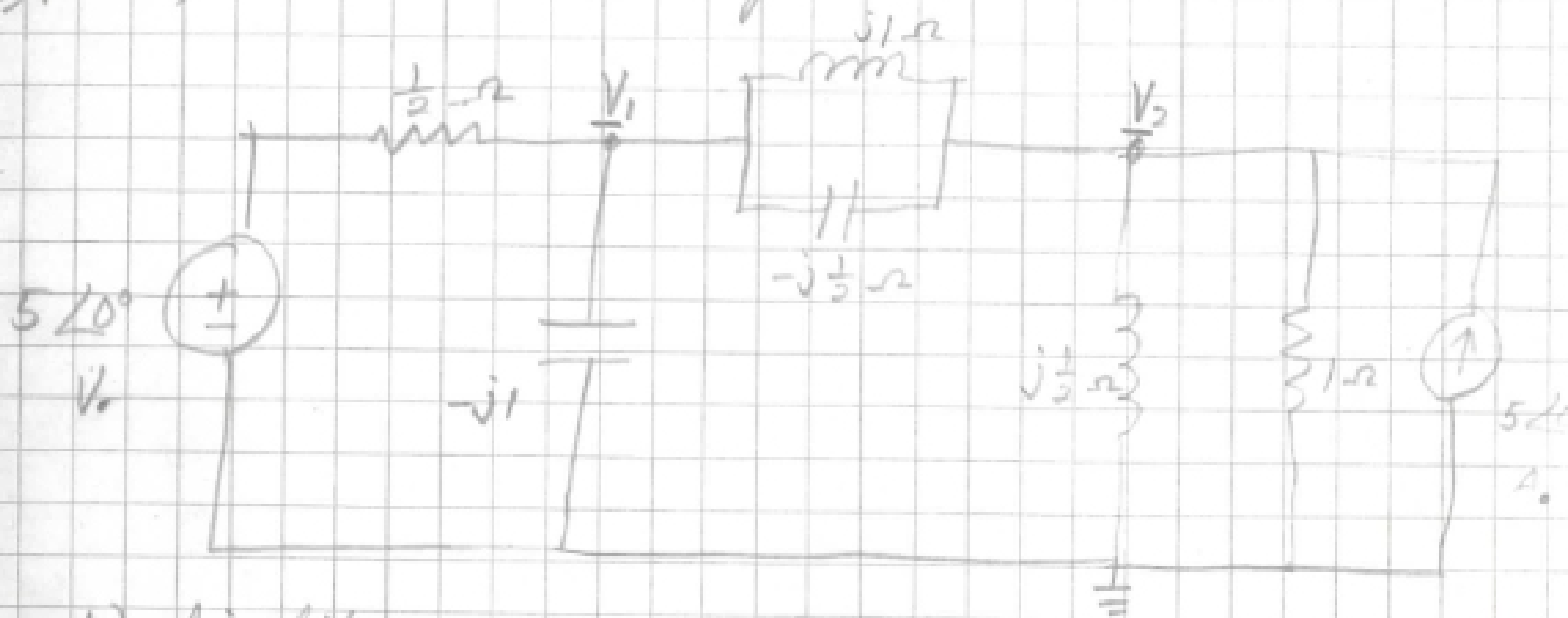$\omega = 7$  a) Go to the phasor circuit



b) simplify

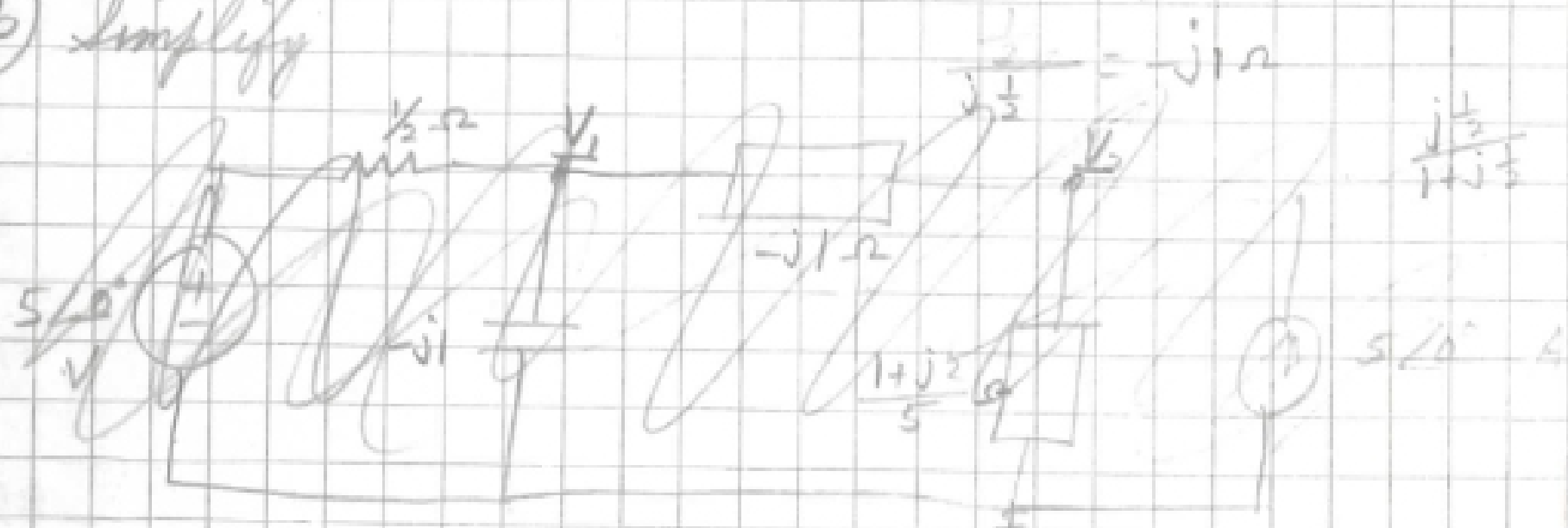

Q1:

$$\frac{V_1 - 5}{1/2} + \frac{V_1}{-j1} + \frac{V_1 - V_2}{j1} + \frac{V_1 - V_2}{-j1/2} = 0$$

Q2:  $\frac{V_2 - V_1}{j1} + \frac{V_2 - V_1}{-j1/2} + \frac{V_2}{j1/2} + \frac{V_2}{1} - 5 = 0$

Simplify

$$2V_1 - 10 + \cancel{jV_1} - \cancel{jV_1} + jV_2 + j2V_1 - j2V_2 = 0$$

$$-jV_2 + jV_1 + \cancel{j2V_2} - j2V_1 - \cancel{j2V_2} + V_2 - 5 = 0$$

$$\begin{bmatrix} 2 + j2 & -j1 \\ -j1 & 1 - j1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 5 \end{bmatrix}$$