

Lecture 6w: Frequency Response Inspection Analysis I


Lecture 6: Frequency Response Inspection Analysis

- Announcements:
- This is our make-up lecture
- We will have lecture tomorrow (Tuesday), as well, at our regular time and place
- Lecture Topics:
 - ⇒ Amplifier Bode plot
 - ⇒ Open Circuit Time Constant (OCTC) Analysis
 - ⇒ Frequency Response Inspection Analysis
 - ⇒ Frequency Response Examples

• Last Time:

Mos Inspection Formulas w/ Substrate Grounded

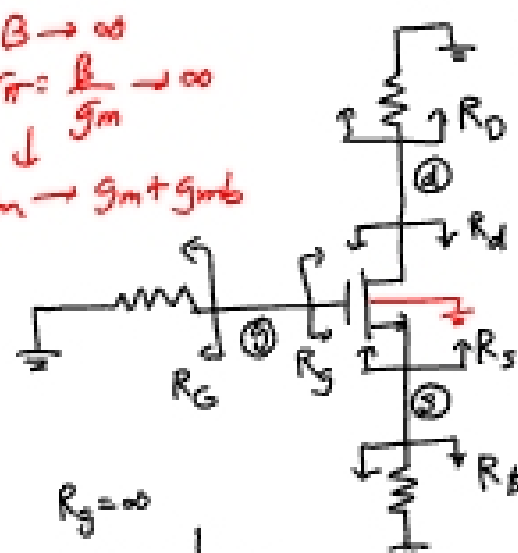$\beta \rightarrow \infty$
 $r_{\pi} = \beta / g_m \rightarrow \infty$
 \downarrow
 $g_m \rightarrow g_m + g_{mb}$



$$R_g = \infty$$

$$R_s = \frac{1}{g_m + g_{mb}}$$

$$R_d = r_o [1 + (g_m + g_{mb})R_B]$$

only difference from substrate tied to source case is that g_m is replaced by $g_m + g_{mb}$ in some of the formulas particularly over where the source is involved!

over


$$\frac{N_d}{N_g} = -G_m R_{\text{out}}, \quad G_m = \frac{g_m}{1 + (g_m + g_{mb})R_B}$$

$$\frac{N_d}{N_s} = -G_m R_{\text{out}}, \quad G_m = -(g_m + g_{mb})$$


$$\frac{N_s}{N_o} = \frac{g_m R_B}{1 + (g_m + g_{mb})R_B}$$

Remark: When the substrate is tied to the source, $g_{mb} = 0$.

Effect of g_{mb} (one more example)

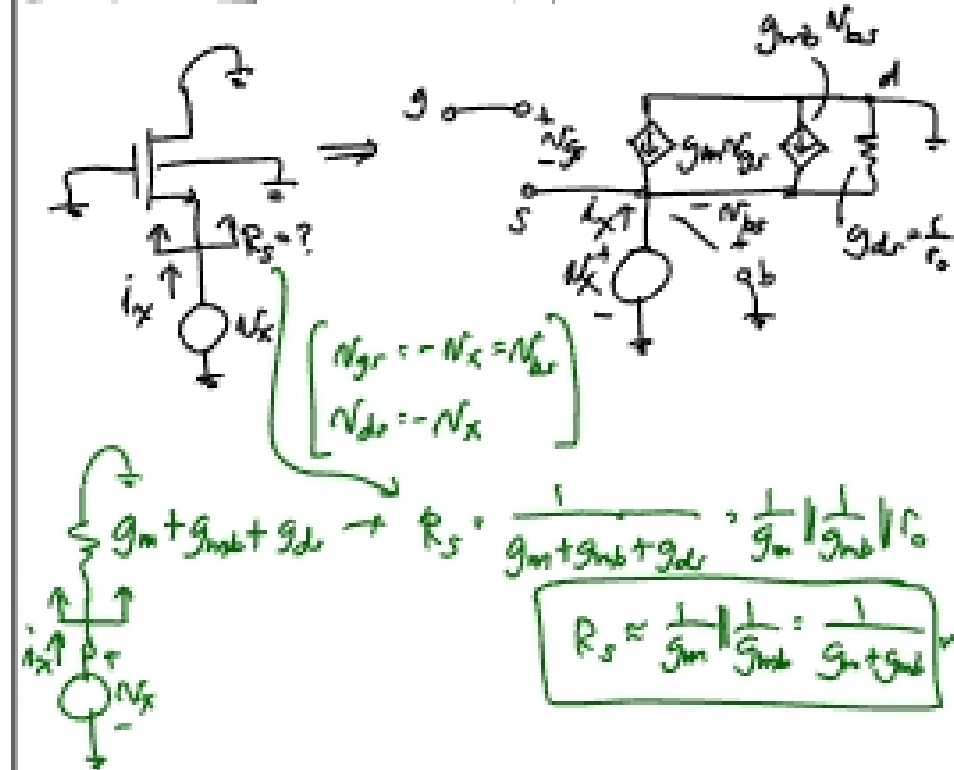

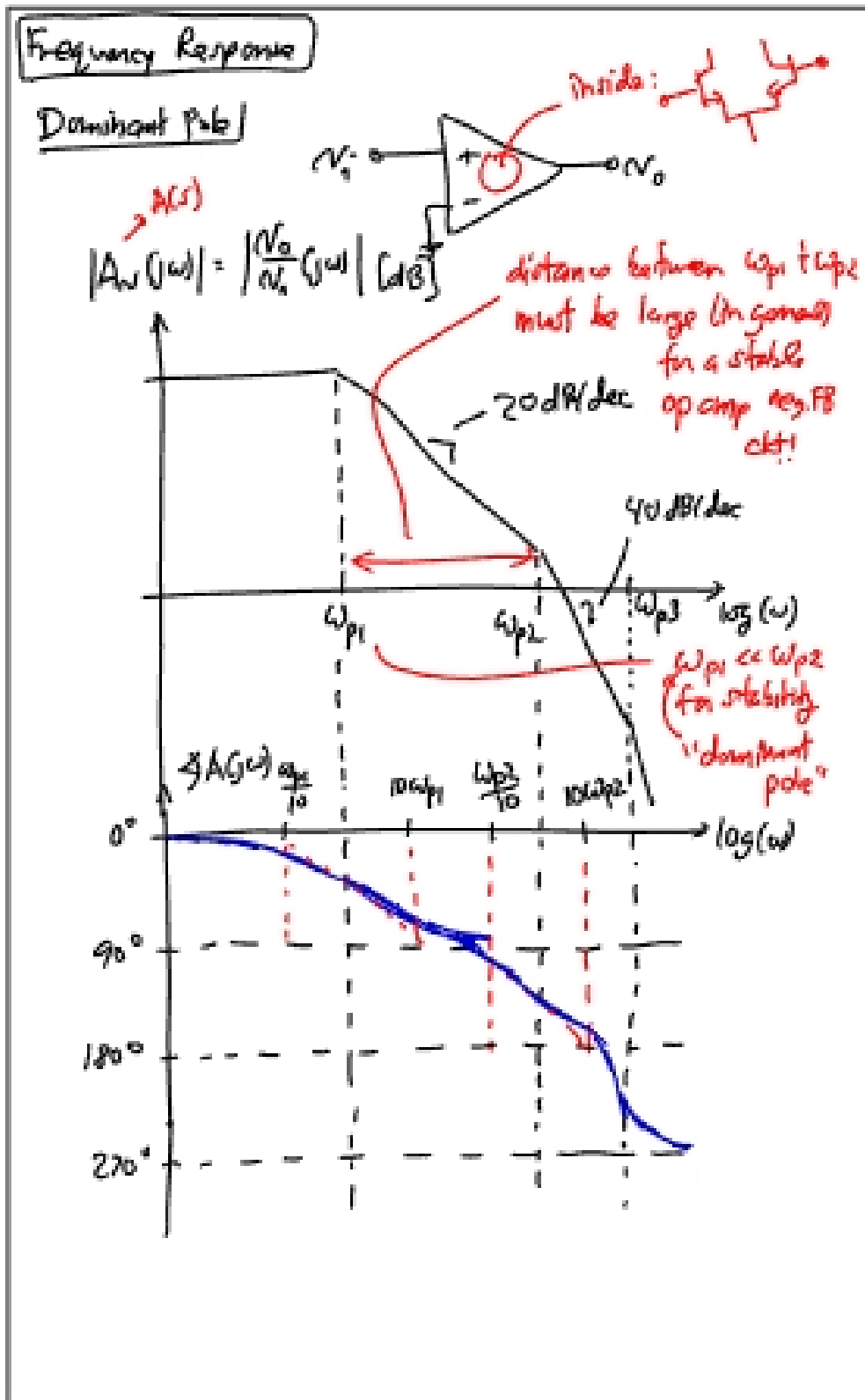Lecture 6w: Frequency Response Inspection Analysis I




Freq Response

Recall that the transfer function of a general amplifier can be expressed as a function of frequency via:

$$A(s) = A_M F_L(s) F_H(s)$$

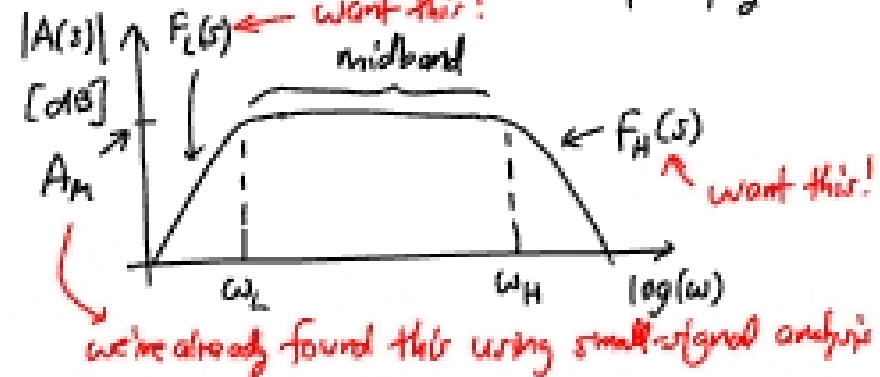midband gain \uparrow high frequency shaping \uparrow low freq. shaping



High freq. Response Determination Using Open Ckt. Time Constant (OCTC) Analysis

In general:

$$F_H(s) = \frac{1 + a_1 s + a_2 s^2 + \dots + a_{n_z} s^{n_z}}{1 + b_1 s + b_2 s^2 + \dots + b_{n_p} s^{n_p}}$$

n_z poles \downarrow zeros \uparrow
 $n_p = n_z$

$$= \frac{\prod_{j=1}^{n_z} \left(1 - \frac{s}{z_j}\right)}{\prod_{i=1}^{n_p} \left(1 - \frac{s}{p_i}\right)} = \frac{\prod_{j=1}^{n_z} \left(1 + \frac{s}{\omega_{zj}}\right)}{\prod_{i=1}^{n_p} \left(1 + \frac{s}{\omega_{pi}}\right)}$$

from which:

$$b_1 = \frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} + \dots + \frac{1}{\omega_{pn_p}} = \sum_{i=1}^{n_p} \frac{1}{\omega_{pi}} = \sum_{k=1}^{n_p} \tau_{pk}$$

\uparrow coeff. of the 1st order term

time constant

Lecture 6w: Frequency Response Inspection Analysis I

Through network theory, one can prove that: (see Gray & Meyer, Chpt. 7)

$$\sum_{i=1}^{np} \tau_{pi} = \sum_j C_j R_{j0} = \sum_j \tau_{j0}$$

where C_j are capacitors in the H.F. ckt., i.e., small ones
 $R_{j0} \triangleq$ driving pt. resistance seen between the terminals of C_j determined with

- ① all small (< 1nF) capacitors open-circuited
- ② all independent sources eliminated (i.e., short voltage sources, open current sources)
- ③ short all large (coupling/bypass) capacitors (i.e., > 1µF or > 1µF)

In calculating the H.F. response, we use the dominant pole approximation:

(i) $\omega_{p1} \ll \omega_{p2}, \dots, \omega_{pnp}$ ← n poles

$$F_H(s) \cong \frac{1}{1 + \frac{s}{\omega_H}}$$

(ii) $b_1 \cong \frac{1}{\omega_{p1}} \rightarrow \omega_H = \omega_{p1} \cong \frac{1}{b_1} = \frac{1}{\sum_j \tau_{j0}} = \frac{1}{\sum_j C_j R_{j0}}$

When there is no dominant pole, an approximate expression for ω_H is:

$$\omega_H \approx \frac{1}{\sqrt{\frac{1}{\omega_{p1}^2} + \frac{1}{\omega_{p2}^2} + \dots - \frac{1}{\omega_{z1}^2} - \frac{1}{\omega_{z2}^2} - \dots}}$$

(just FYI)

Example: H.F. Analysis of a C.E. Ckt.

