

Logistics:

- I will miss Thursday, Feb. 12
- Make up lecture time:
 ↳ Tonight, Tuesday, 7 p.m., 247 Cory

Today:

- High Frequency Cut-Off Examples
- Short-Circuit Time Constant Analysis for Low Frequency Cut-Off


Problem 1(c)

$R_i = \frac{v_x}{i_x}$
 $i_c = (\beta + 1)i_b$
 $i_x = i_b + i_{be}$
 $v_x = i_x(r_{\pi} || R_{BE}) + [(\beta + 1)i_b + i_x - i_b]R_E$
 $i_b = i_x \left(\frac{R_{BE}}{r_{\pi} + R_{BE}} \right)$ (Current Divider)
 $v_x = i_x \left[(r_{\pi} || R_{BE}) + \left[\beta \left(\frac{R_{BE}}{r_{\pi} + R_{BE}} \right) + 1 \right] R_E \right]$

$R_i = \frac{v_x}{i_x} = (r_{\pi} || R_{BE}) + (\beta' + 1)R_E$
 $\beta' = \beta \left(\frac{R_{BE}}{r_{\pi} + R_{BE}} \right)$

Input Resistance Formula:

$R_i = \underline{v_{\pi} + (\beta + 1)R_E} \approx \underline{v_{\pi}(1 + g_m R_E)}$
 $R_i = (r_{\pi} || R_{BE})(1 + g_m R_E)$
 $= (r_{\pi} || R_{BE}) + g_m \left(\frac{R_{BE}}{r_{\pi} + R_{BE}} \right) R_E$
 $= (r_{\pi} || R_{BE}) + \beta \left(\frac{R_{BE}}{r_{\pi} + R_{BE}} \right) R_E$

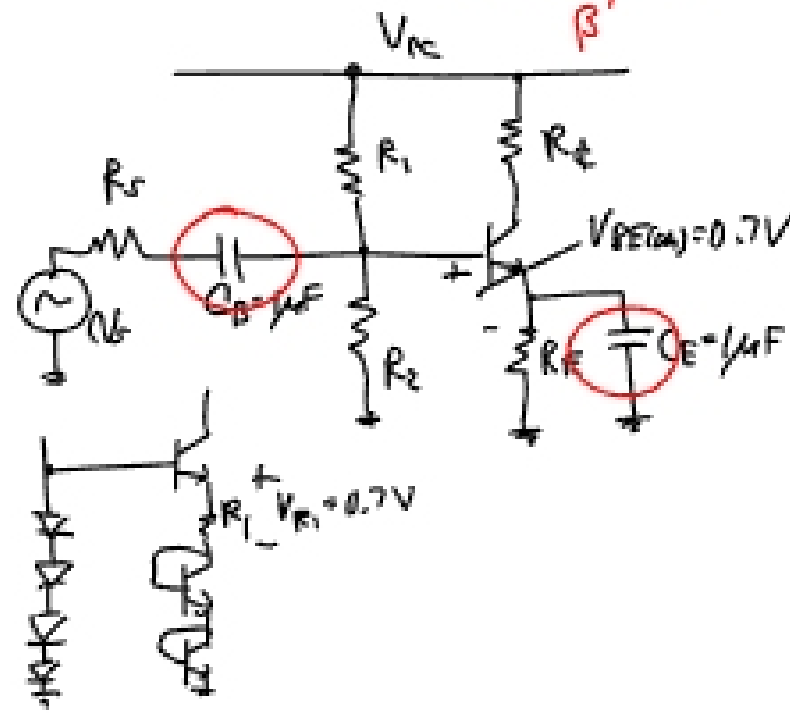

Last Time - OCTC

Find $\tau_{(1)}$:

$$R = \frac{N_x}{I_x} = r_{\pi} \parallel R_C \parallel R_B$$

$$\tau_{(1)} = C_{\pi} (r_{\pi} \parallel R_C \parallel R_B)$$

Find $\tau_{(2)}$: replace C_{μ} w/ N_x use inspection formula "linear in-shunt"

$$R_{xo} = \frac{N_x}{I_x} = R_C + R_B + g_m R_E$$

$$R_{\mu o} = R_s \parallel R_B \parallel r_{\pi} + r_{\mu} \parallel R_C + g_m (R_C \parallel R_B \parallel r_{\pi}) (C_{\mu} \parallel R_E)$$

$$\tau_{\mu o} = R_{\mu o} C_{\mu}$$

Find $\tau_{(3)}$:

$$\tau_{(3)} = C_{cs} (r_{\mu} \parallel R_C) \approx C_{cs} R_C$$

$$\omega_H = \frac{1}{\tau_{(1)} + \tau_{\mu o} + \tau_{(3)}}$$

Now, use Miller's Theorem

$$C_{\mu}(1-av) = C_{\mu}(1+g_m R_E)$$

$$\tau_{(1)} = (r_{\pi} \parallel R_C \parallel R_B) (C_{\pi} + C_{\mu}(1+g_m R_E))$$

$$\tau_{(2)} = R_C (C_{\mu} + C_{cs}) \quad \omega_H = \frac{1}{\tau_{(1)} + \tau_{(2)}}$$

Multi-Stage Ex.

$$\tau_{(1)} = (2r_{\pi} \parallel R_C) C_{\mu 1}$$

$$\tau_{(2)} = C_{\mu 1} \left(r_{\mu 1} \parallel \frac{R_s + \frac{1}{g_{m2}}}{1 + g_{m1}(\frac{1}{g_{m2}})} \right)$$

$$\tau_{(3)} = C_{\mu 2} \left[\left(\frac{1}{g_{m1}} + \frac{R_s}{\beta_{T1}} \right) \parallel \frac{1}{g_{m2}} \parallel R_{EE} \right]$$

$\tau_{\text{out}} = (C_{gs2} + C_{gs1}) R_{\text{out}}$

$$\omega_H = \frac{1}{\tau_{\text{out}} + \tau_{\text{in}} + \tau_{\text{out}} + \tau_{\text{out}}}$$

MOS Two-Stage Amplifier

Step 1: Eliminate caps.
Step 2: Determine the constants.

$\tau_{\text{in}} = [C_{gs1} + C_{gs1}(1 + g_{m1}R_{ds1})] R_s$

$\tau_{\text{out}} = [C_{gd1} + C_{db1} + C_{gd2}] (r_{o1} \parallel R_{ds1}) \sim R_{ds1}$

$\tau_{\text{out}} = C_{db2} \left(\frac{1}{g_{m2} + g_{mb2}} \parallel R_{ds2} \right)$

$\tau_{gs2} = C_{gs2} \left(\frac{R_{ds1} + R_{re}}{1 + (g_{m2} + g_{mb2})R_{re}} \right)$

$$\omega_H = \frac{1}{\tau_{\text{in}} + \tau_{\text{out}} + \tau_{\text{out}} + \tau_{gs2}}$$

Low Freq. Amplifier Response Using Short Circuit Time Constant Analysis (SCTC)

Recall:

In general, for the low freq. response:

$$F_L(s) = \frac{s^{n_z} + d_1 s^{(n_z-1)} + \dots}{s^{n_p} + e_1 s^{(n_p-1)} + \dots}$$

n_z = # poles = # zeros

We can express the coefficient e_1 by:

$$e_1 = \omega_{p1} + \omega_{p2} + \dots + \omega_{pn}$$

For the case of a dominant pole:
i.e., the highest freq. pole

Similar analysis to that used for OCTC...

$$F_L(s) \approx \frac{s}{s + \omega_{p1}} = \frac{s}{s + e_1} \rightarrow e_1 \approx \omega_{p1} = \omega_L$$

$$\omega_L \approx e_1 = \sum_j \omega_{pj} = \sum_j \frac{1}{C_j R_{j_s}} = \sum_j \frac{1}{\tau_{j_s}}$$

where $C_j \triangleq$ various large (> 10 nF) capacitors in the ckt. (e.g., the bypass caps.)

$R_{j_s} \triangleq$ driving point resistance seen between the terminals of C_j determined with:

For reality, can go to Sedra & Smith

① all large capacitors short-circuited, except C_j , which is replaced by the test voltage source for R determination