
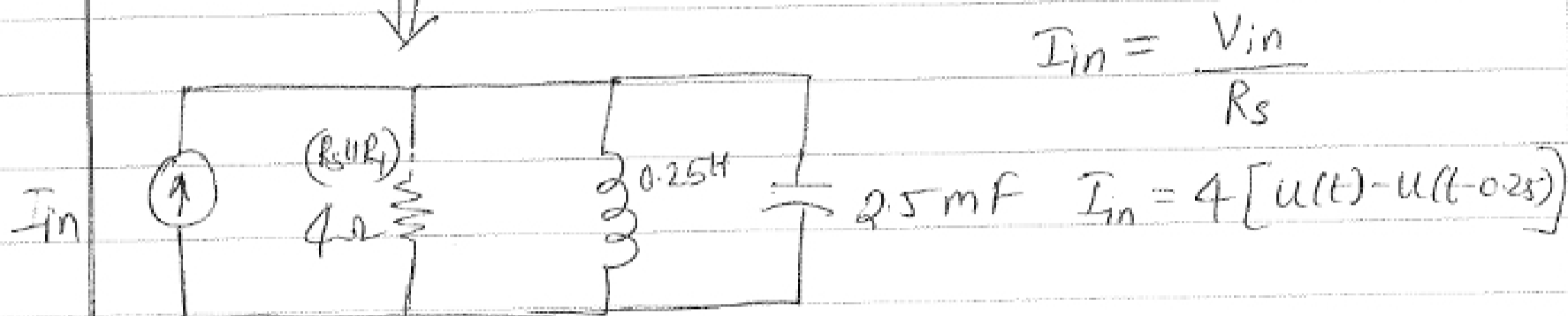


HW-25

Chap-9 (37)

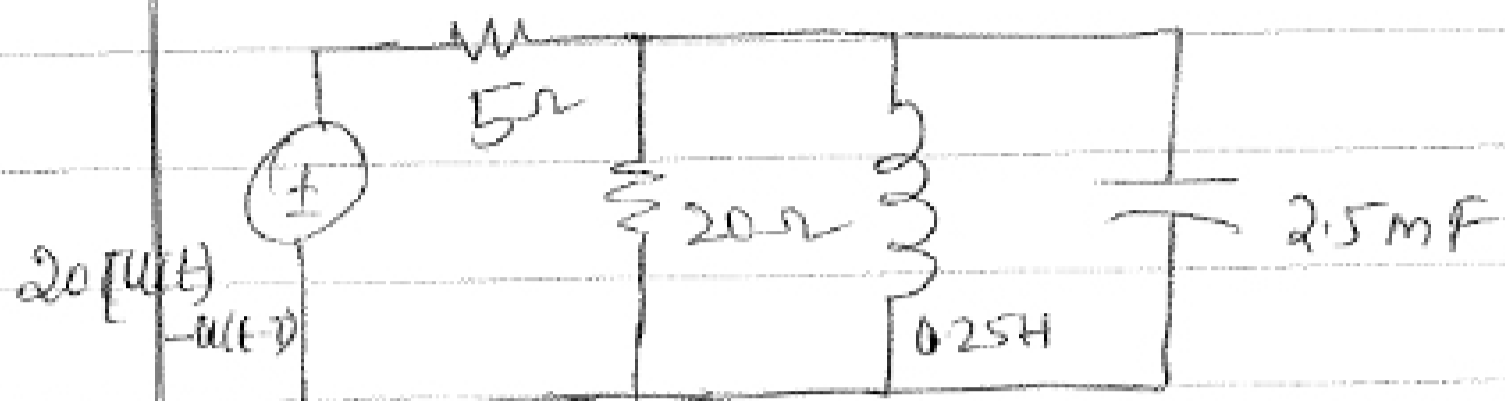

Characteristic eqn:

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$$

$$\Rightarrow s^2 + 100s + 1600 = 0$$

roots  $s_1, s_2 = -20, -80$  & real & distinct

$\Rightarrow$  overdamped response.

General form of soln  $x(t) = Ae^{s_1 t} + Be^{s_2 t} + X_F$

For  $t: 0 < t < 0.25$

Zero state response  $i_L(0) = 0$   $V_C(0) = 0$   $I_{in} = 4$

$$i_L(t) = Ae^{-20t} + Be^{-80t} + X_F : X_F = i_L(\infty) = 4$$

$$\Rightarrow i_L(t) = Ae^{-20t} + Be^{-80t} + 4$$

$$i_L(0) = A + B + 4 = 0 \Rightarrow \boxed{A + B = -4} \quad (1)$$

$$V_C(t) = V_L(t) = L \frac{di_L}{dt} = -5Ae^{-20t} - 20e^{-80t} \cdot B$$

$$V_C(0) = 0 \Rightarrow 0 = -5A - 20B \Rightarrow \boxed{-4B = A} \quad (2)$$

Solving (1) & (2) we get  $B = \frac{4}{3}$   $A = \frac{-16}{3}$

∴ Zero state response  $0 < t < 0.25$

$$i_L(t) = \frac{-16}{3} e^{-20t} + \frac{4}{3} e^{-80t} + 4$$

$$V_C(t) = \frac{80}{3} e^{-20t} - \frac{80}{3} e^{-80t}$$

⇒  $0 < t < 0.25$

Zero  $i_p$  response:  $0 < t < 0.25$

$I_{in} = 0$  From circuit conditions before  $t = 0$

$$i_L(0^-) = 0 = i_L(0^+)$$

$$V_C(0^+) = 0 = V_C(0^-)$$

$$i_L(t) = A e^{-20t} + B e^{-80t} + X_F \quad X_F = 0 \quad (\text{as its Z.I res})$$

$$\Rightarrow i_L(t) = A e^{-20t} + B e^{-80t}$$

$$i_L(0) = 0 \Rightarrow A = -B \quad \text{--- (3)}$$

$$V_C(t) = -5A e^{-20t} + (-20)B e^{-80t}$$

$$V_C(0) = 0 \Rightarrow A = -4B \quad \text{--- (4)}$$

Eqn (3) & (4) have only trivial soln @  $A = 0$  &  $B = 0$

∴ Zero  $i_p$  response:  $0 < t < 0.25$

$$i_L(t) = 0 \Rightarrow 0 < t < 0.25$$

$$V_C(t) = 0$$

This can be intuitively realized as the initial conditions are zero

the zero  $i_p$  response has to be zero, as there is nothing in the circuit to have a response.

∴ Complete response = Z.S + Z.I response

⇒ For  $t$ :  $0 < t < 0.25$

$$i_L(t) = \frac{-16}{3} e^{-20t} + \frac{4}{3} e^{-80t} + 4$$

$$V_C(t) = \frac{80}{3} e^{-20t} - \frac{80}{3} e^{-80t}$$

For  $t > 0.25$  still the circuit is overdamped as  $R, L, C$  values are the same

Zero input response  $I_{in} = 0$

We have to find initial cond @  $t = 0.25$

$$V_C(0.25) = 0.1796$$

$$i_L(0.25) = 3.964$$

$$I_{in} = 0$$

$$\Rightarrow X_F = I_L(\infty) = 0$$

$$i_C(t) = C e^{-20(t-0.25)} + D e^{-80(t-0.25)} + X_F$$

$$i_L(t) = C e^{-20(t-0.25)} + D e^{-80(t-0.25)}$$

$$\textcircled{5} \quad \text{@ } t = 0.25 \quad i_L(0.25) = 3.964 = C + D$$

$$V_C(t) = L \frac{di_L}{dt} = -5C e^{-20(t-0.25)} - 20D e^{-80(t-0.25)}$$

$$V_C(0.25) = 0.1796 = -5C - 20D \quad \textcircled{6}$$

Solving  $\textcircled{5}$  &  $\textcircled{6}$   $D = -1.333$   $C = 5.3$

$\therefore$  Zero  $i_p$  response

$$t > 0.25 \quad \left\{ \begin{array}{l} i_L(t) = 5.3 e^{-20(t-0.25)} - 1.333 e^{-80(t-0.25)} \\ V_C(t) = -26.5 e^{-20(t-0.25)} + 26.666 e^{-80(t-0.25)} \end{array} \right.$$

Zero state response :  $i_L(0.25) = 0$   $V_C(0.25) = 0$


$$\Rightarrow i_L(t) = C e^{-20(t-0.25)} + D e^{-80(t-0.25)} \quad X_F = 0$$

$$\Rightarrow i_L(0) = 0 \Rightarrow C = -D \quad \textcircled{7}$$

as  $I_{in} = 0$   
after  $0.25$

$$V_C(t) = -5C e^{-20(t-0.25)} - 20D e^{-80(t-0.25)}$$
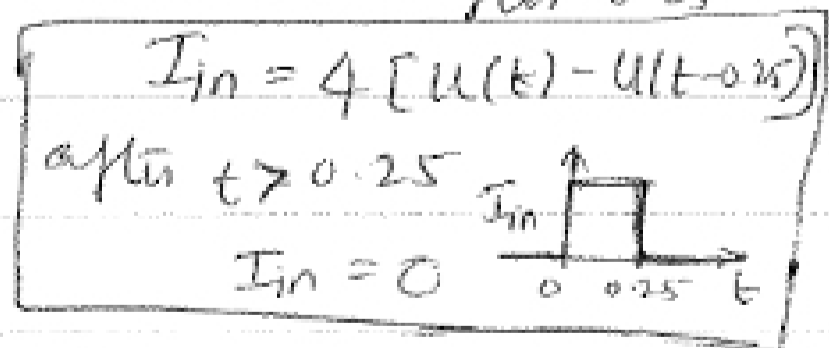
$$\Rightarrow V_C(0) = 0 \Rightarrow C = -4D \quad \textcircled{8}$$



Eqn  $\textcircled{7}$  &  $\textcircled{8}$  has just the trivial soln  $C = 0$   $D = 0$

$$\Rightarrow \left\{ \begin{array}{l} i_L(t) = 0 \\ V_C(t) = 0 \end{array} \right. \quad t > 0.25$$

Zero state response

This can also be intuitively seen, as with zero  $i_p$ s, your zero state response has to be zero and its mathematically shown