

ECE 201 Spring 2010

Homework 17 Solutions

Problem 27

(a)

Let V be the common voltage across C_1 and C_2 . Thus

$$\begin{aligned}(C_1 + C_2) \frac{dV}{dt} &= i_s(t) \\ C_2 \frac{dV}{dt} &= i_{C_2}(t) \\ \Rightarrow i_{C_2}(t) &= \frac{C_2}{C_1 + C_2} i_s(t)\end{aligned}$$

(b)

Using KVL across the second loop and relation from part (a), we get

$$\begin{aligned}r_m i_{C_2}(t) - (L_1 + L_2) \frac{di}{dt} &= 0 \\ v_{out}(t) &= L_2 \frac{di}{dt} \\ &= r_m \frac{L_2 C_2}{(L_1 + L_2)(C_1 + C_2)} i_s(t)\end{aligned}$$

Problem 38

(a)

Starting from the right end and combining the inductors in series and parallel consecutively, we get L_{eq} as

$$\begin{aligned}L_{eq} &= 4 + ((36) \parallel (10 + ((1 + 5) \parallel (3)))) \\ &= 4 + ((36) \parallel (10 + ((6) \parallel (3))))\end{aligned}$$

$$\begin{aligned}
&= 4 + ((36) \parallel (10 + (2))) \\
&= 4 + ((36) \parallel (12)) \\
&= 4 + 9 \\
&= 13 \text{ mH}
\end{aligned}$$

(b)

Clearly, the given circuit has 1.2 mH and 0.6 mH in parallel, and this combination is in series with 2.4 mH, the equivalent of which is in parallel with 7 mH. Thus

$$\begin{aligned}
L_{eq} &= 7 \parallel (2.4 + (1.2 \parallel 0.6)) \\
&= 7 \parallel (2.4 + 0.4) \\
&= 7 \parallel 2.8 \\
&= 2 \text{ mH}
\end{aligned}$$

Problem 41

(a)

Remember that the equivalent capacitance expressions for series and parallel connections are opposite of that used for resistances. The equivalent capacitance can be written as

$$\begin{aligned}
C_{eq} &= C_1 \parallel (C_2 + (C_3 \parallel C_4)) \\
&= 4 + \frac{6 \times 3}{9} \\
&= 6 \mu F \\
v_s(t) &= \frac{1}{C_{eq}} \int_{-\infty}^t i_s(\tau) d\tau \\
&= \frac{1}{6} \sin(10^4 t) \text{ V}
\end{aligned}$$

(b)

$$C_{eq} = C_1 \parallel (C_2 + (C_3 \parallel C_4) + C_5)$$

$$\begin{aligned}(C_2 + (C_3 || C_4) + C_5) &= \left(\frac{1}{18} + \frac{1}{54} + \frac{1}{10.8} \right)^{-1} \\ &= 6 \mu F \\ \Rightarrow C_{eq} &= 6 + 60 \\ &= 66 \mu F \\ v_s(t) &= \frac{1}{C_{eq}} \int_{-\infty}^t i_s(\tau) d\tau \\ &= \frac{1}{660} (1 - \cos(10^5 t)) V\end{aligned}$$